

## COLLEGE OF ENGINEERING & COMPUTER SCIENCE

## **Pick Pocket Tuner**

Senior Design I - Group 42 Fall 2021

Lucas Grayford - Electrical Engineering Paul Grayford - Electrical Engineering Luis Vargas – Computer Software Engineering Jamie Henry – Computer Software Engineering

Project advisor: Dr. Samuel Richie

## Table of Contents

Table of Figuresv
Table of Tables vi
Table of Equationsvi
1.0 Executive Summary1
2.0 Project Narrative
2.1 Participant Identification2
2.2 Project Motivation2
2.3 Project Description2
2.4 Features and Options3
2.5 Stretch Goals4
2.6 Restrictions and Constraints4
3.0 COVID-19 Supply Chain Issues
3.1 COVID-19 Supply Mitigation Plan4
4.0 Budget Constraints
4.1 Budget Mitigation Plan5
5.0 Weekly Scheduled Meetings6
6.0 Miscellaneous Constraints
7.0 Design Process
7.1 Technical Investigation7
7.2 Applications of Engineering Fundamentals7
7.3 Preliminary Testing8
7.4 Subsystem Testing8
7.5 Overall Testing9
8.0 House of Quality Diagram9
9.0 Competition
10.0 Tuning Background
11.0 Hardware Block Diagram 15
12.0 Physical Components 16
<b>12.1.1 ¼" Output Jack</b>

12.1.4 Preliminary Testing Results 12.1.5 Implementation	
<b>12.2 Motor</b> 12.2.1 Motor Testing 12.2.2 Motor Research 12.2.3 Motor Conclusion	
<b>12.3 Driver/Pulse Width Modulator</b> 12.3.1 Driver/Pulse Width Modulator Testing 12.3.2 Driver/Pulse Width Modulator Conclusion/Encoder	24
<b>12.4 Peg Winder</b> 12.4.1 Peg Winder Testing	
12.5 Filament and Cura	27
<b>12.6 Battery</b> 12.6.1 Battery Theory	
<b>12.7 Switch and Buttons</b>	
12.8 Housing Theory	
12.9 Buzzer	
12.10 Vibration Sensor	
12.11 Display	
12.11 Display	
<ul><li>12.11 Display</li><li>12.12 Analog to Digital Converter</li></ul>	
<b>12.12 Analog to Digital Converter</b> 12.12.1 Selection of ADC 12.12.2 Testing Process	
<b>12.12 Analog to Digital Converter</b> 12.12.1 Selection of ADC 12.12.2 Testing Process 12.12.3 Testing Results	
<b>12.12 Analog to Digital Converter</b> 12.12.1 Selection of ADC 12.12.2 Testing Process. 12.12.3 Testing Results. 12.12.4 Implementation.	<b></b>
<b>12.12 Analog to Digital Converter</b> 12.12.1 Selection of ADC         12.12.2 Testing Process         12.12.3 Testing Results         12.12.4 Implementation <b>12.13 Voltage regulators</b>	
<b>12.12 Analog to Digital Converter</b> 12.12.1 Selection of ADC         12.12.2 Testing Process         12.12.3 Testing Results         12.12.4 Implementation <b>12.13 Voltage regulators</b> 12.13.1 Prototyping Regulation	<b></b>
<b>12.12 Analog to Digital Converter</b> 12.12.1 Selection of ADC         12.12.2 Testing Process         12.12.3 Testing Results         12.12.4 Implementation <b>12.13 Voltage regulators</b> 12.13.1 Prototyping Regulation         12.13.2 Voltage Regulation Strategy         12.13.3 Buck Converters	<b></b>
<ul> <li>12.12 Analog to Digital Converter</li></ul>	<b></b>
<ul> <li>12.12 Analog to Digital Converter</li></ul>	<b></b>
<ul> <li>12.12 Analog to Digital Converter</li></ul>	<b></b>
<ul> <li>12.12 Analog to Digital Converter</li></ul>	<b></b>
<ul> <li>12.12 Analog to Digital Converter</li></ul>	<b></b>
<ul> <li>12.12 Analog to Digital Converter</li></ul>	<b></b>
<ul> <li>12.12 Analog to Digital Converter.</li> <li>12.12.1 Selection of ADC.</li> <li>12.12.2 Testing Process.</li> <li>12.12.3 Testing Results.</li> <li>12.12.4 Implementation</li> <li>12.13 Voltage regulators</li> <li>12.13.1 Prototyping Regulation</li> <li>12.13.2 Voltage Regulation Strategy.</li> <li>12.13.3 Buck Converters.</li> <li>12.13.4 Voltage Regulator Designs, 3.3V</li> <li>12.13.5 Regulator Schematic and Specifications, 3.7-12V</li> <li>12.13.6 Ordering Process for Regulators</li> <li>12.13.7 Testing Process for Regulators</li> <li>12.13.8 Implementation of Voltage Regulators</li> <li>12.14 Processor / Controller</li> <li>12.15 Clock</li> </ul>	<b></b>
<ul> <li>12.12 Analog to Digital Converter</li></ul>	<b></b>
<ul> <li>12.12 Analog to Digital Converter</li></ul>	38 38 38 39 39 39 39 39 40 40 40 41 41 41 41 41 41 43 44 44 44 45 45 45 46 46 46 48
<ul> <li>12.12 Analog to Digital Converter</li></ul>	38 38 38 39 39 39 39 39 40 40 40 41 41 41 41 41 41 43 43 44 44 45 45 46 46 46 48 48
<ul> <li>12.12 Analog to Digital Converter</li></ul>	38 38 38 39 39 39 39 40 40 40 40 41 41 41 41 41 41 43 43 44 45 45 46 46 46 46 48 48 49

12.16.6 Implementation Process for MCP73831/2 12.16.7 Prototyping Charging Circuit	
12.16.8 Testing Charging Circuit	
12.16.9 Prototype Charging Circuit Implementation	
12.16.10 Using the Prototype as Plan B	
12.16.11 Mounting Prototype in Housing	
12.16.12 Testing Process 12.16.13 Implementation Plan	
13.0 Printed Circuit Board Design	
13.1 Overall Layout of PCB	
13.2 Power Distribution	
13.3 Fusion 360	55
13.4 Collaboration Method	55
13.5 Designing Components Using Fusion 360	56
13.6 Supplier	58
13.6.1 How to Order from JLCPCB	58
13.7 PCB Assembly	59
13.8 Testing the PCB	60
14.0 Prototype Construction	60
14.1 Prototype Construction Beginning Notes	60
14.1 Frototype construction beginning Notes	
14.2 Prototyping Components	60
14.2 Prototyping Components	<b>60</b>
<b>14.2 Prototyping Components</b> 14.2.1 Processor/Controller 14.2.2 Sensor	60 60 61
<b>14.2 Prototyping Components</b> 14.2.1 Processor/Controller 14.2.2 Sensor 14.2.3 Motor	60 60 61 61
<b>14.2 Prototyping Components</b> 14.2.1 Processor/Controller 14.2.2 Sensor	
<b>14.2 Prototyping Components</b> 14.2.1 Processor/Controller14.2.2 Sensor14.2.3 Motor14.2.4 Motor Driver14.2.5 LCD Display14.2.6 USB-C Charging Circuit	
<b>14.2 Prototyping Components</b> 14.2.1 Processor/Controller14.2.2 Sensor14.2.3 Motor14.2.4 Motor Driver14.2.5 LCD Display	
14.2 Prototyping Components14.2.1 Processor/Controller14.2.2 Sensor14.2.3 Motor14.2.4 Motor Driver14.2.5 LCD Display14.2.6 USB-C Charging Circuit14.2.7 Battery	
14.2 Prototyping Components         14.2.1 Processor/Controller         14.2.2 Sensor         14.2.3 Motor         14.2.4 Motor Driver         14.2.5 LCD Display         14.2.6 USB-C Charging Circuit         14.2.7 Battery         14.3 Additional Components in Prototype Construction         14.3.1 Piezo Sensor Filter	
<ul> <li>14.2 Prototyping Components</li> <li>14.2.1 Processor/Controller</li> <li>14.2.2 Sensor</li> <li>14.2.3 Motor</li> <li>14.2.4 Motor Driver</li> <li>14.2.5 LCD Display</li> <li>14.2.6 USB-C Charging Circuit</li> <li>14.2.7 Battery</li> </ul> 14.3 Additional Components in Prototype Construction <ul> <li>14.3.1 Piezo Sensor Filter</li> <li>14.3.2 DC-IN Power for Breadboard</li> </ul>	60 60 61 61 62 62 63 63 63 63 63 63 63 63
<ul> <li>14.2 Prototyping Components</li> <li>14.2.1 Processor/Controller</li> <li>14.2.2 Sensor</li> <li>14.2.3 Motor</li> <li>14.2.4 Motor Driver</li> <li>14.2.5 LCD Display</li> <li>14.2.6 USB-C Charging Circuit</li> <li>14.2.7 Battery</li> </ul> 14.3 Additional Components in Prototype Construction <ul> <li>14.3.1 Piezo Sensor Filter</li> <li>14.3.2 DC-IN Power for Breadboard</li> <li>14.3.3 3D Printed Guitar Peg-Winder</li> </ul>	
<ul> <li>14.2 Prototyping Components</li> <li>14.2.1 Processor/Controller</li> <li>14.2.2 Sensor</li> <li>14.2.3 Motor</li> <li>14.2.4 Motor Driver</li> <li>14.2.5 LCD Display</li> <li>14.2.6 USB-C Charging Circuit</li> <li>14.2.7 Battery</li> </ul> 14.3 Additional Components in Prototype Construction <ul> <li>14.3.1 Piezo Sensor Filter</li> <li>14.3.2 DC-IN Power for Breadboard</li> </ul>	
14.2 Prototyping Components14.2.1 Processor/Controller14.2.2 Sensor14.2.3 Motor14.2.4 Motor Driver14.2.5 LCD Display14.2.6 USB-C Charging Circuit14.2.7 Battery14.3 Additional Components in Prototype Construction14.3.1 Piezo Sensor Filter14.3.2 DC-IN Power for Breadboard14.3.3 3D Printed Guitar Peg-Winder14.4 Next Prototype Construction Steps and Ending Notes	
14.2 Prototyping Components         14.2.1 Processor/Controller         14.2.2 Sensor         14.2.3 Motor         14.2.4 Motor Driver         14.2.5 LCD Display         14.2.6 USB-C Charging Circuit         14.2.7 Battery         14.3 Additional Components in Prototype Construction         14.3.1 Piezo Sensor Filter         14.3.2 DC-IN Power for Breadboard         14.3.3 3D Printed Guitar Peg-Winder         14.4 Next Prototype Construction Steps and Ending Notes         15.0 Inside of the Jowoom	
14.2 Prototyping Components         14.2.1 Processor/Controller         14.2.2 Sensor         14.2.3 Motor         14.2.4 Motor Driver         14.2.5 LCD Display         14.2.6 USB-C Charging Circuit         14.2.7 Battery         14.3 Additional Components in Prototype Construction         14.3.1 Piezo Sensor Filter         14.3.2 DC-IN Power for Breadboard         14.3.3 3D Printed Guitar Peg-Winder         14.4 Next Prototype Construction Steps and Ending Notes         15.0 Inside of the Jowoom         16.0 PCB Layout	60 60 61 61 62 62 63 63 63 63 63 63 64 64 64 64 64 64 65 68 68 69
14.2 Prototyping Components         14.2.1 Processor/Controller         14.2.2 Sensor         14.2.3 Motor         14.2.4 Motor Driver         14.2.5 LCD Display         14.2.6 USB-C Charging Circuit         14.2.7 Battery         14.3 Additional Components in Prototype Construction         14.3.1 Piezo Sensor Filter         14.3.2 DC-IN Power for Breadboard         14.3.3 3D Printed Guitar Peg-Winder         14.4 Next Prototype Construction Steps and Ending Notes         15.0 Inside of the Jowoom         16.0 PCB Layout         16.1 Ultra Librarian	60 60 61 61 62 62 63 63 63 63 63 63 64 64 64 64 64 64 64 64 65 68 68 69 69
14.2 Prototyping Components         14.2.1 Processor/Controller         14.2.2 Sensor         14.2.3 Motor         14.2.4 Motor Driver         14.2.5 LCD Display         14.2.6 USB-C Charging Circuit         14.2.7 Battery         14.3 Additional Components in Prototype Construction         14.3.1 Piezo Sensor Filter         14.3.2 DC-IN Power for Breadboard         14.3.3 3D Printed Guitar Peg-Winder         14.4 Next Prototype Construction Steps and Ending Notes         15.0 Inside of the Jowoom         16.1 Ultra Librarian         16.2 PCB Parts Placement	

17.0 Project Summary – Hardware	
18.0 Prototype Testing	
18.1 Prototype Testing Beginning Notes	75
18.2 Prototype Component Testing	
18.2.1 ESP8266 Testing 18.2.2 Piezo Sensor and Filter Testing	
18.2.3 Motor Testing	
18.2.4 LCD Display Testing	82
18.2.5 FFT Input Testing 18.2.6 USB-C Charging Circuit and Battery Testing	
18.3 Next Prototype Testing Steps and Ending Notes	
19.0 Software Block Diagram	
20.0 Algorithm	86
21.0 Software Features/Functions	86
21.1 Fast Fourier Transform	86
21.2 Tuning a New String	87
21.3 Display Interface	87
21.4 Tuning Libraries (Stretch Goal)	88
21.5 Tuning Other Instruments (Stretch Goal)	88
21.6 Programming Language(s)	89
21.7 Programming/Software Libraries	89
22.0 UI/UX Software Hierarchy and Design	
22.1 Software Hierarchy Description	92
22.2 Software Tuning	92
22.3 Software Display	94
22.4 Handling Flat and Sharp Notes	96
22.5 Math for Voltage Sent to Motor	97
22.6 New String Mode	98
22.7 Autotune Mode	
22.8 Free Move Mode	
23.0 Software Summary	102
24.0 Project Budget Estimates	102
24.1 Final Prototype Cost (Estimated Range)	
24.2 Project Development Costs	
24.3 Development Cost (Estimated Range)	

25.0 Project Milestones	05
26.0 Hardware & Software Requirement Specifications Tables	06
26.1 Hardware Requirement Specifications10	06
26.2 Software Requirement Specifications1	10
27.0 Final Testing Plan 11	13
27.1 Objective for Final Testing1	13
27.2 Description of Final Testing Environment1	13
27.3 Stopping Criteria1	15
27.4 Description of Individual Test Cases1	15
27.5 Trace of Individual Test Cases to Requirements12	21
28.0 Conclusion	22
Bibliography	. <i>A</i>

## Table of Figures

FIGURE 1, HOUSE OF QUALITY DIAGRAM	10
FIGURE 2, REPRESENTATION OF PHYSICAL COMPONENTS ON AN ELECTRIC GUITAR	14
FIGURE 3, REPRESENTATION OF PHYSICAL COMPONENTS ON A VIOLIN	14
FIGURE 4, HARDWARE BLOCK DIAGRAM	15
FIGURE 5, COMPARISON OF PURE TONE OUTPUT JACK TO A STANDARD STEREO OUTPUT JACK	17
FIGURE 6, 5V STEPPER MOTOR (MODEL: 28BYJ-48)	
FIGURE 7, BRUSHLESS DC MOTOR WITH ENCODER 12V 159RPM	21
FIGURE 8, LINE CONNECTIONS FOR ARDUINO (WILL VARY FROM ESP8266 CONNECTIONS SLIGHTLY)	22
FIGURE 9, 12V DC MOTOR DIMENSIONS IN MM	23
FIGURE 10, UL2003 DRIVER BOARD (LEFT), L298N MOTOR DRIVER CONTROL BOARD (RIGHT)	24
FIGURE 11, UNIVERSAL PEG WINDER HEAD	26
FIGURE 12, 3.7V LITHIUM ION POLYMER 1200 MAH BATTERY	
FIGURE 13, ROCKER SWITCH WITH LEAD WIRES	
FIGURE 14, FULL BUTTON LAYOUT FOR CONNECTIONS	
FIGURE 15, MULTICOLOR CHANGEABLE BUTTONS	
FIGURE 16, JOWOOM GUITAR TUNER	34
FIGURE 17, HYDZ 3-5V BUZZER	
FIGURE 18, ROUNDED IPS-TFT LCD DISPLAY	37
FIGURE 19, REGULATION DIAGRAM	
FIGURE 20, DESIRED VOLTAGE REGULATOR DESIGN	
FIGURE 21, SCHEMATIC DESIGN CHOICE	42
FIGURE 22, 12V REGULATOR DESIGN	43
FIGURE 23, ESP8266 ON NODEMCU DEVELOPMENT BOARD	46
FIGURE 24, CHARGING CIRCUIT DESIGN WITH LM317 (INTELLECTUAL DESIGN PROVIDED BY TEXAS	
INSTRUMENTS)	47
FIGURE 25, SIMPLE APPLICATION CIRCUIT BY MICROCHIP	
FIGURE 26, LIPO CHARGING CIRCUIT TO BE USED IN PROTOTYPING AND TESTING PHASE OF PROJECT	50
FIGURE 27, IMAGE OF ADAFRUIT CHARGER SHOWING MOUNTING HOLES	52

FIGURE 28, STUDENT-MADE PIEZOELECTRIC SENSOR (SYMBOL ON LEFT AND FOOTPRINT ON RIGHT)	57
FIGURE 29, ARTISTIC RENDITION OF THE INITIAL PROTOTYPE MOCK-UP	65
FIGURE 30, JOWOOM INTERNALS	67
FIGURE 31, JOWOOM INTERNALS FRONT SIDE	68
FIGURE 32, PCB PROTOTYPE	71
FIGURE 33, JOWOOM AUTOMATIC TUNER (DECONSTRUCTED) SHOWING TWO PIEZOELECTRIC SENSORS IN	
PARALLEL	78
FIGURE 34, BREADBOARD PROTOTYPE DEMONSTRATING IPHONE SPEAKER VIBRATION/TONE TEST	80
FIGURE 35, OSCILLOSCOPE FREQUENCY FROM PIEZO SENSOR, IPHONE TEST	80
FIGURE 36, OSCILLOSCOPE FREQUENCY FROM PIEZO SENSOR, IPHONE TEST, WITH FILTER	81
FIGURE 37, SOFTWARE BLOCK DIAGRAM	85
FIGURE 38, UI/UX SOFTWARE HIERARCHY/DESIGN	91
FIGURE 39, LCD DISPLAY TENTATIVE GUI LAYOUT DURING TUNING	95
FIGURE 40, NATURAL NOTES WRITTEN ON THE KEYS OF A KEYBOARD	96
FIGURE 41, RELATION BETWEEN DEGREES PER STEP AND PULSES PER REVOLUTION	

## Table of Tables

TABLE 1, REQUIREMENT SPECIFICATIONS	
TABLE 2, FREQUENCIES FOR A GUITAR STANDARD TUNING	13
TABLE 3, CRITICAL SPECIFICATIONS FOR EFFICIENT REGULATORS	42
TABLE 4, CRITICAL SPECIFICATIONS FOR CHOSEN REGULATOR	42
TABLE 5, CRITICAL SPECIFICATIONS FOR 12V REGULATOR	
TABLE 6, POWER DISTRIBUTION CALCULATIONS (INCOMPLETE TABLE)	54
TABLE 7, MOTOR PIN CONNECTIONS	
TABLE 8, DISPLAY PIN CONNECTION	
TABLE 9, PUSH BUTTON PIN CONNECTIONS	
TABLE 10, FREQUENCY DEVICE PIN CONNECTS	74
TABLE 11, FFT COMPUTATION TIME BASED ON DURATION OF TEST FREQUENCY	93
TABLE 12, AVERAGE COMPUTATION TIME FOR THE FFT USING SCIPY AND NUMPY	93
TABLE 13, FLAT/NATURAL/SHARP FREQUENCY EXAMPLE STARTING AT MIDDLE C	97
TABLE 14, FREQUENCY EXAMPLES OF ONE HIGHER AND LOWER OCTAVE FOR EACH FREQUENCY	99
TABLE 15, DEMONSTRATING ONE AND TWO STEP OFFSET TUNING FROM E STANDARD TUNING	
TABLE 16, ESTIMATED FINAL COST FOR DEVICE	103
TABLE 17, ESTIMATED COST FOR DEVELOPMENT OF PROJECT	
TABLE 18, PROJECT MILESTONES CHART	106

# Table of Equations No table of figures entries found.

## 1.0 Executive Summary

To tune a stringed instrument, a peg is used for tightening or loosening the string threaded into a cylinder. This peg usually consists of a worm drive and the peg head or key. The worm drive consists of a screw-like gear and a spur gear to create a smaller volume object with similar gear ratios. Some players also use peg locks to help ensure that the peg will stay in place to help reduce loss in tuning on the string.

The purpose of tuning a stringed instrument is to create sounds that illicit emotions in those who hear and play it. Tuning the strings to the correct pitches ensures that all notes that can be played on the instrument will make the correct sounds and will create captivating music. To ascertain that the tuning of a stringed instrument is correct, the user would match the frequency of the plucked string to a known frequency, such as a tuning fork or another audible device, by ear. However, tuning stringed instruments by ear could lead to incorrect tuning and incorrect pitches across the strings. This has led to the creation of automatic guitar tuners to eliminate human error and make the tuning process faster.

Sensors are used by these automatic guitar tuners to help eliminate the human error. These include vibrational and microphone sensors that pick up the frequency of the plucked string. This gives an accurate reading of the string's frequency that can then be compared to the tuning specifications. Our group's Pick Pocket guitar tuner will use a Piezo vibrational sensor that will sit in the housing of the product to pick up that string's frequency. This frequency, read in as analog voltage, will then have to be transformed into the frequency domain to read its value. To achieve this, the Fast Fourier Transform will be used. The Fast Fourier Transform was chosen as opposed to the Discrete Fourier Transform solely on computation time. Since time is valuable to our automatic tuner and is one of the deciding factors among competitors.

The main purpose of his transform is to have the sensor's input value as a value in Hz to compare to the desired string frequency the user picked. Our tuner will then figure out the magnitude of the difference of the two frequency values and send voltage to the brushless DC motor accordingly. The motor will then spin the peg winder that is designed to fit a wide array of pegs to allow for the tuning of multiple instruments. When the desired frequency is met, auditory and visual feedback will let the user know to move on to the next string.

To compete with the existing automatic guitar tuners, our group's focus was to capitalize on cost efficiency, computation/tuning time, and the ability to tune multiple string instruments. These aspects were researched heavily along with dismantling of some competitors' tuners to meet these requirements. Another way to compete with the market was to have our tuner have multiple modes for everyday string instrument use. This would include tuning new strings and freely tuning the guitar to the desired pitch with added visuals of what note the frequency is closest to. With the creation of the prototype, further testing will be conducted on the algorithm/software created to tune the instruments within 5 cents accuracy to further develop the tuner and within the desired time frame.

## 2.0 Project Narrative

#### 2.1 Participant Identification

The proposal for our Senior Design project is, tentatively, called Pick Pocket Tuner, an automatic guitar tuner that facilitates quick tuning a guitar within a small timeframe. Group number 42 consists of the following members: Lucas Grayford, Paul Grayford, Jamie Henry, and Luis Vargas. The composition of the group by academic major consists of two Electrical Engineering majors, Lucas and Paul, and two Computer Engineering majors, Jamie and Luis.

Currently there are no defined sponsors, or financiers, to the project beyond the members of Group 42, however the groups are in contact with the College of Music at the University of Central Florida for potential financial support for the project to lessen the financial burden on the group members.

### 2.2 Project Motivation

The main motivation is to assist musicians, specifically guitar players, in tuning their instruments quickly, and accurately in any environment. Usually tuning a guitar accurately, is a tedious process that can take quite some time away from a musician. When on stage, recording, or just at a jam session, environmental noise is a thing that needs to be accounted for, and a tuner with a ¼-inch input isn't always readily available or the musician needs to tune as they're playing. However, we are also trying to add the option of tuning with a ¼ -inch cable for guitarists who can use this accurate form of measurement.

When starting out to learn the guitar, one of the most intimidating roadblocks is tuning the guitar correctly. Anyone should be able to learn an instrument, and this is a way in which our product could help people feel more confident in picking the guitar up. Whether the guitarist is just a beginner, or an expert playing in front of fans, we want to create an accurate, fast way of tuning that is comfortable and easy to use.

#### 2.3 Project Description

Through preliminary discussions within Group 42, the Pick Pocket Tuner will include a motor, a screen, buttons, a power switch, a controller, two sensors, and a basic housing to keep it all enclosed. As a method of powering the device, the group is still doing further research to determine if they will be doing replaceable or rechargeable batteries for powering the device. As far as determining the method to find the frequency at which the strings on the guitar are reverberating at is to use two sensors, a microphone, and a

vibration sensor. The microphone can be used as a traditional tuner to analyze the frequency at which the strings are vibrating to then adjust the tuning peg.

The method of operation is as follows: the user will take this portable device, and it will have a screen and button interface that would allow the user to interact with the software interface that would give feedback to the user on whether the string is in tune once it is in use. The device will then be placed with the tuning peg device on the tuning peg itself, and the user will strum the desired string to be tuned. The device will then use one, or both, of the sensors within to determine the vibrational frequency and then direct the motor to either adjust the string tension by turning the tuning peg clockwise or counterclockwise. While still being researched further to determine

exactly what part to use, a controller of sorts will be the 'brain' of the operation that will take the information from the sensors through UART, SPI, or I2C, and calculate how much power to give the motor and which direction to turn it to accomplish the accurate string tension for the correct string tuning.

Requirement Specifications	Measurement	Units	Interval
Tune a guitar in a maximum time	3	minutes	±1
String a new guitar in a maximum time	5	minutes	±1
Tune strings to the correct frequency	1	cents	±5
Battery life with respect to strings tuned	100	strings	±15
Max weight	2	pounds	±0.5
Ease-of-use interface with respect to time to select and tune a string	45	seconds	±10

Table 1, Requirement Specifications

## 2.4 Features and Options

After discussions within the group, and technical research, we have decided that the following list would add good functionality as a standard set of features and options to the Pick Pocket Tuner:

- Comfortable, ergonomic, and able to fit in one hand
- Ability to tune a guitar to alternative tunings (Drop-D, Drop-C, DADGAD, etc..)
- Tune new strings quickly from start to finish
- Input jack for tuning with a quarter inch cable

Our team believes that including these features and options, would give us a quality device we can be proud of by the end of senior design 2. We are hopeful that we will accomplish all of these while staying on time and keeping costs low.

#### 2.5 Stretch Goals

After discussions within the group, and technical research, we have decided that the following list would constitute as a good set of stretch goals to be implemented into the Pick Pocket Tuner:

- Ability to tune other stringed instruments like a ukulele or a banjo
- Tune the instrument faster and more accurately

### 2.6 Restrictions and Constraints

After initial discussion and considerations, our group has determined that this is a list of the most crucial restrictions and constraints that we would face while developing, prototyping, and testing the Pick Pocket Tuner:

- Budget of the project
- Allotting enough time for the project
- Steep learning curves
- Supply chain issues (Difficulty in part acquisition)
- Competition in the market

There are no federal restrictions to be aware of while completing the project. We feel these requirements would demonstrate satisfactory engineering qualities on both the software and hardware side of things. Below are flowcharts that show how these requirements will be achieved on both ends of the spectrum.

## 3.0 COVID-19 Supply Chain Issues

One of the most constraining issues that our group will be attempting to overcome is the supply chain issues that are happening in the world today due to the COVID-19 pandemic. Electronics specifically are suffering a lot due to the pandemic, and an increase in demand does not help the situation. As our group is trying to order different components, we run across issues of large delays, specifically, when trying to order a voltage regulator for the device. We have seen delays for almost two months, so our team has decided to come up with a mitigation plan.

#### 3.1 COVID-19 Supply Mitigation Plan

One of the last components that we will have to implement in our device is our voltage regulator, which seems to have the most concern of arriving on time. Setting a plan in place to prepare for this is crucial to being able to deliver a product that will be functional by the end of the semester.

The first crucial step in this mitigation plan will be ordering almost all the other components that we will be using. This does not mean resistors and capacitors necessarily, but components like the display, sensor, output jack, motor/driver, etc. Once these parts are determined, we will be able to find the power consumed by all of the components and be able to choose a voltage supply that will meet all of our design requirements. Once this is determined, we will be able to pick a regulator for the system. All of this being stated, we need to have all these components picked out, ordered, and tested by January 28<sup>th</sup>, 2022. This will give us about two chances to pick the correct regulator. This is not ideal, however, if the supply chain issues do not improve, this will be best case scenario.

Even though this will be a difficult issue for our team to overcome, it will provide us with great experience on how to deal with these issues once we get jobs in the engineering industry. It will also make sure we do not procrastinate and get most of our work done on a strict schedule, allowing us a stress-free integration process. Some may find it easy to look at all the negative ramifications of the supply chain issues happening right now, but our team is trying to look at the positive side, by using it as a tool to help us stay way ahead of schedule.

## 4.0 Budget Constraints

Our group was unable to secure a sponsor for our project, so the budget will be split up between all of the group members easily. Since our expenses are coming from out of our own pockets, the team will have to be careful not to make any unnecessary purchases, and we will have to be extra careful when prototyping our project, to not burn or damage any components we plan on using in our final design.

## 4.1 Budget Mitigation Plan

Even though our team must foot the bill for the entire project, it gives us an opportunity to learn how to improve our money handling skills. Our plan is quite simple, yet hopefully effective. We are currently recording the costs of everything anyone purchases in an excel document. At the end of senior design 2, we will be splitting the cost in four even amounts, and we will pay each other back once all is said and done. Since we are all aware of the fact that we will be sheeling out our own money for this project, it will allow us to pay attention to detail and keep waste to a minimum and efficiency to the maximum. Also, it will provide us an opportunity to research more about all of our components before we make a decision on buying certain products.

Using our own budget for this project could be looked at as a huge constraint, however, our team seems to be responding well, and everyone is on the same page about spending each other's money. We will have to be extra focused and stay on top of schedule to avoid paying any extra fees due to expedited shipping or ordering things last minute that could cost more money than we would want to. Staying ahead of schedule will not just give us peace of mind for our project itself, but it will also allow us to not have to spend so much money.

## 5.0 Weekly Scheduled Meetings

Every week we plan to have group meetings to discuss the progress of what has been completed and what needs to be completed. Some meetings are arranged in an online means too if there are incidents that keep members from having to be remote for reason that may be deemed reasonable. These regularly scheduled meetings are an important requirement that is needed to keep the team focused as a whole. They help with keeping track of what each member needs to do and get taken care of. They also allow team members to work together when maybe one team member is stuck and needs help completing a task so that they can keep up with the group. These meetings are typically held in the library every Tuesday and Thursday from usually 9AM-12AM. There may need to be more meetings to keep track of tasks that are getting done and or need to get done. Most meetings have been productive but have most of the time been for check ins or updates on the tasks at hand. Most of the members have a full load of classes so it makes it harder to accommodate for each member. We have also used ClickUp which allows planning and dividing of tasks for the main parts that need to be done each time.

A good amount of timing issues needed to be taken care of mainly due to other class loads and outside jobs that members have to do. All members have been understanding towards the daily struggles that each member has outside lives and other important tasks or issues that may arise. There have been a few missed meeting days that have happened but not a substantial amount to cause any major issues with progress. Some meetings have ended in a stuck scenario on what to do next or how to go about the next task that needs to get done. There are different ways to solve each issue, it just comes down to determining which is the right method to go about getting it done.

## 6.0 Miscellaneous Constraints

There are many constraints one can run into while designing and producing a project. Time constraints are very common, hence why keeping a strict schedule is so important. Our team is overall a very busy group, so it is essential to complete all of our schoolwork on time or early. This especially includes classes outside of senior design 1. If we are not performing well in any of the classes we are taking, then senior design will suffer significantly, and this needs to be avoided at all costs.

Another constraint can be the lack of knowledge we might have in certain areas of our project. Working on a project can be discouraging if we get stuck or just have a hard time understanding certain concepts. This gives us an opportunity for growth in skill and knowledge of the projects we are working on. This does not only include our senior design project, but on any project, we might be working on outside of school. Also remembering that we are not alone is important when questions like these arise. We have resources on the internet, but if we are not experiencing any progress, then we have so many resources that the college can offer us.

There is a wealth of knowledge at our disposal, and we must take advantage of that. This constraint can greatly affect our project by reducing the amount of time we are able to

spend on building and designing other parts of our device. The longer we are stuck on something, the shorter amount of time we have to make a working useable project.

## 7.0 Design Process

An effective design process will be essential to meet all deliverables for the year. Our design process will consist of technical investigation, application of engineering fundamentals, and testing (preliminary testing, subsystem testing and overall testing). These will keep us on the correct track and allow us to learn a lot about each of the components we chose for our project. It will allow us to manipulate the components in a way that will give us the best results.

#### 7.1 Technical Investigation

Our project starts with a great amount of technical investigation. All of the investigation our team conducts will act as the backbone of our project. Without going through datasheets, surfing websites, watching essential videos, we would not even be able to begin working on our project. As the team becomes more familiar with the components we plan on ordering, the more likely we will be able to make them work together quickly and easily.

The goal is to compare at least three different products we could use for one component and go through all the datasheets and reviews and see how easy they are to implement with our other products and narrow them down to one final product we order. However, if for some reason the product we order does not work, we would hopefully have two viable back up options we could use as a second option. This will come in handy if one of our components is not behaving like we expected them to because we will not be starting from square one again. Technical investigation is another key element to this project, and we hope to be able to conduct research effectively, and thoroughly as to not suffer when the time comes to assemble our product.

#### 7.2 Applications of Engineering Fundamentals

Throughout our time at college, we have learned how to think critically and attack different problems in all sorts of fashions. This project gives us students an opportunity to apply what we have learned to be able to demonstrate to prospective employers, and our professors, that we are capable of being engineers. On the hardware side of things, we expect to apply what we have learned about Kirchhoff's Law to calculate the current in and out of all the components to make sure that nothing is being overloaded, or if something is not receiving enough current.

Additionally, we also plan to calculate power consumption, as that will be very important to our project specifically since there are many components that will be drawing power. We also want to implement what we have learned in embedded systems such as different lines of communication, writing code, and enabling different pins of the device. Other

software components will be implemented as well like creating an algorithm and making a graphical user interface for the display that we are implementing.

We as students have been given all the foundational tools, we need to complete this project, however, as bourgeoning engineers we will need to become more familiar with new methodologies, practices, and technologies to be able to specialize in all the different areas involved to create a final working product. Our team is very competent, and through applying the knowledge we have gained throughout our academic careers, we are confident will perform well when necessary to deliver a final working product, through the utilization of all the Engineering Fundamentals.

## 7.3 Preliminary Testing

We will start to develop parts of our project by conducting preliminary tests. This will give us a solid foundation to not only start developing subsystems, but this will also allow us to begin more in-depth research on how pieces will integrate into the whole system, and with one another. Preliminary testing essentially will be composed of one "generalized" step, getting a response for each component as it pertains to our project. For example, we will be implementing buttons on our project, so whatever button we end up deciding to use will be connected to our development board through a breadboard, and we will simply just try to get a response from pressing the button.

An example of something we have already performed would be us turning a prototype servo motor. This was successful as it taught us how to manipulate the speed and rotation parameters of the motor. This process has been incredibly insightful as this will be a crucial step when our finalized design becomes entirely autonomous. The purpose of this Preliminary Testing is to bring the components to their basic operational capacities, so that the group can gain an in-depth understanding of each component that will be needed, and/or utilized, to deliver a finalized working product.

## 7.4 Subsystem Testing

Subsystem testing will also be a crucial next step to our development process. This process will consist of trying to get two or three different related components to interact with one another. This will be based off of responses from those different components that have been part of the Preliminary Testing. An example of this Subsystem Testing would be using the buttons to scroll through the graphical user interface (GUI) we will have on our screen. On a higher level, this would demonstrate to us that the buttons are able to be integrated with the display, the GUI works, the software detailing the menus works, and that the processor/controller is able to execute the necessary code to realize the function we are testing, scrolling through a menu using the buttons as a User Interface.

A step further would be to utilize said buttons to then select an option on the menu being shown on the display, then be able to visually see the correct output for whatever the option chosen was. Subsystem testing will be similar to putting a complex jigsaw puzzle together. This process will assist the group to see the overall, broad-spectrum/picture of the whole project. The successes of the Subsystem Testing will be a crucial milestone in our implementation process, and successes in this will allow us to move our project into the overall testing phase.

## 7.5 Overall Testing

Once we have successfully determined that the different components involved are interacting with one another in the correct manner, we will then go into what our team will refer to as overall testing. This process will be when the prototyping process will start coming to fruition. By this point we would hope that we have gotten most, if not all of the necessary components to communicate, relay the necessary/correct information between one another efficiently, effectively, and as error-free as possible. If this is the case, this would demonstrate that we are now in a place to begin the implementation of all the features and functions we have outlined in the Requirements Specifications section that we have determined our project include. An example of this sort of testing would be selecting an option on the interface, plucking the string we want to have tuned, the sensor picking up the vibrations, the algorithm running and relaying the information necessary to the motor controller to then have the motor turn to try and tune the guitar string, and having this process repeating until the string is completely in the correct tuning.

Overall testing will be the process that will consume the most amount of time to complete. Once we have determined that the project is comfortably at this point in our development process, we will most likely begin the ordering process of the necessary PCB's. The reason for this is because if we get the device working on a breadboard prototype, we do not want to waste any time, especially due to the logistic issues that are still plaguing the technology-based creator space due to shortages and/or production issues world-wide. We are aware that the ordering of components will be tricky both this semester, as well as the coming semester, so we will need to start perfecting our project as early in the semester as possible. This will result in testing being an essential step for creating any kind of product, and our Senior Design project is no exception. We believe that being proactive in these steps will help us tremendously in our endeavor and make our lives easier, and ideally lead to the successful delivery of our final project.

## 8.0 House of Quality Diagram

From our house of quality diagram, we see that most of the client requirements have a positive correlation to our technical requirements. With most of our requirements being related to time. Time is a valuable aspect with our product as our main goal is to tune instruments automatically and efficiently. Since this is a valuable aspect, our requirements were built around and positively correlate with it.

This is seen in the correlation matrix at the top of our diagram. Our competition is the Roadie 3 automatic guitar tuner and performs quite well with the customer requirements show in our diagram. However, the cost is where the Roadie 3 does not perform well as

it is quite expensive. We will try to outperform the competition in this customer requirement to put our product ahead.

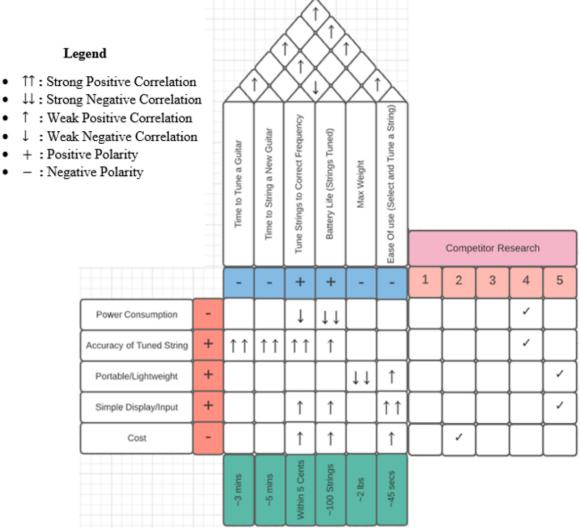


Figure 1, House of Quality Diagram

## 9.0 Competition

Initially, to begin analyzing the competition one must take a look at specifically vibrational sensor based chromatic/strobe tuners to fully be able to understand how the necessity for an automatic guitar tuner came about. As a result one of the most popular, and accurate, tuners on the market that utilize vibration sensing technology is the Snark ST-8 Super Tight Clip On Tuner. This chromatic tuner is a simple device with a LCD screen that informs the user whether the current string being plucked is sharp or flat, based on the chromatic tuning system that it employs.

The way the Snark ST-8 operates is that it has a plastic clip, that has a silicone/rubber padding that allow the vibration waves to traverse from the point of origin on the headstock, through the clip and the attached stem, and into the main housing of the ST-8 device. Once the waves reach the housing, there is a piezoelectric disc within the housing that would reverberate indicating that here is some sort of vibration happening at a certain frequency that then is relayed onto the user based on what the tuning is desired. The ST-8 is a very popular tuner because it is capable of being used while in loud environments, however the tuning itself is still manual. Based on all this, our group decided that using this device as a 'base-point' to begin our research was a solid foundation.

A device like this already exists in market, the Roadie3 designed and sold by Band Industries, Inc. This product by Band Industries has been in market since about 2017 and has gone through 3 iterations, and they have a specific device for bass guitars. One of the limitations that this device has is that there is no additional input to verify the accuracy of the string tuning. To bypass this issue, our project will be implemented so that the accuracy is within a  $\pm$  of 5 cents. Additionally, the choice of motor will be one that allows us to make fine adjustments of the tuning peg to be able to obtain that desired accuracy. We also want to find a way to combine their two products into one.

Our project is going to attempt to find a motor that can turn a bass guitar peg, which will allow for our tuner to tune both instruments. We also wanted to implement an extra jack that will allow an artist to tune very accurately to the pickups that are already placed on the guitar, by the company that made the guitar. Another potential competitive edge we can gain is by adding an option to tune a new string quickly.

The Roadie3 does not have an option for tuning a new string from start to finish, however it does have a manual driver, that turns the peg whenever a button is pushed by the user. We want to implement a software setting that allows the user to select an option that tunes a string from having zero tension to the correct tension and frequency. Finally, one last small software improvement would be to add a requirement for tuning accuracy when the string has too high of a frequency.

When tuning a guitar, if the string has too sharp of a pitch, the person will tune below the frequency, then back up, to ensure that the string is under tension and at the correct frequency. This seems like a small feature; however, all musicians have a standard of tuning the string low if it is high and then back up. The Roadie3 does not have a feature like this, therefore, the guitar goes out of tune more quickly.

Another product that already exists on the market that is similar to the Roadie3, is called the Jowoom T2 Smart Tuner. The way it operates, assumedly so, is similar to that of the Roadie 3 as it utilizes sensors embedded within the device housing to sense the vibrational response from strumming a string to then activate a motor into turning at a variable rate in order to turn the peg winder so as to tune the guitar. The main components are fairly similar between the T2 and the Roadie3. They both analyze the frequency and tune the guitar using a motor based on the frequency response and the difference from what the current pitch of the string is and what the desired pitch is. In both cases the devices have already entered market and are therefore primary competitors, however the main drawbacks of the T2, based on reviews, is that the motor used on the device is not very fast, and is prone to slippage when trying to wind a string fast. Similarly, to the Roadie3, the T2 is unable to tune a Bass Guitar as the motor inside the T2 does not produce sufficient amount of torque to spin the geared tuning peg on the heads of Bass Guitars. With that said, based on reviews, the consistent feature that the T2 does have over the Roadie3 is the cost. With the Roadie3 costing upwards of \$130 per unit, it doesn't make full sense why someone would choose the Roadie3 over the T2 when they basically both have the same feature set and similar limitations.

Our group believes that these features are enough to compete with the Roadie3 and deliver a product that goes above and beyond. The hope is to be able to implement all these changes, but we are confident that we will be able achieve most of these.

## 10.0 Tuning Background

A guitar, as well as majority of all other stringed instruments, have simple operational concepts. Through history, there have been different stringed instruments that have been utilized to make some sort of tonal sound, whether for ritual or entertainment we can't really be sure of. However, the operational concept is that there is a string, some material, usually wood, that provides tension, and a body of said instrument. The methods of playing the instrument would vary from plucking to using another tensioned string, both of which had the goal to create vibrations that would then produce sound, at the appropriate pitch.

Some of the oldest stringed instruments were bowed, and closely resemble what is today a violin, and as a result the basic design for stringed instruments hasn't really changed drastically and can be translated across different instruments. In the design, there is typically a body, a bridge, a neck, a head which can be referred to as the pegbox, and tuning pegs. The idea is that the body neck and head are connected in a linear fashion (see Figure 2 and Figure 3 below for reference). From there the strings that are to be used are fed through the appropriate orientation to be anchored at the bridge, and then they are fed to the tuning peg. The tuning peg, through a series of gears, provides torque that then translates to tension on the string. This change in tension is effectively what changes the pitch/intonation of the string, and by relation the vibrational frequency. As in a violin, a lute, mandolin, or guitar, the operational concept remains the same, however in further discussion, as it pertains to our project, we will be referring to the guitar explicitly.

Like a violin, with a guitar there is a bridge, neck, body, head, and pegs, the difference is the size of the instrument, the shape, and number of strings, but fundamentally the tuning operates the same. The tension for a guitar string varies through each string manufacturer, metal used, coatings, gauge, whether it's meant for electric or acoustic guitars, and a slew of other variables that are yet to be determined for a baseline for our project, however, tension is directly representative of the tuning and vice versa once all other variables have been accounted for, so there are ways to mathematically represent the tunings in relation to their tension, and frequency giving us a way to quickly adjust if necessary for other instruments.

As such, a guitar string tuning process begins once the string is anchored at the bridge and fed through the tuning peg. The peg is then turned and depending on the orientation of the peg and head this turning would either be clockwise or counterclockwise, this turning of the peg is what provides the tension. More tension means that when the string is played the higher the frequency the string vibrates at and thus the higher the pitch, conversely lower tension means lower pitch, and frequency.

For a guitar, the tuning standards have been established for some time, and many people will argue about which frequency to use. In our project, and going forward, when we refer to standard tuning it is to mean the EADGBe tuning, which is based on the pitch standard of A440. Breaking this down, this means that if you play guitar and are trying to tune it, the thickest and lowest string is the E, followed by A, all the way until you get to the thinnest which is the e string, on a traditional, right-handed guitar it would be that the strings go from left to right, from thickest to thinnest.

The A440 standard is referred to as the Stuttgart Pitch, and it is corresponding to the 440Hz frequency for the A note above the middle C in a Piano. This A440 pitch is standardized by the International Organization for Standardization as ISO 16, and as such it is used as a reference frequency to calibrate the equipment and instruments to be used in tuning. EADGBe was chosen as the 'standard' tuning for a guitar, mostly due to playability across keys and scales, making the arrangement of music to be the most pragmatic in this tuning. With that said, since we are operating under the generally accepted standardization of EADGBe tuning, the corresponding frequency values for each of the strings under the correct tuning is characterized by the following table, with accompanying Scientific Musical Notation.

Tuning	Frequency	Units	Scientific Musical Notation
Ε	82	Hz	E2
Α	110	Hz	A2
D	147	Hz	D3
G	196	Hz	G3
В	247	Hz	B3
е	330	Hz	E4

Table 2, Frequencies for a Guitar Standard Tuning

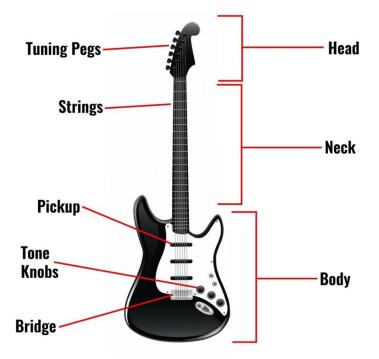


Figure 2, Representation of Physical Components on an Electric Guitar

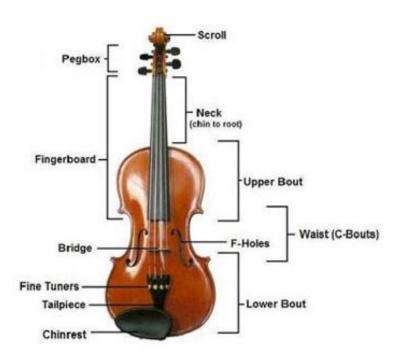


Figure 3, Representation of Physical Components on a Violin

## 11.0 Hardware Block Diagram

The main setup for the hardware diagram consists of the battery tied to an on/off switch to keep the system from running all the time. Next dropping down in voltage to reach the correct voltage level for the processor to the display and the regulator to the motor. The processor will be in charge of taking readings from the vibration sensor and telling the driver what to do which will then control the motor to tighten or loosen the pegs on the instrument. The processor will also be displaying values on the OLED display which will have inputs and buttons that will be read on the processor to change the settings on the display and select on a small screen interface.

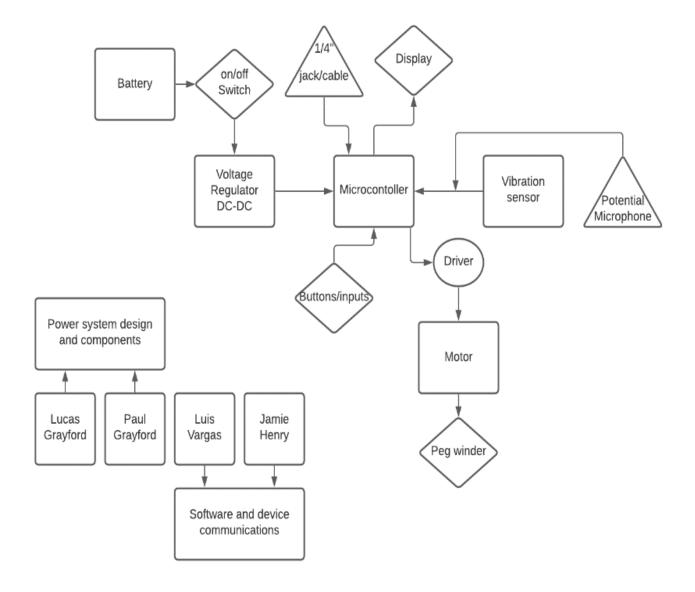


Figure 4, Hardware Block Diagram

## 12.0 Physical Components

## 12.1.1 ¼" Output Jack

One of the electrical components that will be used in our project will be the ¼" output jack that a cable will be plugged into to read the frequency from the pickup of the actual guitar. There are four commonly used output jacks. These being mono, stereo and TRS (tip-ring-sleeve). Each type of jack has its own advantage, however for the sake of the project, we believe that the mono jack and the stereo jack will be the most useful jacks for this project.

The mono jack only has two connections, a live/hot connection, and a ground pin. The live pin picks up the signal produced by the pickups in the acoustic or electric guitar and sends them through to the output on our device. This means that we will be able to read exactly what the guitar is producing, making a more accurate tuning experience. The way our project will implement these will be by connecting the device to our PCB and processing the analog signals into digital signals. This will aid in communicating these digital values to our device.

The stereo jack has an extra ground pin that completes the circuit in the active electronics on the guitar themselves. This could be useful to implement into our project, to complete a circuit for the device to detect the jack immediately, thus bypassing the vibration sensor all together. More research is going to be conducted through testing both jacks, and their usefulness. This component will add hardware complexity to the project.

#### 12.1.2 Selection of Output Jack

Since one of our requirements for this project is accuracy, we do not want to sacrifice on components that will gather data. There are many products that could work well in our project; however, we will be testing the accuracy of two different output jacks. One is a simple stereo jack and the other is a Pure Tone Mono Multi-Contact ¼ inch output jack. The stereo jack has three pins as stated before, and the Pure Tone jack has 5 pins, two positive pins and three ground pins. The Pure Tone jack has already been ordered and the stereo jack will be acquired by going to either a music shop, an electronics store, or by online ordering.

The stereo jack is used in many guitars and bass guitars, and works very well to complete the job that is required of it. The pins create a contact with the cable that is plugged into it and reads an analog signal from the instrument. This analog signal can then be amplified through an amplifier or go into a tuning pedal for the guitarist to fine tune his instrument without the hinderance of any unwanted noise or interference.

One of the common issues with this jack, is over time, the connection pins can become less sensitive and become looser over normal use. This can cause unwanted crackling or interference, which is the sign of a poor electrical connection. We want to deliver a quality product that can be reliable for a long time after it is purchased. This degradation over time will be accounted for in our project.

The Pure Tone output jack has two live connection pins and two ground connection pins that connect to the cable coming from the guitar. It also has an extra ground pin to complete the connection in the circuit it plugs into. The advantage of having these two extra pins is reliability, accuracy and longevity of the product. This jack will be put to the test against the stereo jack to see that if the accuracy and reliability gained from this product will offset the cost of a normal stereo jack.

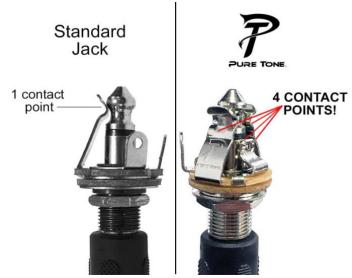


Figure 5, Comparison of Pure Tone output jack to a standard stereo output jack

## 12.1.3 Testing Process

The plan for testing these jacks is laid out in a few simple steps:

- 1. Tune a guitar with a device that is already known to be accurate and reliable. (Guitar must have an output jack already.)
- 2. Connect an oscilloscope probe to each jack, and ensure the connections are sturdy
- 3. Use a ¼ inch cable to connect the output jack from the guitar, to the output jack that is being tested. (Ensure all connections made are still solid and on the correct pins.)
- 4. Pluck the desired guitar string and watch the oscilloscope measure the frequency. This process will be repeated thoroughly to ensure accurate readings.
- 5. The frequency that is clearest and closest to the frequency attained when the guitar was tuned originally, will determine which output jack will be used in our final project.

The team's prediction is that the Pure Tone output jack will read a signal that has less noise and is more accurate to what the guitar is producing. This is due to the extra pins, and the quality of product.

## 12.1.4 Preliminary Testing Results

At the time of writing this document, the preliminary testing of the Pure Tone output jack has been limited to being able to detect a signal altogether. No particular testing has been conducted as to which jack is better or worse for our purposes

### 12.1.5 Implementation

The implementation of whichever jack is chosen will be the same. The output jack will most likely be mounted firmly with hardware, on an accessible location on the final device. The pins on the inside will be connected to the PCB most likely through wires that are soldered onto the output jack, and connecting to pins on the circuit board. These connections will also be connected to an analog to digital converter (ADC) to do the obvious and convert an analog signal to a digital signal that will go straight into the processor.

If the user decides to use this form of input, then the piezoelectric sensor readings will be bypassed. This comes from the expectation that the jack will be a more exact reading than the sensor, and we do not want to confuse the processor, on which data to read. The idea for this bypass will be implemented in the hardware. The extra ground pin on the jack that completes the circuit, will completely bypass and cut off the sensor signal so as to only have the output jack being read. If designing this circuit becomes too complex, and nothing seems to be working, our backup will be implementing a software bypass somehow. However, this should not be too complicated, and we are hopeful that we will be able to implement this hardware design.

## 12.2 Motor

For the overall motor there are multiple options to use. The main two options are between using a stepper motor or a servo motor. The system could end up using either one, more research and testing is required to see which one will exactly be the best to use. The whole plan varies how we want to apply the motor in the end. With the battery being a DC power source there is a preference to try and attain a DC type motor and not have to deal with a larger power drawing AC motor. The stepper motor is the current option that is being considered more since they are accurate, precise, high torque, efficient, and low speed. It is an open loop system, but it can be made a closed loop system if it needs to be. The vibration sensor is going to be telling the processor the values which then the processor will tell the driver which will tell them motor which way it needs to turn and by how many steps it will be. Stepper motors are relatively cheap and have a longer life span than most servo motors. Servo motors typically have a good to average torque yield and usually have a better torque yield at high rpm from the 1000+ rpm range. For this case on restringing a guitar it is a little excessive to go past 500 rpm. Most stepper motors start losing most of their torque past the 500-1000 rpm marker, which again there is no need to go past that point. Also, if choosing a stepper motor the choice of phase would be additional factor to consider whether to use a 2-phase or a 5-phase stepper motor. The best option between those two would be using a 5-phase if one can be found that fits in the budget. 5-phase would provide more torque, less noise, and more accuracy by lowering the rotation for each step it takes. Servo motors would just waste more power not only that the servo motors usually cost around double what stepper motors costs, but servo motors life span is about half as much as a stepper motor.

If there is no correctional feedback, and the stepper motor can give enough torque while maintaining accuracy that is the current method of choice. Most stepper motors can have a relatively fast rpm rate around 1000 rpm which would allow for extremely fast restring speeds. The Roadie 3 does 110 rpm where ours could be almost 10 times faster than the leading brand of the Roadie. Comparisons will be tested between both motors to determine which one will be the best use. Roadie does not state the motor type that they used for their design, so once a Roadie 3 has been attained and dismantled to see the kind of motor that is used. Once that is done the calculations for the torque and be found and used to help determine the motor and if the continued use for the stepper motor will be used.

#### 12.2.1 Motor Testing

There are varying motors to choose from and there has been no final decision on which motor type that will be used in the final system. One of the main motors that have been used for current testing is a 5V Stepper motor 28BYJ-48. It is a relatively small stepper motor that works with the current software that is being used and developed in the project. The first test was to see if the software was even compliant with the motor's controls. We were able to get the code to function with the vibration sensor plate and at least turn when a vibration was picked up and it was successful in turning the motor head. The only issue is to break down the calculations of the actual vibration that is being received from the sensor and processed by the processor and calculating whether the motor needs to turn left or right and by how much. It sounds simpler than what it is made out to be. There is going to be changes made in the software to gauge the proper amount to turn the tuning pegs for the instrument chosen. There are other methods that some musicians use to tune their instruments by tuning it to the correct frequency then tuning up and back down a hair to tension the string better. Which this method is an additional preset to add when getting the final reading from the sensor after the string is plucked and reads the correct relative frequency for the string.



Figure 6, 5V Stepper Motor (Model: 28BYJ-48)

This motor is more for experiment testing than being the actual motor that is going to be used on the final design. This motor is meant more for learning purposes rather than much useability purposes. It is a uni-polar stepper motor and does 32 step with a 1/64 gear reduction giving it 2052 steps per revolution which is more than what is really needed. The motor also falls very short with its 6rpm which is a tenth of the speed of the Roadie. It does not have a high enough torque rating for what is needed to turn a tuning knob from what has been researched for what is needed to turn a knob is around .2 Nm of force, this motor only produces about .015 Nm which is not practical and is less than a tenth of what is actually needed. Again, it is a test motor, which another result was found that these motors are relatively easy to break.

The motor head cannot withstand a good amount of force applied to the peg head before it has some kind of internal break causing it to no longer work. Its plausible breaking point was from trying to apply force to the peg head of the motor trying to put the tuner head piece on the end of the motor to conduct further testing. After the tuner head was attached to the motor there was a test to see if the motor could even turn a guitar peg, but before that could happen the motor would not turn at all. There was either a failure in the connection lines and hooking up the testing setup or a failure in the motor. It turned out to be a failure in the motor since the software would run and the motor would make noise, so it was trying to turn but most likely one of the gears got stripped when putting the tuner head on with a good amount of force. This only caused a slight delay of needing to get more test motors since they are ample in supply.

#### 12.2.2 Motor Research

There was also vested money and research in a Nema 17 Bi-polar stepper motor which we have not put to test for two main reason it is heavy and does not meet the handheld friendly requirement since no one wants to stick a almost 1 lb. block in their pocket and with all the other components that need to fit in the housing it would not make it practical for a handheld device, also the driver requires at least 10-28 VDC for the driver even though the actual stepper motor is rated for 2.9 V it would take a power supply to test.

The motor exceeds in the torque rating that is needed where this motor was rated .46 Nm which was a bit excessive but would allow for the stretch goals tuning. Looking at the competitors Roadie 3 we are uncertain which type of motor they decided to use for their system until a Roadie 3 is attained, tested, and dismantled to see how they went about picking components for the build. Most of the motors that are supplied are either too much or too little and there is no nice in between. The thought is that the Roadie uses a planetary styles gearbox motor that would fit the way it is styled in the housing since they are typically longer and thinner type motor and give a decent amount of torque behind them to turn most knob pegs but a bass guitar's tuning knob.



Figure 7, Brushless DC Motor with Encoder 12V 159rpm

The motor chosen was another Nema 16 stepper motor which was a step down we went for more of a exact rating motor for torque, where this motor has .21 Nm of torque, and has a lower current draw of only .4 A compared to the Nema 17 that was rated for 2 A. It also weights about half as much as the other motor. The only problem with the motor is that it is rated for 12 V which is a little higher than what was wanted so varying on the power supply that is going to be used for the system there will be a high probability for a step-up voltage to supply power to the motor to run it at max efficiency. The only part for the motor that may fall short is the possible rpm since the data sheet does not state it, which will mainly affect the restringing feature of the guitar since the actual tuning will be smaller turns so the rpm is not a large focus for the tuner than the actual degrees are for turning the motor.

After further consideration for a finalized motor we have decided to go with a brushless DC that functions at 12V that can function up to 159 rpm. We decided to go with this motor for multiple reasons. The Jowoom used a very similar motor and we were unable to find a motor that met the qualifications that their motor was. This motor comes with a encoder so there is no extra need for a on board driver which helps save room and added costs on to the final design for the tuner. The motor is slightly smaller than the Jowoom and is only about 20 rpms less than the competition of the Jowoom, but the main competition is going to be more of the Roadie 3 than the Jowoom. The Roadie 3 motor is 110 rpm so ours will still be overall faster at restringing the instrument and tuning if the code is

optimized to its fullest. The motor also reaches the proper torque that is needed to turn the tuning pegs. It has a reduction ratio of 45:1, when we were thinking that we needed to be super accurate with the tuning we were a little wrong when thinking about the amount that the motor actually needs to turn. When we used the Jowoom to tune a standard electric guitar with the Jowoom and it did a good job for a quick tune, but its interface is lacking, but besides that point their motor was good enough in accuracy. The holding torque is .231 Nm which falls into the range that is needed. The motor is compatible with the Arduino software that is going to be used. The motor is a 5 pin motor for wire 1:PWM, 2:Power-, 3:direction, 4:FG, 5:Power+.

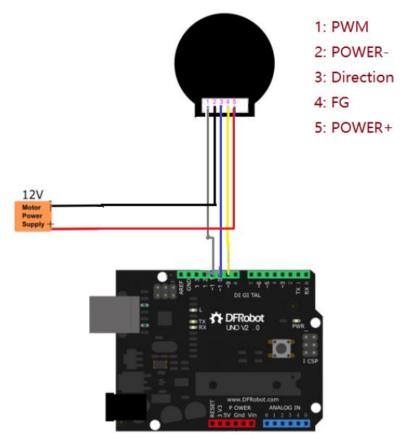


Figure 8, Line Connections for Arduino (will vary from ESP8266 connections slightly)

The supplier for the motor is Digikey for \$19.90 with 20 in stock. It is rated for 12 volts and does 159 rpm, it has a stall current of .7 amps meaning no matter how much torque the motor is fighting that the current will not exceed. Technically the motor has a base rpm of 7100-7300 rpm internally then has a gear reduction ratio of 45:1 dropping it down to the 159 rpm, where it sacrifices speed for torque, allowing this small motor to produce the torque that is needed. There is no given value for what the regular amperage will run at but estimations are about half of that, but will be found once testing with the appropriate motor is done.

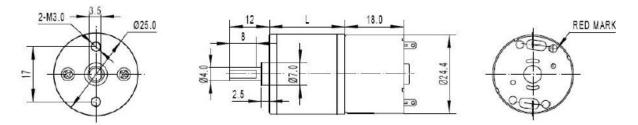


Figure 9, 12V DC Motor Dimensions in mm

#### 12.2.3 Motor Conclusion

The overall motor is a key part for this device to work and since stepper motors are relatively accurate and can have a relatively high holding torque it should be good enough for the design even aside from its blocky size, but in our case the later change to a even lighter weight motor is a better method while keeping the same torque although it is no longer a stepper motor. There are a lot of motors to choose from but whether they would be the right fit for the system is questionable since there is already a fair amount of head way that was made on the software side for programming the test motor to work and being a long the lines of a stepper motor even thought the testing has been done with a uni-polar stepper motor, so small changes will be needed to compensate for the change in the end system. The most difficult part was trying to find a motor that would meet all system requirements without copying the competitors motor even though the motor that they used is unknown and maybe more simplified, also the torque rating is unknown that they used.

#### 12.3 Driver/Pulse Width Modulator

Along with using the stepper motor, a stepper motor driver will be required so the pulse width modulations that are sent to the driver can tell the motor how many turns will be needed. There may be a need for a pulse generator to send a signal to the driver to then tell the motor what it needs to do. It is still to be determined if using that extra step is better than having a driver with a built-in controller to store the data, it would save an extra step and save on housing space for the overall device. Correct drivers will have to correspond with the proper phase motor since a 2-phase motor might not work with a 5-phase driver and vice versa. If a stepper motor is used it will also make it easier to have preset restringing options for the tuner rather than having a manual wind-up. There are also other integrated drivers that would be heavily considered.

Using an integrated driver would help save a lot of space compared to using most block drivers that most of the time are used for controlling multiple motors, and would take up the space of someone's hand, which would ruin the whole design of being handheld in one hand. Since only one motor is being used for the tuner, the integrated driver would only focus on that singular stepper motor. The integrated driver is substantially smaller than most drivers, they are small and fit on the back side of the motor which makes it

convenient for saving on the housing space overall. A more accurate driver can be accounted for once the proper motor is selected for use.

#### 12.3.1 Driver/Pulse Width Modulator Testing

Most of the current testing that has been done for the driver is the ULN2003 driver board although it has mainly been used for the software testing purposes with the current 28BYJ-48 5 V stepper motor this driver is only compatible with uni-polar stepper motors. When the actual swap is made to the bipolar stepper motor the driver will no longer be useful for testing purposes and the SN754410NE will be used for testing the Nema 16 bipolar stepper motor when it arrives.



Figure 10, UL2003 Driver Board (left), L298N Motor Driver Control Board (right)

This board has only been used in testing purposes for the software and is not in the final components of the tuner. So far, the driver has be compatible with the ESP8266 processor that the main programming is being implemented with. When testing for the bipolar stepper motor the L298N motor driver control board supplied by Amazon for \$10 for a pack of 4 is going to be used for the testing of the Nema 16 motor, but it will not be implemented in the final design unless there is a issue in the supply demand for the proper driver needed to run the through Arduino.

Due to changing the motor to a even smaller motor that uses and encoder. A driver is still able to be used for the motor, but with the simpler motor that is going to be used in the final design. After current testing the driver will not be used in the final design, The previous driver that was going to be used was said to be a wrong choice for the final design and has been removed from the final system design.

#### 12.3.2 Driver/Pulse Width Modulator Conclusion/Encoder

There is no need for a pulse width modulator since the servo motor has been a throw away option, but the driver is necessary for the motor to function the way we want it to for the tuner. There were encoder brushless motors but they are harder to control and use pulse width modulation, rather than for the stepper motor and driver can accurately be told how much to turn and knowing how much it will actually turn. It makes life a little easier for being able to tell the driver to tell the motor how many steps need to be done for a quick restring so it can already be close to being tuned and would only need smaller fine tuning afterwards. There are ways to run the motor without the driver but there would need to be more testing with the new motor with the encoder. Usually there are usually four types of encoders being a optical, mechanical, electromagnetic, magnetic encoder type. The Jowoom uses a magnetic encoder due to the magnet that juts out on the back of the whole motor encoder section. All that is known for the encoder that it is incremental motor type, but between the different types of methods that it uses to read was not stated in the data sheet between the four different types and it is just known that it is not a magnetic type at least. The only thing that is known is that it uses pulse width modulation to control the speed and rotation of the motor, if the encoder is completely taken apart to determine what type it exactly is it will be stated later otherwise there is no risk wanted in breaking the current motor just the find the exact type.

### 12.4 Peg Winder

The peg winder will be the head attachment at the end of the tuner that will grab the peg heads to be tightened or loosened. It may be a simple piece, but it needs to be able to function with enough strength that it won't break after a couple of windings. The thought is to design it out of a strong thick plastic that will allow the vibration sensor to make proper readings through the material of choice. There will be two potential design heads that will be tested, one of hard plastic and another made of metal that will need to be coated with clear epoxy so not to scratch the actual pegs of the instruments being tuned.

There are additional thoughts on adding an interchangeable peg winder head for the tip of the motor since the pegs on a bass guitar are much larger than average guitars. If the winder head is too small, it might break or damage the motor since it would not allow the proper torque to be applied towards the tuning pegs of the guitar. There could also be a possibly to make a peg winder head that would be ergonomic and usable for both plain guitars and bass guitars. This will only follow though if the stretched goals are able to be achieved where the motor can give enough torque for the bass guitar peg heads.

## 12.4.1 Peg Winder Testing

For the peg winder there were a variety of peg winding heads to choose from. The competitor chose to use a 4 prong styled head piece for their tuner and it being the third iterations there are not many more improvements that they could make to the peg head design to make it more robust. Their peg head seems to be either made of aluminum or a dense plastic and is rather low profile. Being in a lower budget range and with the friendly use of 3D printers it saves a bit of time and money to 3D print a peg head for the for the tuner. There was a file that was made public and required small modification to the back side of the tuner piece to make a proper keyhole for it to fit on the end of the motor.



Figure 11, Universal Peg Winder Head

The dimensions for the peg winder heads outer shape is 25mm in diameter and 42mm in height, the internal peg notch perpendicular to crevasse is 21mm long by 6mm wide by 7mm deep. The whole notch is crevasse is also 21mm deep and tiers down in 3 widths all the way down from 6mm to 4.5mm to 2mm. The larger middle notch in line with the crevasse is 17mm long by 10mm wide by 8mm deep and The current peg head for the design is a universal tuning head since the aim is to try and get a wider variety of stringed instruments. It has a longer peg head than the Roadie 3 but it has deeper notches to make up for all the varying tuning knob types there are on varying stringed instruments. It is also not a four-prong design and is a split 2 prong head which allows it to run deeper. There is a thought to modify it to be four prongs, but there is a risk of the prongs braking since the shaft is relatively long the tuner knobs would possibly break due to the torque at the tip of the peg head. Even if the peg head for the tuner was 100% infill plastic it would still possibly break. If the peg head was made out of metal, then it would be more possible to make that adjustment. There are more modifications that need to be made to the file since the current modifications are made for testing the 5 V motor. Once the bipolar Nema 16 is ready for testing the motor shaft might be too long for the peg head and will need an extension made in the file. Also, the keyhole for the back will need to be changed to match the shaft.

For the final form of the peg winder is going to be edited to have a 15mm long screw to thread in the lower side of the peg winder and come into contact with the flat side of the motor time so it is well secure to the tuner. There might be an issue making the hole large enough in the Freecad software and making the STL and porting the final version as a STL file to Cura. Varying at what layer height and how big of a flat end screw that is used it should still make a tight fit, this will help keep the universal tuning peg on the end of the motor tip without the need of gluing the piece to stay in place. It needs to have a solid enough contact so that the vibrations can be picked up better by the tuning device. The back peg winder keyhole needs to be changed to allow a 4mm diameter, but the round head of the motor tip is cut and flattened out a 3mm and it needs to be relatively accurate because if the motor head is slightly off it wont feel smooth for fast windings when restringing a guitar or any musical instrument for that matter.

### 12.5 Filament and Cura

Most of the part making for housing and the peg winder is being crafted using a 3D printer from one of the team members. The filament being used is supplied by Amazon and is around \$20 from when last purchased. It is 1.75mm grey PLA+ filament, we are using PLA+ because it holds better than regular PLA and ABS, ABS filament was not chosen to be used for two main reasons and the filament has a tendency to warp and bend due to changing temperatures and humidity in the air, where being in Florida there is a lot of humidity in the air which would cause problems for clean and level prints. The second reason ABS is not being used is because it gives off toxic fumes which are not healthy for humans to be inhaling. An additional note is that most printers do not like swapping between the two different filaments and the nozzles have to be changed more frequent if that is the case. Only perks of ABS is a lower print temperature, but the after product in the end is still usually not as strong as PLA or PLA+ is.

PLA+ melts at varying temperatures if not being heated at the proper temperature could cause the filament to not feed at a proper rate and the stepper motor of the printer will start skipping which is bad. Heat the filament too high and it will no longer melt and go straight to burning. The melting point for the filament is anywhere from 180 - 230 °C, but for most printing the housing and the peg winder are going to be printed at 218 °C with a layer height being .2mm which gives a better layer adhesion which should help with the vibrations carried through the housing to be a little better than other layer height options. PLA+ is strong and durable enough for containing all the components in a compact fashion. PLA+ is mostly made out of recycled corn starch so it does not burn any toxic fumes and smells sweet than burning plastic.

When using Cura it is the main software that is going to allow the file that is going to be made in FreeCad and put in a STL file. Cura runs taking STL and other 3D file types and makes a pathing for the 3D printer to follow by making a gcode file time where the printer is able to understand what is meant to be made and make a real-life version of the 3D model designed. For the settings made in Cura for the prints the infill will be 100% meaning it will be a solid plastic fill for the best rigidity structure and best way for the vibrations to be picked up by the sensors. Setting the printer to do 100% infill also allows some other parameters to be ignored like wall thickness and wall count since it will just be a solid piece of plastic, other fields that are ignored are the infill pattern because the printer is at max infill percentage it will only follow one specific pattern doing each print layer's print lines 90° from each other so it maximizes the layer adhesion.

For the bed of the printer, it will be heated to the temperature of 55 °C. However, the print bed usually can almost be skipped because it can still allow prints to stick to the bed even at room temperature or a little warm, varies on how much power you want the printer to be drawing, but for now that will be the temperature of the print bed for the housing and peg winder head. For the print speed it will be 60 mm/s which is a decent speed for running on max infill to keep the layers warm while printing. Each print will be printed on a breakaway raft so it has better contact to the print bed and keeps from prints failing and

snapping off of the print bed. Supports will be used for both prints whether it my need them or not, but the motor end of the shaft will need support since that end will be circular and the peg winder head only needs a small amount of support on the base just for the keyhole on the back. That is mostly all the settings that will be used by Cura for printing with an addition of a light layer of glue put down by a glue stick on the print bed for the initial layer to stick the best. It will be run on a slightly older version of Cura on 4.4.1 version since it is a open source type of slicer and constantly gets added features to it, but with small variations from each software version.

#### 12.6 Battery

The Pick Pocket Tuner will most likely be operated with a battery. Currently, the options that we have are making the project rechargeable battery with USB power charger, or simply using a 9V battery. The exact choice of the battery will come later once all the electrical components are properly accounted for. 9V battery was the original thought for a version where the battery replacement would be quick and easy only downside is determining how long it will be able to power everything before it runs out of power. Currently the main competitor the Roadie 3 is powered by a 500 mAh LiPo rechargeable battery however they did not give a voltage range for their battery but most of the batteries that match that criterion are 3.7 V LiPo. Having a rechargeable battery could be a selling point, due to the sustainability and common place of having a chargeable device. Replacing batteries for devices has been phased out in most common appliances, therefore implementing a rechargeable battery could make our product more marketable and competitive.

The battery choice will be determined by the voltage ratings for all our components. If the components for the device only require a maximum of 5V, then getting a battery as close to that output would be great for dealing with the regulation of the voltage. Another key feature that will be important for the battery will be the current output. We do not want the output to be too low to where our project will not function properly, but also not too high in case anything gets burned up.

## 12.6.1 Battery Theory

The plan for the battery is on the end half to the spectrum for parts needed. Once all main components have been accounted for the battery will be more of a final decision for how much power will be needed to run the system. For now, the thought is sticking with a 3.7 Volt Lithium-ion polymer 1200 mAh battery supplied by Amazon for \$12, where is weighs about 23 grams, it is a larger battery than the competitor of the Roadie 3 but is smaller than the Jowoom, but where the Roadie 3 did not state the what exact voltage that they used but they did use a battery rated at 500 mAh and is a Lithium-ion type battery most of those batteries with those 2 parts going together are rated at 3.7 V. It could be higher but based on the size it is most likely that the battery used by Roadie 3 the theory could change if and when a Roadie 3 is attained and dismantled for further inspection. The battery does not have enough voltage to power mainly the motor and driver since the two

together require a little more than 12 Volts. The overall system is going to need power a OLED screen, processor, driver and motor. There may be further investment in a voltage step up or booster for when running power for the motor and driver. This battery is in the plan to be tested in the system and calculated for all the correct voltage and current measurements are gathered. The reason of using a 3.7 Volt battery is because most of the competitors ended up using that as their voltage amount. It may make it less difficult to step up the voltage. The thought is to do a voltage divider followed by a necessary regulator to give a more exact voltage when going into the processor and OLED screen.

Since the battery is going to be a DC power supply there is going to be a way to recharge the battery after it is depleted. The exact type of recharging method for what cable type has yet to be determined but it will most likely be a USB type charger either type b, c, or mini. The choice will most likely be a usb type c charging port because it is pretty commonly found along most phone charger types so if the charger for the device is ever lost a phone charging cable will make a good substitute for it. The battery pack is a bit larger than what we are planning for, but there is a decent amount of room in the housing that can be accommodated, it will also allow for balancing of weight distribution in the housing to counter the weight of the motor, although it will put a damper on the overall weight of the tuner, but it will be reliable and give it a more solid feel in the user's hand. The dimensions for the battery are 60mm long by 35mm wide by 5mm height with a 100mm lead wire length.



Figure 12, 3.7V Lithium Ion Polymer 1200 mAh Battery

The thought is to use Lithium-ion battery like the competitors, we thought there would be a issue in finding them in a higher voltage but we are deciding to use more regulators to deal with that issue. There was a thought of getting around with a higher voltage at first and thought that is combining two or three of them in series giving either 6.4V - 11.1V however, the method may sound nice but could lead to hazards and is not recommended.

There is a possibility of one of the Lithium-ion battery packs to not charge properly, it would be similar to putting water into two cups, an overflowing cup and an empty cup where the now overflowing cup has to leak water into the empty cup. If that were to happen a battery could be overloaded when charging and potentially explode. It does not offer a balanced way for recharging the batteries to have a proper functioning system. It would ruin the consistent voltage rating for each of the components that is needed for the design. Another battery option is the standard 9V Alkaline battery there are slight plus sides and down sides to the option.

The main upsides to them that they are commonly found in almost any store, but they can be a little costly if they are constantly getting burned through, also most musicians use them for some of their other devices so it would add a slight convenience if they are already on hand. The downside is how long they would last in tuner which would be less than hour if not even 30 minutes if the motor was constantly running. They only have about 500 mAh which is the same as the Roadie 3 battery rating but higher voltage rating than the Roadie 3.

It is not the best choice so we decided to stay away from using that option for now since it would not be as efficient, so rather than being wasteful the decision for a rechargeable battery is the better option and it makes is more user friendly. Power efficiency has not been the main concern for the system, but it is a concern to be focused on when trying not to waste power and drain the battery quicker than what is wanted. The plan is to optimize the system later with tweaking components and parts as we keep moving forward. The main part is getting the closest parts that will comply with the system and allow it to at least run, once getting past that the fine tuning can happen and more accurate parts can be attained after proper testing.

# 12.7 Switch and Buttons

Most of the interacting with the interface will be done through the buttons. There are 2 types of button layouts that are considered. First layout is to have a five button Directional pad layout to make it easy for the user to interact with the interface on the display screen. The basic D pad would cover the options to move around on the selection screen with up, down, left, right, and a center select option. There is the thought of adding two extra side buttons that will be a back button and or a home button varying on how complex the interface is going to be.

The other option is more of a limited option where it would minimize the number of buttons needed to be pressed which would be a either a left, right, and select, or it would be a up, down and select. The button choices will mainly be determined by the interface and how many features are going to be made available for the user. Lastly the switch for the tuner so the device can be turned on and off. There are also thoughts about either adding and additional button or switch for a turbo mode on the device allowing for quick tuning from the device to where it will still be accurate enough for the instrument to sound proper and in tune.

# 12.7.1 Switch and Buttons Options

For the main power option, we are going to rely on using a simple on off rocker switch. There are a few other options that could be considered but rather than having a switch that is tied down to the PCB layout where it is physically on the board. The thought is to run wires to connect and solder them in so the switch can be used in a more practical spot rather than being limited where the PCB layout must be at. It gives a little more freedom when it comes down to the finalized housing of the tuner, where the option to put the switch could go almost anywhere on the outside surface of the housing. The Rocker switch is supplied on Amazon but only in bulk which is okay just incase and switches break they can be replaced easily.

The switches can handle up to 6A / 250V which is not a big worry since we are not going any higher than 12V and 1A in the system. The switch is 21mm in height by 15 mm in diameter and a wire length of 22 cm, which will be cut down to a smaller size when needing to solder it to the PCB board. The switch has a lifetime of 20,000-40,000, which is good enough to last the user a long while since they won't be tuning their instrument every day. The plastic casing and snap in should give the switch a nice snug fit when being mounted to the housing case.



Figure 13, Rocker Switch with Lead Wires

As for the buttons there are planned to be at least 3 buttons for interacting with the interface varying from up, down, and select or a left, right, and select. There are some nice buttons that have color coding to them where green would be made the select or okay option and a button one the left and right. The question of either adding a back button did arise but rather than adding an additional button to either back to the home menu or back in general the thought is to add and additional press and hold on either of the three buttons for more than half a second and it will go back to the home menu.

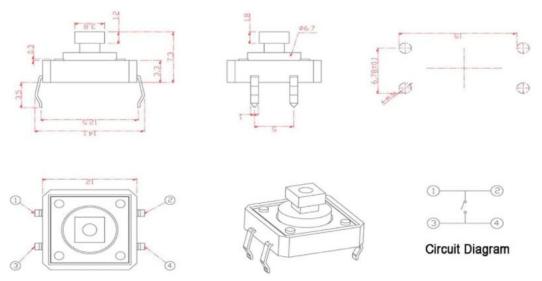


Figure 14, Full Button Layout for Connections

Another option is to make it a array set up where there are tier selection options to where all the main options will be sorted through left or right and then use select where there would be a subsection menu to navigate through. The thought is to have a minimal number of buttons of the device so it is simplistic for the user and not too many buttons to where is starts becoming confusing to use the device. The dimensions for the buttons are 12mm by 12mm by 7.2mm height, but that is without the top caps of the colored buttons on the actual push buttons. These are momentary push buttons for inputs with the interface and are not toggle inputs. They work up to a 12V DC environment which works for our tuner design. The buttons also have a lifetime of around 30,000 pressed before possible failure. The buttons are 4 pin buttons and will be soldered onto the PCB layout. The kit comes with 25 push buttons and 5 varying color caps for the buttons making for a total of 25 push caps too. The buttons are going to be wired to the 3V output from the ESP8266 then out to the three buttons that will have their own lines tied to their corresponding GPIO pins to be read as a input by the processor. Each button will have a  $1k\Omega$  resistor then run off tied to ground. For example, how one of the buttons is wired up using the schematic pin numbers from above in figure 9. The 3V line would go out form the ESP8266 and connect to either pin one or two then on pin three the line would run into the corresponding GPIO pin for that button's action on the interface. Lastly pin four on the button would connect to a  $1k\Omega$  resistor to then ground.



Figure 15, Multicolor Changeable Buttons

# 12.8 Housing

The housing of all the components will be the last part of the process once all the proper parts are attained. The overall quality that needs to be met with the housing is that all the components are concealed away where only the front facing. The whole design is going to be made where it can fit in the comfort of one of the user's hands. There is a consideration to make the design ambidextrous so if the user were to play the guitar lefthanded or righthanded they could still see the display screen properly.

The Roadie 3 has a flaw with this, and it is not friendly for the user to tune a guitar peg head with the right hand since the display screen for their design would be on the underside facing away from the user. There are a few design concepts that were though of on how to fix the issue, but none of them are final since all the parts would need to be able to fit in the housing. As for the housing design a CAD design software will be used to make prototype builds for all the part to fit while keeping an ergonomic and comfortable feeling for the user. The design material is going to be PLA+ and 3D printed to keep costs down for the budget.

# 12.8.1 Housing Theory

The final determination for the housing for all of the components will be the very last part of the project, most components are going to be a jumbled mess for a while testing. Once the PCB layout is created and designed the housing can come after that. It is going to have to be a tight compact design with most of the bulky components being on the outside perimeter, the design might be closer to the Roadie Bass which is bit bigger than the Roadie 3. It has a bulkier design to it, there is an obviously larger motor in it. Since the motor is a squarer shaped design most of the components can be straight stacked behind the stepper motor varying on PCB size and the final size of the battery which did not have labeled dimension. The main concern for the housing is where to place the screen on the outside of the tuner. There are two main options for the screen placement, which are either on the butt end of the device which would be the opposite end from where the peg head is or on the flat side facing away from the palm of the hand. This would be if we went for a more palm sized drill type of tuner.



Figure 16, Jowoom Guitar Tuner

The other style would look more box shaped at the top with a lower grip handle shaped like the Jowoom. Varying on how large the battery would end up being it could be located in the handle grip of the device and all the PCB board components would be located behind the motor since there would be more empty space in the top side than beside the battery in the handle grip area. There is one main issue with most of the designs and that they are not really ambidextrous friendly that allow the user to still view the screen when tuning the guitar. If the screen is on the very back side of the device, it could still be viewable in either hand it would just take a little proper angling from the users side. Since the screen is a nice square shape it would fit nicely on the backside of the motor. There are still some issues with tuning some instruments where some pegs are on the opposite side of the guitar head like most classical guitar heads.

When tuning those types of guitars, it is in the hand of the user at that point whether they want to spin the guitar around and tune it backwards or reach their hand around to the other side and lose visibility of the screen. Since there is a high chance that the user will lose visibility of the screen in this way, there is a thought to either add a audio beep or vibrations that will notify the user to go to the next peg or whether the tuning is complete. There are a couple ideas on how to model it to be comfortable in the hand and provide functionality for the user. The design of the housing will be done in FreeCad which if a pretty user-friendly free software. The material used will be standard grey PLA + 1kg spool supplied from Amazon. When using the material on hand varying on the walls thickness the final design will use 100% infill for when printing the housing so we can maximize on the vibrations carrying through the unit to be read off of the peg winder head that is in contact with the instrument. The main housing design is either going to be a split in half case design like the Jowoom but in a different shape or to do a lid shape design that will allow all the components to be easily accessed the lid would be held down by four 15mm by 2mm screws. The motor will follow a similar front facing screw mounting like the Jowoom

#### 12.9 Buzzer

As an added in thought the has been a question of how the user will know when the tuner is done tuning the peg of the instrument. There is a decision to add in a buzzer to the system as an extra notification feature for the user. The main reason this arose was because of a housing issue where if the user was tuning their instrument and have the tuner in a position where they are unable to see the screen and know whether to go on to the next peg or not. Most people would not notice a small detail be there as an extra aid, but it would be beneficial for the user in the end than getting frustrated not knowing whether the tuning is done, and the device needs to be moved to the next peg. The main feature of the buzzer is a simple notification to the user where once the vibration sensor meets the proper tuned note and the motor no longer needs to make a turn, the buzzer will give off a beep to let the user that the tuning is done for that peg and to move on to the next peg. There is also the option to have a different beep for the final beep to let the user know they are fully done with their tune.

#### 12.9.1 Buzzer Testing

The buzzer does not require an alternating current signal and just needs a 3V - 5V to allow it to give off a 2 kHz beep. Another good point about the buzzer it does not need a control signal sent to it just a voltage input to give off sound which is completely fine for the system. The only downside to the buzzer it does not give off any other frequency besides the 2 kHz frequency, which still works for our system. For when tuning is done for one peg and needs to go to the next peg the buzzer can give off a simple quarter second long beep to let the user know. When the tuning is fully done for the instrument, we can have the buzzer give off 2 beeps so do quarter long beep and wait another quarter second and beep again for another quarter second duration or it could a whole one second beep. The specs for the buzzer's dimensions are 12mm in diameter and 9.7mm in height. For the pins they are 6mm long wires separated by a distance of 7.6mm. Supplied by Amazon and salvaged from the Piezo sensor, also available for individual ordering.

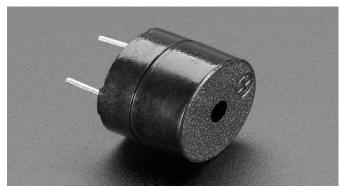


Figure 17, HYDZ 3-5V Buzzer

#### 12.10 Vibration Sensor

The vibration sensor will be the pseudo-heart of the project, since this is the piece that will enable the tuner to function in just about all environments (i.e., loud, quiet, on stage, etc.). The sensor to use is still under determination, due to testing and parts acquisition. As it stands the vibration sensor is due to operate by taking the vibrational input from the guitar, through the wood, and through the guitar tuning peg, and interface with the processor to determine what frequency the string is reverberating at. Once that frequency is determined the processor does the rest and 'tells' the motor to be used to turn to tune. The choice of the vibration sensor has been hampered through determining what kind to use, MEMS, Piezoelectric, etc. Through research and direct comparison with other products already in market that accomplish a vibration-based tuning approach, it was determined that the most cost-effective sensor to go with seemed to be a piezoelectric device (PES for short).

The operational concept of this device, and size/shape of a PES determined that due to cost and ease of integration that it would give a device that is very sensitive and relatively accurate to be able to accomplish what our project is set out to do. Since the PES can effectively 'generate' the voltage due to the vibration being sensed through the guitar strumming, we then should be able to use those voltage peaks to determine the frequency at which the string is vibrating at, and thus relay through the processor to turn the stepper motor accordingly.

One aspect of the vibration sensor that might often get overlooked is that the choosing of a PES sensor makes sense due to its innate resistance to electromagnetic radiation, and electric fields. Take for example an end-user utilizing the product in a live performance setting. In such a setting there are typically multiple electric devices around, and with a guitar you also have magnets, high currents and other electromagnetic field generating devices, such as amplifiers, effects cabinets/racks, circuit breaker panels, computers, etc., that could interfere with the vibration sensors.

With choosing a PES as our vibration sensor, we would anticipate that the device wouldn't have this issue and would then be an issue to not worry about. As previously mentioned, the integration of the PES sensor is rather simple, and straightforward. The PES device takes two lead, or two contact points, to then be able to be interfaced with. Those two leads, one a 'signal/voltage' lead and the other a ground, would be what we directly interface with to be able to determine the voltage being generated by the vibrational sensations, then use some mathematical formulas to convert those voltages generated to the appropriate frequencies to determine what note to tune the guitar to.

Another reason we have chosen the PES is because most tuners have a device like this in them already. Therefore, we would be using something that is already accurate and used in the market. We also decided against choosing a microphone because of the inaccuracies that can be factored in such as background noise or electromagnetic frequencies. Many phone applications for tuning a guitar use a microphone, and there have been common complaints of this feature not working very well because of people trying to tune in a noisy environment. Since we want to stick to the accuracy of our project, the PES made a lot more sense. Overall, the PES is much more impressive on an electrical standard because of the simple, yet complex way the device performs. Finding the correct PES will be a challenge because there are many options in the market. Further testing will determine which sensor best suits our space, accuracy, and functionality requirements.

# 12.11 Display

Our device will include a small 1.69" rounded display to make the user experience more intuitive and enjoyable. Our screen will be compact since we want the whole project to fit in one hand comfortably. The screen will display instructions, frequency values, waveforms, menu options, and other useful information. The screen will connect to the processor through an SPI configuration. The screen that will be used is a thin-film-transistor liquid-crystal display and has a driver. The display also has an Arduino library which works with our chosen ESP8266 processor as it is an Arduino processor. This will allow us to spend more time on creating an esthetic display that is user friendly and that will complement our software design.

We also thought of making a phone application for this device, however, the decision was made that having a physical display on our device would be a better fit for our project. Making a phone app for our project did not make sense for a few reasons. The goal for the tuner is to be useable by anyone from any age. If we were to force the user to use a smartphone, we would be missing out on anyone who does not own one like young children or adults who do not own one. Also, it will decrease our overall budget because there is no need to buy a license for an application. Having an app available for this device one day might make sense as an additional feature, but not as a necessary tool. Therefore, we will stick with having a streamlined high-quality screen on the device that will make the experience a pleasurable one.

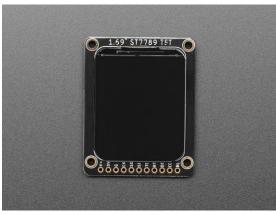


Figure 18, Rounded IPS-TFT LCD Display

# 12.12 Analog to Digital Converter

After some more design efforts, we concluded that we would need to implement an analog to digital converter (ADC). The ADC will be used to translate the analog signal from the guitar and convert them into digital signals, which the algorithm can read. This means that when the frequency reading from the vibration sensor comes in, it will pass through the ADC and be converted to a decimal value. The value that will be read by the processor and read the feedback from the device. The resolution for the ADC has not yet been determined, because we do not know to what degree we can be accurate. This depends on other things as well such as the motor, the vibration sensor, <sup>1</sup>/<sub>4</sub>" output jack, and the other connections in the circuit that are yet to be implemented/considered. We believe that we can be very accurate with a simple 10-bit converter, as the values are divided by 1024 accuracy division. Since the frequency range of a guitar has only 4 significant figures maximum, this should be a sufficient degree of accuracy, while allowing us to maintain the cost low on this specific component. More research will be done on how to implement this device but finding the correct ADC will be crucial to how accurate our product can be.

# 12.12.1 Selection of ADC

After performing some technical investigation, our team has considered ordering and testing a 10-bit ADC from Texas Instruments (Part number: ADS7888SDBVT).

Another option would be to be to use the analog input pin (A0) on the ESP8266 which also includes a 10-bit ADC. This ADC can receive an input voltage of 0-3.3 Volts. This would be perfect to use for the piezo sensor which does not in generate nearly enough voltage for this to be destroy the ADC on the ESP8266 itself. A reason that we would use an external ADC, is because we have not yet tested the output jack and how much current and voltage it will generate. If the voltage is greater than 3.3V, then we will be needing to use an external regulator. This will be tested, and if we do not need an external ADC, this will reduce the cost of our project, and allow our PCB to be smaller.

# 12.12.2 Testing Process

Once the output jack goes under the correct testing procedure, we will be able to see if we need to implement the external ADC. From there, we can move forward with one of two options:

- 1. Using the internal ADC alone:
  - Testing the software, and getting correct digital values to what voltage is actually being produced
  - Find the maximum and minimum digital values that are attained
  - Reach desired results
- 2. Using the internal ADC along with external ADC:
  - Find out how to transmit the digital value to the ESP8266 from the external ADC

- Use the software to extract the data from the ADCs and use them in conjunction to give information
- Find the maximum and minimum digital values that are attained
- Reach Desired results

The testing results will be shown below after proper results and data is recorded.

# 12.12.3 Testing Results

The team has concluded that the ADC on the ESP8266 itself is going to be sufficient for the purposes of our project.

#### 12.12.4 Implementation

This device will be implemented into our project by being placed between the output jack, and the processor. The job of this component will be to take the analog inputs from the sensor/jack and make a digital signal for the processor to use in the calculation algorithms. The data will be translated, and directed to ethe correct r. The Vin terminal will have to positive branches coming from the jack and the sensor, and the negative terminals will be tied to ground.

#### 12.13 Voltage regulators

For the voltage regulation for our system, we are expecting to need inputs of 3.3V, one input of 5V, and one at 12V. The current plan for the regulators is to regulate a voltage from a battery, down to one of those expected levels. However, a linear regulator, will most likely overheat, and cause damage to our PCB. We expect to use a switching regulator to regulate to the correct 5V and 12V. This should not overheat our product and should allow for our project to run efficiently. One thing to consider is how to step down to 3.3V, and this subject still needs to be answered with some research and testing.

The regulator that is already on the NodeMCU-ESP8266, is the AMS1117. Looking into this regulator would be beneficial for our product would be beneficial to the team, because we would be using something that we know could work. There are many different packages that the AMS1117 can come in. One package can produce 3.3V while another can produce 5.0V. This knowledge is super useful, because we would have to probably regulate the battery down to these two voltage levels. An issue with these regulators is that they are linear regulators. The team believes that it will still be useful to test these regulators our to see if we can manage the heat and power dissipation properly. If these regulators work, it will save a lot of time and headache when figuring out how to regulate the voltage correctly throughout the circuit.

If these linear regulators do not work as intended, then we will have to do some research on some buck converters. There are prototyping regulators that electronic distributors sell, which would be helpful for us test with.

# 12.13.1 Prototyping Regulation

To get the design correct for our project, we will need to prototype the voltage regulators to see if our calculations are correct. To do this, we can use the XL6009 buck boost converters. These converters are able to take in 1.25-35V. this is plenty of DC regulation for our project, and should work for what we need it to do. It could be said as well that the regulators would not run at an above average efficiency, due to their wide input and output voltage ranges, however, they should still be efficient enough for our device. This board is larger than we would want for our project, and we would most likely need 2 of these boards to accomplish a complete prototype. This means that we will not be accomplishing our goals of keeping the device as compact as possible. Hence why using these solely to prototype our project is the goal. They would allow our project to function, and would be a good way to test and understand how different voltage levels will be used in the system as a whole. This whole process should help us tremendously in showing how we need to incorporate all of the correct components and regulators we want to have.

#### 12.13.2 Voltage Regulation Strategy

Since our voltage source is going to output 3.7V we need to be strategic about the different regulators we decide to use. The three components that require different voltage levels are the motor (12V), the display (3.3-5V), and the ESP8266 (3.3V). The strategy to satisfy all of these requirements is to design one step down regulator and one step up regulator. Below is a flowchart that shows the progression of all of these regulators.

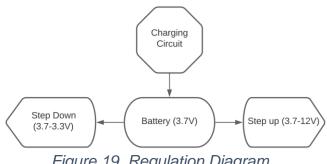


Figure 19, Regulation Diagram

From the diagram above, once can tell that this is the most effective regulation solution to our problem. It allows every component to receive its correct voltage, while allowing for optimal regulation. The display that we are using, has a 3.3V Ultra low-dropout voltage regulator, which means it can take an input of 3.3V and use that to run whatever logic it needs. This is very convenient for use, because it allows us to use the 3.3V output pin from the ESP8266 to power our display, and we would not need an extra voltage regulator to get us to 5V because it is already included on this module. This will not only save us money, it will also save us on power consumption for the circuit, which means our battery life will be extended. Using the least number of regulators possible will be crucial for being able to physically build this product since so many regulators are on backorder.

Also, worth noting is the charging circuit we will be using. The plan so far for the charging circuit is to implement a USB Charging port. The voltage level the battery will be charging at will be slightly higher than the battery voltage, so as to reach the correct charging value. USB charging usually stands at around 5 volts, so building a charging circuit for this should not be too complicated.

# 12.13.3 Buck Converters

The ideal design for our PCB would be to include buck-boost or buck converters. However, the problem our team is having, as well as every other team, is actually being able to order these converters. Voltage regulators especially have insane backlog times (39 weeks or greater). This obviously will not work for us since our project has to be built in about 20 weeks. Most of the regulator designs we would like to use because of their efficiency and size ratings, are out of stock. This does not leave our team with very many options for our design; however, we may have found a solution to the supply chain issue. The next section will discuss the type of voltage regulators we would have used for our project, if it had not been for the global supply chain issues. The design below is a very efficient, compact, and useful designs for what could have been implemented into our project. We also used the TI WEBENCH tool to design each specific regulator. WEBENCH is a very useful tool, and provides ample information for each design. After the very good design option is shown, I will be providing all of the schematics that has the parts in stock so we could actually build our project. They are not the most efficient or impressive designs, but we are hoping that they will work for our project.

# 12.13.4 Voltage Regulator Designs, 3.3V

The example for an improved design compared to the one we will be using in our final project, is shown in the figures below. The specifications of this schematics are shown in the tables right below the figures. This shows a good comparison of what we wanted to use versus what we may have to use for our project.

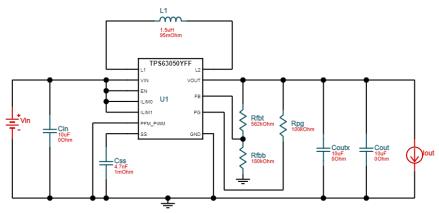


Figure 20, Desired Voltage Regulator Design

Vin	3.0 - 3.7V	
Vout	3.3V	
lout	200mA	
BOM Cost	\$1.09	
BOM Count	9 items	
Power Draw	0.04W	

Table 3, Critical Specifications for Efficient Regulators

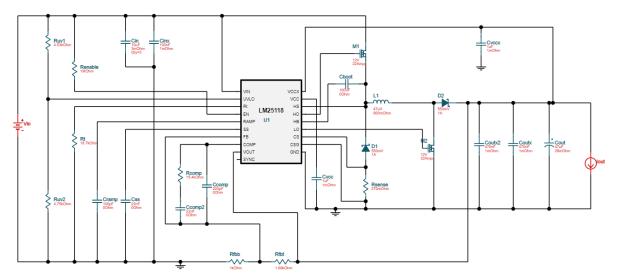


Figure 21, Schematic Design Choice

Vin	3.0 – 4.2V	
Vout	3.3V	
lout	200mA	
BOM Cost	\$5.87	
BOM Count	29 items	
Power Draw 0.28W		

Table 4, Critical Specifications for Chosen Regulator

Unfortunately, these comparisons aren't even close as to the what the better design is. The battery we will be using has a total of 4.4Wh to use, and one of these regulators is already using up 0.21W to run. With one more inefficient regulator, our battery life could suffer. However, this may still be the best way of dealing with the supply chain issues.

Since we do not want to waste space in this document, we will design efficient regulators along with ones we must choose. However, the other efficient schematic will be shown in the appendix for reference, and the regulators that will be chosen will be shown along with all specifications for each circuit.

# 12.13.5 Regulator Schematic and Specifications, 3.7-12V

To design the next regulator, we again used the WEBENCH tool on TI, and put in the parameters we wanted our circuit to have. As expected, we ran into some supply chain issues, and actually ended up using a similar circuit to our last design. Both circuits are actually going to use an LM25118 IC to achieve the correct voltage regulation. This integrated circuit has a very wide input range (3 - 42V). There are regulators out there that have a much smaller range, and a much smaller output range, however, this regulator should serve us well in this project. There was an option of using a different regulator that was also available, however that regulator had an even wider voltage range, which would cause our circuit to be less efficient, and it would take up more of a footprint on our PCB. The output voltage range is 1.23 - 38V, which is way more than our project would need. However, this circuit is very available which means we should be able to receive these ICs for when we need to order our printed circuit board. This was one of the only circuits that would suit us well for this device, and was available at the same time.

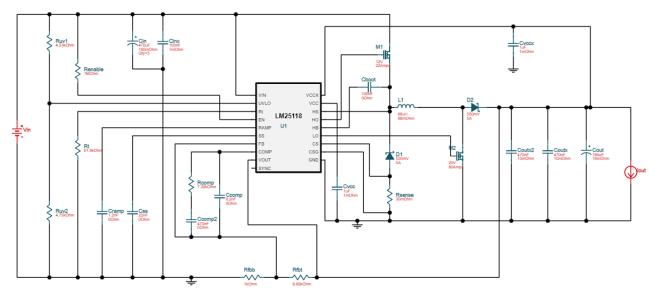


Figure 22, 12V Regulator Design

Vin	3.0 – 4.2V	
Vout	12V	
lout	700mA	
BOM Cost	\$6.87	
BOM Count 28 items		
Power Draw 1.27W		

Table 5, Critical Specifications For 12V Regulator

The circuit above seems like a very complex circuit, just to get us to 12V, however it runs at a good efficiency and should be able to be implemented into our design. The footprint for this circuit will definitely take up some real estate, however we should still be able to consolidate our board to make everything fit on our board in an efficient way.

# 12.13.6 Ordering Process for Regulators

Since voltage regulators are in such high demand, we cannot waste any time in ordering these components. After doing many thorough technological investigations online, there seems to be enough parts for us to order the regulators we need. This does not necessarily mean it will be the case next semester. Therefore, it would only be wise to start ordering these regulators as soon as possible. A great way to achieve this would be to have a completed design of our PCB, so as to simply implement the circuits and get our PCB built all at one time. However, we may not get very many opportunities to improve regulator design, or build another PCB if there is something else wrong with the board itself. Which is why another option is on the table.

Another plan for our design is to order separate miniature PCBs. This means we could order a few regulators of each kind and test them. If they are functioning properly, that means when we order our actual PCB and troubleshoot the problems on the board, we can do it separately from the regulators. This will allow us to be able to solder on the regulators onto the PCB when everything on that board is functioning properly. The implementation process above may be the only way to get all components in on time, and allow us to use our own design rather than using the prototyping regulators in our final product.

# 12.13.7 Testing Process for Regulators

Since we will most likely order the regulators on their separate boards, they should be fairly simple to test. Below are the steps that will be taken, in order to ensure a proper test is conducted on our products.

- 1. Connect the regulator to a breadboard using lead wires.
- 2. Turn on DC power supply and set to 3.0V first.
- 3. Connect the supply to the breadboard
- 4. Connect a load on the other end of the voltage regulator, and connect a multimeter in parallel with the load to measure the voltage travelling across the load.
- 5. After correct voltage is being measured across the load, increase the voltage up to 4.2V to see if the same output is being generated.
- 6. Record data and results.

This test can be conducted for both regulators and should be an effective and safe way for us to test the voltage regulation. If for some reason the regulators do not function as they should, then we will need to go back to the drawing board and start over on our regulation designs. The regulators not working after the first or second time could be detrimental to the project as a whole, because of the supply chain issues could prevent us from improving on our design. However, we are hopeful that the designs we implement will be effective and will work as we intend them to.

#### 12.13.8 Implementation of Voltage Regulators

Implementing the regulators into our design should be straightforward. The regulators will both be connected to the terminals of the battery in parallel. The end of the 3.3V regulator will go straight into the ESP8266 to give it the voltage required to power that design. The 12V regulator will have its input connected to the battery and its output connected to the positive and negative terminals of the motor we will be using. This should provide the correct voltage levels needed for both the MCU and motor to operate at peak performance. The motor however will also have three wires going to the MCU to be controlled by pulse width modulation. The implementation of these regulators again should be fairly simple and should allow all components to operate as they should.

# 12.14 Processor / Controller

The processor we have chosen for this project is the ESP8266 which is a CPU with low power consumption and Wi-Fi capabilities. The processor is 32 bit with a maximum clock speed of 160 MHz which is more than capable of reading our input sensor, powering our motor, and drawing to the display. The processor also has low power consumption is also ideal for our project as one of our technical requirements is to have around 100 strings tuned in respect to battery life. For memory, the processor has 80 KB of RAM and flash storage. With the standard for flash memory being 4 MB. This amount of storage is plenty for our software to run and for our user-saved string frequencies to be stored for faster selection and ease-of-use.

As for communication, the ESP8266 has pins for SPI, UART, and I^2 C. This is ideal as we have choices for which communication method we will implement when interacting with the other devices of the project. These multiple communications could also be used for concurrent communication among multiple connected devices. This is ideal for our technical requirement of timing as we would like to be able to tune all the strings on a guitar in around 3 minutes and around 5 minutes for a newly stringed guitar.

As of now, our group is researching and testing different ways to implement our project in terms of reading the frequency from the plucked guitar string. One implementation that we are researching is having the sensor attached to the bridge communicate with an ESP8266 and have that processor communicate with the handheld device that has another ESP8266 and winds the motor for maximum accuracy. This processor can be ideal for that implementation as they have Wi-Fi capabilities and could communicate with each other. With the sensor on the bridge of the guitar, we can achieve a greater accuracy in terms of reading frequency which would satisfy our technical requirement of being within 5 cents of the user desired frequency.



Figure 23, ESP8266 on NodeMCU Development Board

# 12.15 Clock

The type of clock that the group intends to use is being researched. With the ESP8266, compatible clocks will be further researched and tested. At this moment, we are looking at external clocks as opposed to internal RC clocks which tend to be inaccurate and are influenced by temperature changes. For external clocks, we have the choices of a quartz or ceramic crystal, silicon, or an external RC circuit. Our Pick Pocket Tuner will require the utmost accuracy when communicating. The processor will be communicating with the sensor, the display, and the motor driver all to perform precise measurements and calculations. Since our project has the engineering requirement of having the frequency accuracy be within 5 cents, we will most likely go with the silicon or quartz crystal choice, as these clocks have the best accuracy. Further research and testing are needed on these clocks and a final choice will also be dependent on the processor picked.

# 12.16 Charging Circuit

Since the team has decided on using battery, we wanted to implement a charging circuit. This is an enticing feature since it allows our project to have a sustainable way of being used. Replacing batteries is a hassle, and it creates waste by going through so many batteries assuming this product is used every time a musician wants to tune his guitar. Having replaceable batteries is more sustainable on the environment and just makes it more convenient if you want to reuse this product regularly. This product will be draining quite a bit of power as well because of the motor that will be implemented in the project. This means that the battery life may deplete fairly quickly, thus making it more inconvenient to go through many 2AA batteries all of the time.

# 12.16.1 Design of Charging Circuit

After performing some technical investigation, it can be assumed that we will need to find a circuit that can charge a Lithium-Ion battery (Li-ion) or a lithium Polymer (Lipo) battery.

Luckily LiPo Batteries and Li-ion batteries charge the same way, by requiring a constant voltage to charge the circuit. We are still looking into the size of the battery we will need; however, we will likely be using a 9.6V li-ion battery or a 3.7V LiPo battery. One important parameter to keep in mind will be the charging current rate. The current battery we plan on choosing has a max current rate of 1.35A, however, it is recommended that only a 0.5A current charging rate be used in the design. It also has a rated voltage of 9.6V and a peak voltage of 11.7V. Having all of these parameters in mind, we can start to develop our charging circuit for the 9.6V battery.

Integrated circuits have been created by companies such as TI to make help rechargeable circuits easier to design. One of the Integrated circuits we plan on using for our charging circuit is the LM317 from TI. Below is the basic schematic we may use for our design. The output voltage to the battery is should usually be about 17-18% higher than the voltage listed on the battery, according to online resources. Therefore, if we plan on using the 9.6V battery, this means that the output voltage from the charging circuit should be around 11.23-11.32V. Also, we only want a current of 0.5A to be entering the battery, so this parameter is known as well. If we know these two parameters, we can use simple equations to solve for what the resistor values should be in this circuit. The equations we will be using are shout below.

(1) 
$$V_{out} = 1.25 \left(1 + \frac{R_3}{R_2}\right)$$
  
(2)  $Z_{out} = R_1 \left(1 + \frac{R_3}{R_2}\right)$   
(3)  $I_{out} = \frac{V_{out}}{Z_{out}}$ 

Final Values:

 $R_1 = 2.5 \Omega, R_2 = 1 K\Omega, R_3 = 8 K\Omega, Z_{out} = 22.46 \Omega, V_{out} = 11.3 V, I_{out} = 0.5 A$ 

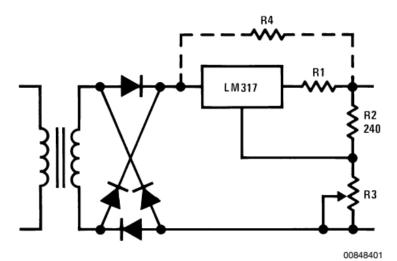


Figure 24, Charging Circuit Design with LM317 (Intellectual Design Provided by Texas Instruments)

Tas one can see, this circuit may not be the best to charge our battery, because the LM3117 is not very efficient and finding 20hm resistors is not easy and would not fit well

into our circuit. Also, since the devices in our project either run off of 12V or 3.3V, having a 3.7V battery may be a more efficient battery for us to use. Due to the fact that the voltage regulation should be much easier, and more efficient, our team will move forward with the 3.7V LiPo battery.

# 12.16.2 Charging Circuit Using MCP73831/2

After doing some further research on circuits for charging batteries, I found that there are many other options to use, that are more efficient, smaller and cheaper. One of theses circuits is the MCP73831/2. The integrated circuit has all the requirements we need for our project. The following paragraphs will discuss the circuit to be built around it, suppliers, implementation and plans to test this circuit.

#### 12.16.3 Requirements and Specifications of MCP73831/2

The integrated circuit has five pins, each with specific labels. These labels are STAT, VSS, VBAT, VDD, and PROG. The VDD label is the input voltage that is being provided by either a wall outlet or a USB-C cable. In our design we will most likely be using a cable that comes from a premade wall outlet that will work for our conditions. The VSS label is the designator for ground that the company who made this circuit chose. VBAT is where the positive end of the battery will connect to. This will be where our red lead wire coming from the battery will be connecting. That STAT pin is used to determine the charging status of the battery. In most diagrams, LEDs will be connected to this pin to indicate that the battery is charging, and will usually turn off to indicate that the battery has been fully charged. Finally, the PROG pin is used to determine the charging current rate. The datasheet for the IC shows different resistor values that one can use to regulate the current rate that goes into the battery to charge it. We are planning on using a 2K resistor for this to give us the fastest charging rate for our device.

The output voltage for this product is 4.4V which is perfect for what we need our project to be charged by. Since the LiPo batteries use the constant voltage method to be charged, the voltage charging the battery needs to be slightly higher than the rated voltage for the battery. However, the majority of the charging comes from the constant current method. The battery is mainly charged by receiving a constant current which will eventually raise the voltage of the battery until the rated voltage is reached. The circuit shown below is the layout we will most likely be using in our own design.

500 mA Li-Ion Battery Charger  $V_{IN}$   $4.7 \ \mu F$   $4.7 \ \mu F$  5 5  $2 \ k\Omega$   $2 \ k\Omega$   $2 \ k\Omega$ MCP73831

Figure 25, Simple Application Circuit by Microchip

This circuit is most likely going to be used in our design. The 4.7uF capacitors are the values recommended for the capacitances because it compensates for when there is no load.

One more component that will be added into out schematic for this circuit is the USB-C Charging port. This I where Vin will pass through so our circuit is able to be interacted with by the user. There are data lines on the USB-C port, but these will most likely not be used, since we are just trying to charge a battery. Adding this USB-C Port will also us to be competitive in a global market since the world is trending mostly towards the desired USB-C interface.

Something that our team must be aware of it any heat dissipation that might occur in this circuit. It seems that this IC can run warm, but through designing and testing different components used in this circuit, out team believes that the heat will not be a problem.

#### 12.16.4 Suppliers for MCP73831/2

Our team plans on ordering this circuit from Mouser electronics. They seem to have a very reliable track record, and they see mt have plenty of these chips in stock. Microchip themselves seem to distribute to a warehouse in Atlanta, which means that the shipping time for this product should not be too much of an issue. It also will help since this seems to be a pretty common circuit to come by.

# 12.16.5 Testing Process for MCP73831/2

Testing the design for our circuit should be fairly simple. We shall build the circuit using the components stated above, using a breadboard and electronic equipment to simulate and test our circuit. This IC can be ordered on a breakout board which will make it very easy to test. Once the circuit has been checked and all the connections have been made correctly, we will move forward with the simulation process. After the simulation is ran correctly, we can finally connect a battery to the charging side so we can ensure that the circuit is functioning correctly. After some charging is done to the battery, we will test the voltage level and make sure that the battery is charging. We will also take into account any heat that may come from the battery or from the IC, and make sure nothing is overheating or damaging any components. Once this method is perfected, we will create the final schematic layout in Fusion 360/EAGLE, and save the schematic.

# 12.16.6 Implementation Process for MCP73831/2

Implementing the charging circuit design will first start with implementing it into our PCB design. Once the schematic is created, it will be imported into our final PCB schematic. Once the PCB Design is finished, we will then design the board layout to have the charging circuit near an edge of the board so we can build our housing around that spot to allow a place for the port to stick out and be plugged into. This process should be fairly simple, however designing the 3D model of the housing around this component may be

fairly tricky, since none of us have a great deal of experience working with CAD modeling, however, we believe that after some trial and error we will be able to incorporate it well.

# 12.16.7 Prototyping Charging Circuit

For efficiencies sake, and the sake of gathering more data on the battery consistently, we will need a reliable way to charge the battery multiple times to give a detail specifications sheet. Therefore, having a charging circuit prototype will benefit the process of design and implementation. There are many premade circuits on the market that hep with charging batteries, but there is one made by Adafruit, that should give us exactly what we are looking for in our project. The device is very small and compact, and uses 5V USB Charging to charge the circuit. There is also an option to use USB -C which would be an even better implementation due to the fact that most electronics are starting to use USB-C more commonly. The circuit is shown below in comparison to a small LiPo battery and a laptop.

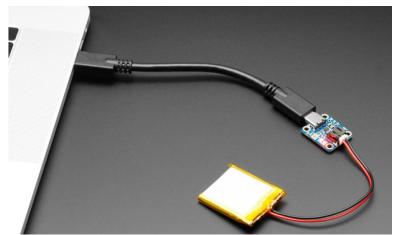


Figure 26, LiPo charging circuit to be used in prototyping and testing phase of project

This means that our project can be distributed anywhere in the world, and it should be able to be charged without a hitch. And as one can see, the circuit is very compact, and would fit well within our design requirements and specifications. Below will discuss how to implement and test the charger for our project.

# 12.16.8 Testing Charging Circuit

There are multiple criteria that we will be tested on this circuit, so that we can become very comfortable in utilizing this circuit. The different questions we will be attempting to find answers for are as follows:

- Does it work?
- How long does it take to charge a fully depleted, half depleted or quarter depleted battery?

- Can the circuit damage the battery?

Our team believes that these questions should give us all we need to know about how to use this prototype for our device.

The testing process to answer the first question is fairly simple. All that needs to happen is to connect the charger through a reliable USB-C port that already works. Once the connection is made, and the indicator light turns on, we will know that the circuit is receiving power. After it starts working, we will disconnect from the source and plug the terminals of the battery into the correct terminals on the charging circuit. It is worth noting that the voltage level of the battery will be tested before the circuit starts charging it. The voltage that is measured before the charge will be recorded so that it can be compared with the voltage levels. Now the circuit can be plugged back into a source, and left on for about 30 minutes. After the 30 minutes are up, we will measure the voltage level of the battery and see if it increased. If it has, then we know that the circuit is effective.

The next step in testing the charging circuit would be to see how long it takes to charge the battery at different battery lives. To test these ranges, we will be depleting the battery to each of the levels stated in the question above. After each level is reached, we will measure the time it takes to charge to full capacity at each charge. Once we find all of our times, we will see the consistent rate that the charging circuit supplies, and record that for our data once our project is completely assembled.

Finally, we will be testing overcharging, and seeing if that can either damage the life of the battery, or damage the battery in any other way such as heat. To test this, we will connect a fully charged battery to the charging circuit for a certain time period, and we will then discharge the battery fully. This process will be repeated a number of times to track the life of the battery and see if the battery life becomes weaker, or if there are any signs of damage. This will give us a good understanding of how our customers should go about charging their product safely.

# 12.16.9 Prototype Charging Circuit Implementation

The reason for prototyping a charging circuit, would be to learn how to implement a design of our own, or more specifically condense or improve designs that already exist on the market today. It also allows us to make sure other parts of our circuit are operating correctly and how we expect them to.

Firstly, we will be ordering one of the USC-C charging circuits from Adafruit, and testing it when it is received. Most of the teammates on the team have the capability of plugging this circuit into their laptops or walls with different devices that take the USB-C connection. This will make the process of testing very easy and convenient for us. Also, it is worth noting that the circuit comes with a standard charging rate of 100mA, which is going to be very slow if our battery has a capacity of 1200mAh. However, there is a jumper on the board that if soldered will change the charging rate to 500mA. This means that if our battery becomes fully depleted, it will reach a full charge in about two and a half hours.

This may seem like a large charge time; however, we are expecting the battery to last a long time on a single charge. The Roadie3 only has a 500mA LiPo battery, which means it charges quickly, but can also deplete quickly as well. Therefore, we expect the decision to include the longer battery life will be worth it in the end.

The implementation process for testing purposes is fairly simple. There are positive and negative terminals on the battery charger that connect to the positive and negative terminals on the battery. We must ensure that the connections are at the right terminals, or we could damage the battery or even the charging circuit. Once everything is connected properly, we will start to connect other parts of the circuit that will be powered with the battery to see how well everything is functioning.

# 12.16.10 Using the Prototype as Plan B

The goal for prototyping this circuit is so that we can learn how to design and implement our own. However, our plan B for this prototype, is actually using it in our final device. The team does not plan on using this circuit, however if we must get a working product next semester and this circuit is becoming a major setback, we will simply implement this into our design. All measures will be taken to ensure our best effort was put forth in designing a charging circuit that works.

# 12.16.11 Mounting Prototype in Housing

If it is absolutely necessary to use the Adafruit LiPo charger in our final project, then we will have to figure out a plan to mount the circuit to our housing design. The board comes with four through holes and each hole has a diameter of 2.5mm. The image to depict these holes are shown below.

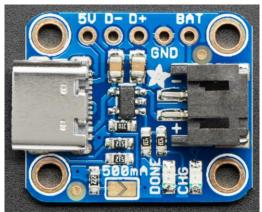


Figure 27, Image of Adafruit Charger Showing Mounting Holes

The plan so far is to mount the circuit using the four holes, and developing the mounting holes on the housing itself. We would need four very small screws, but this is a very common size so the screws would be very east to find. The screws will also most likely have Philips heads on them, since it is the most common design to find for screws this

small. This circuit will have to be very well secured, because it has to be able to withstand people unplugging and plugging in the charging cable. This can be a difficult process for some people, as some people struggle with depth perception, and plugging the cable into the small port with too much force could cause the mounting screws to shift or come out, rendering the mount useless. Therefore, it will be essential to ensure the circuit is secured tightly so as to be able to withstand uncommon forces.

# 12.16.12 Testing Process

The charging circuit will most likely take some time to perfect. The values and approximations shown above are just a baseline to where out charging circuit should start. This design overall may not work for us, however without testing, we will not know for sure.

The first step will be to deplete the battery at a decent rate. This can be done by making a circuit that will drain the battery at a steady rate, without overheating or damaging any of the components. Once the battery is depleted to about half of its battery life, it will be disconnected from the circuit that it was powering, and set aside. This gives us a benchmark as to how much batter life is left, and allows us to proceed with this knowledge.

The next step is to build the charging circuit on a breadboard, and test the output voltage and current we are getting without connecting this circuit to the battery. We want to ensure that it is operating at a safe voltage and current for the battery, before we can connect the two together. Once the team is either satisfied with the results, or have decided to take a different approach, then we will either connect the battery, or scrap the design and start over. If the next step is to proceed with connecting the battery, the team will test just that. After it is connected, we will test to see if the battery is charging like it should. Once the circuit is working properly, we will start a timer to measure how long the battery takes to charge once it is half depleted. If all thing go well, and the battery becomes fully charged, we will record the data we've collected and proceed on how to implement all of these circuits into our design.

However, if this plan does not work very well or at all, there are plenty of other circuit designs we could try to implement. Designing this circuit will most likely take a lot of trial and error, and possibly buying and testing charging circuits that are pre-fabricated to charge the battery in our project. Using a circuit that is already established in the market can give us amateur engineers something to use as a point of reference if we hit a designing wall.

# 12.16.13 Implementation Plan

The implementation process for this circuit will be fairly simple once the design is complete. The circuit will be connected to the positive and negative terminals of the battery, so as to connect in parallel. The terminals of the battery will also be connected in parallel with the voltage regulators that will be used to distribute the correct power throughout the system.

# 13.0 Printed Circuit Board Design

Designing a PCB is no small task. This part alone has the ability to make or break our entire project. There are also many steep learning curves when learning how to design and build a working PCB. This is definitely something that come with practice; however, our team plans on breaking the process down into smaller pieces to make the process go over smoothly. The following subjects will be discussed thoroughly as the regard to the design of the PCB:

- Overall layout of how we think the components will connect
- Power distribution and ratings
- Fusion 360
- Suppliers
- Prototyping and testing

All of these are crucial in our design, and will be discussed in the subheadings below.

# 13.1 Overall Layout of PCB

The layout of our PCB will be a very important quality in our overall project. We will plan on making it a compact as possible, and have a good shape that is affordable and will fit in an ergonomic housing. Most of the components we will have on the circuit board have small footprints, so this will aid in keeping our PCB on the smaller side. The ESP8266 has a very small footprint, however it should have plenty of computing power for what we need to accomplish.

#### 13.2 Power Distribution

Determining how power will be distributed throughout our project is essential to make sure all components are operating at the correct ratings. The table below shows all of our devices that draw power, and at what rate they draw electricity. There are some components that still need to be put under load and tested to see what kind of current they will draw. So far, this table gives us most of the measurements and estimates that we know of.

Component	Voltage	Current	Power
Motor/Encoder	12V	200ma (expected Load current)	2400mW
TFT Display	3.3V – 5V	100mA	330-500mW
ESP8266	3.0V - 3.6V	200mA	600-720.mW
3.3V Regulator	3.3V	200mA	280mW
12V Regulator	12V	0.7A	1270mW
Total			4,880 – 5170mW

Table 6, Power Distribution Calculations (Incomplete Table)

Finding out these measurements is crucial for when we start designing our PCB. Using what we measured will allow us to make sure every component gets the correct voltage and current they need to receive. Otherwise, we could run into problems of components being overloaded, or not running at the load they need to be running at, which could cause major issues for our final PCB. Knowing these calculations can also aid us in estimating our battery life. Knowing how many watts or amps everything draws is crucial in determining battery longevity, and it can also show us some areas where we could improve upon.

# 13.3 Fusion 360

The software we will be using to design our PCB will be Fusion 360. Fusion 360 is a very versatile tool, and will allow us to intuitively design our PCB from scratch. This was also the software that everyone on the team seemed to be most familiar with, so it made sense to choose this as our design tool.

Another contributing factor as to why we chose to use Fusion 360 as our development software was because it was made available to us through an education license. The license to use the software costs \$400 and since we have four group members, the total we would have to pay would be around \$1600 not including taxes. This was a huge savings on our development costs, and will allow us to be able to spend more of our budget on the physical components for our project.

Fusion 360 also has a very attractive user interface. Other Programs like EAGLE seem to be a little more rigid and outdated on the interface tools, however Fusion 360 has very good labels and icons that are easy to differentiate between. This feature does not seem super important, but enjoying and thriving on the design software should translate directly to the efficiency and ability to get work done on our design in a positive trend. So far, this trend has shown to be true and the team is able to work comfortably and on schedule. All of the listed reasons above show why our team chose Fusion 360 to complete all of our design for the printed circuit board we are developing.

# 13.4 Collaboration Method

Something else that was discovered throughout the development of our PCB, was the collaboration method that can be utilized in Fusion 360. This collaboration method works similarly to how Google Drive works, except it is used for the development and design for a printed circuit board. The students were able to create one big project for all of senior design and share the emails used for their accounts, and allowed the folder to be shared between all of the students. The two electrical engineering students Paul Grayford and Lucas Grayford are the main developers of the PCB and are able to work efficiently together through this process of collaboration. The folder containing all of the schematics that were designed are shared between everyone, and both of the students can work on the schematics together in real time. The most efficient way that the to students are utilizing the tool that Fusion 360 implemented is to work on different circuits of the PCB to and once they are finished, copy and paste them into our main design file. This allows

the circuit to be built in individual parts, which will aid us in our overall design by being able to make adjustments wherever we see fit. It also allows each of the students to become more of a subject matter expert for each part of the circuit by allowing each team member to have a hand in something that they were able to design and research themselves.

An example of utilizing this feature would be when Paul Grayford was designing the voltage regulator Circuit, and Lucas Grayford was figuring out the connections from the ESP8266 to the LCD display within our project. As Paul was developing the regulators, in the same folder Lucas was able to work on figuring out and trouble shooting the connections for the LCD display in real time. Both were available to ask each other questions and see what the other was working on real time. Both students were able to assist each other, and in the end complete the design for each circuit and paste them into the main PCB file making the process run very smoothly. This was only one example of many where we were effectively able to communicate and collaborate on different parts of the circuit together.

# 13.5 Designing Components Using Fusion 360

In a perfect world Ultra Librarian would have all of the footprints and symbols we need for our project, however that is not the case. There are some components that we had to design in our project on Fusion 360 itself. An example of using the design tools would be designing a footprint for our piezoelectric component. Paul Grayford headed up this task by first creating a new library that would include all of the student made components for our project. After the library was created, he attempted to create a new part from scratch. After a substantial amount of time learning how to create a symbol, he still was running into issues on how to actually design the component needed. Since he did not want to waste time, after doing some research, he tried importing a similar design and modifying it to the specifications required for the component. This seemed to work better, as he found a library that had a buzzer with a similar footprint. Since buzzers use the piezoelectric disks like the sensor we are trying to implement into our project, it ended up being a good choice to modify. After he modified the symbol, for the schematic diagram, he was able to modify what it would look tike for the footprint to be on the PCB. The symbol and footprint are shown below.

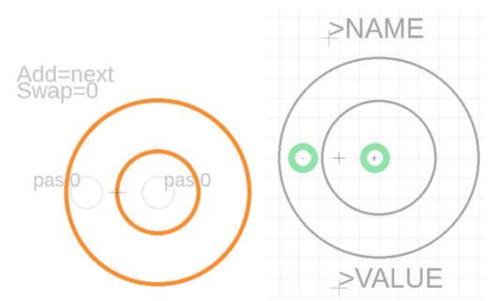


Figure 28, Student-Made Piezoelectric Sensor (Symbol on Left and Footprint on Right)

The actual modification process was learned very quickly. Once the old part was imported, one could select the lines, pins, and other important features of the symbol and modify them so that they fit the description of the part needed. The creation tool also lets you delete segments that will not be used and add segments that will be used. The circular features on the footprint were added in with the draw tool and were modified with accuracy using the dialogue box that changes the width and height of the shapes. The pins that actually connect the wires also had to be adjusted with their position They can be seen as the very faint gray circles that have the labels on them. For the footprint itself, the modification was very simple. All that had to be done was adjust the radiuses of the circles so that they would reflect more of what the component actually looks like. Once this was accomplished both parts of the component were complete and ready to be used.

After the footprint and symbol were made, it was saved in the library that was mentioned before. This allowed our new component to be added to the PCB design by importing the library with the library manager into the main design file. After it was added to the project, the part can now be added with ease by anyone who has access to the main printed circuit board file. Other components needed to be adjusted as well like the Zener diodes, because they were taking up a lot of real estate in the schematic diagram.

Learning how to use the creation tool was very useful and will continue to become a convenient way for us to implement components into our design, even if we could not find a file online that has everything we need. It will also be valuable experience for us to learn how to make different components if this ever comes up in our career path.

#### 13.6 Supplier

The team plans on using the company JLCPCB to supply us with our printed circuit boards. After doing some technical investigation, they seem to be the best company for our needs. JLC provides boards for an affordable price, and they allow the buyer to buy in bulk, which will come in handy once the PCB design is perfected and we are able to have backup boards in case of sustained damaged or unexpected road blocks. Overall, the company seems to have a great track record and will serve us best once the team is ready to start ordering PCBs.

#### 13.6.1 How to Order from JLCPCB

Ordering from this company is fairly simple. Once the board layout and schematic designs are complete, then we will need to generate what is called a Gerber file. The file is used to show all the traces that are used on the board, and will allow them to print the device clearly. Once the file is uploaded, there are many options to choose from such as; How many layers, arear of the board, color, thickness of the PCB, how many boards to be ordered etc. Once all of the selections and preferences have been made, the billing addresses and the checkout is then filled out. JLCPCB claims that the build time for most of the PCB's they build only takes up to 24 hours and then will only take 3-5 Business days to ship. This is a very quick turn-around time, and will be beneficial if some of our boards do not function properly because it will allow us to order replacements in a timely manner.

JLCPCB also gives the option to assemble the components on your board for you. This could be a helpful tool for us to use since we have so many small resistors and capacitors to keep track of, which means that our team could spend a substantial amount of time soldering all of the small components and could make us lose time on testing and design fixes. Therefore, this could be a good option for us, even if we can have JLCPCB assemble certain parts of our PCB, it would save us a lot of time. Also, soldering on the ESP8266 will be a challenge because the distance between the pins on the MCU itself is very small and would be very difficult to solder as amateur engineers. If this piece can also be assembled on the PCB before it ships to us, it would save us a lot of time as well. As the PCBs starts to get ordered, and the process becomes more familiar, we will be able to adjust and order everything we need for the completion of this project. The only downside to this method would be the price. Having it assembled for u is about 3.5x times the price in some cases. This may be something we look towards down the road if we are in a pinch and do not have the time to spend on the task of soldering every little piece as mentioned before. Overall, this method is something to keep in mind if we are

Finally, the pricing of the boards is very affordable, and can be as low as \$2.00. This will most likely not be the case for our board, as we will have many traces, however it should still be pretty affordable, especially if we order more than 1 board at a time. Overall, this should not be outside of our budget when it comes to finally ordering multiple PCBs.

# 13.7 PCB Assembly

If the team decides to assemble the PCB on our own without the help of any supplier, there will need to be a process to assemble the PCB smoothly. Something that will make this process go well be the labeling of the location where each specific component will go. This labeling will have to be placed on the PCB by the fabricator of the board. Something else to consider will be how to keep all the parts separated so as to not get any resistors or capacitors mixed up. Since we have so many semiconductor devices on our PCB that are of different value, it will be a challenge to keep everything organized so as to not solder on the wrong component in the wrong spot of the board. One way to mitigate this risk is to keep the resistor or capacitor in the package until it is ready to be placed. Once it is ready to be placed, the semiconductor will be taken out of the package, and immediately soldered onto the board in the correct spot. This will ensure that we do not have any random semiconductors laying around that could be lost. This process will be time consuming, however it will reduce the chance of losing certain components or placing them in the wrong place. Another way to keep track of all the pieces would be to have the bill of materials open as we're are placing materials. This will allow us to cross components off as we work, and reduce the risk of missing components. It will also help us to stay organized as to what was put on the board already and what was not.

If the above theory somehow goes wrong and a semiconductor is taken out of the package before it is marked where it needs to go, then there needs to be a plan to make sure that the component is taken care of accordingly. The following steps should be taken in order to ensure the product is placed where it belongs:

- 1. Once the semiconductor is found outside of the package and the package is nowhere to be found, stop all production.
- 2. Measure the semiconductor to see what value it carries, and take one of two steps below
- 3. Either:
  - a. Find the location on the PCB and immediately solder the component on
  - b. Or, mark the value and label it as such, stash it in a safe, organized place and continue working on the task at hand before placing the part down
- 4. Continue work once all steps above are complete.

Taking these steps should ensure that every component is accounted for properly and in an organized manner. Not only will these steps reduce the amount of headache during the process of assembling, it will allow us to reduce any unnecessary waste when it comes to cost and time. Cost because if we lose components or damage them, we will have to buy more. Time because the ordering time of these components could set us back a substantial amount of time. Overall, we need to be careful about how we approach the whole assembly process of the PCB.

The actual order that the components be soldered to the PCB could be significant in the amount time spend soldering on the components. Not only could it be time saving, but it could reduce confusion on where components should go. The plan to solder the PCB

components on to the board is to start with the largest components and work our way down. This means soldering on components like the regulators, power transistors, and the ESP8266. This will allow the rest of the components wall into place more easily. Because the larger components will be places, the small semiconductors will start to line up, and it will start to make more sense where stuff goes.

# 13.8 Testing the PCB

Once our first PCB is ordered, it will be smart to assume that the design will not work the very first time it is created. Testing our PCB effectively will be crucial on how we proceed with the project. If the PCB has a design issue and is not working for whatever reason, efficient trouble shooting and critically thinking effectively will be imperative to improving the design and acquiring the desired results for the circuit. It will also be important to test if ALL functions of the PCB are operating properly. The team will not be satisfied if the PCB design is just "good enough." We want to ensure that the PCB is doing what was intended of it, and to make sure that every single function works on the board.

The process for testing the PCB is fairly self-explanatory. We will connect all of the components of our project to the board, and generate a signal with a DC power supply to project and see how everything behaves. Once we have diagnosed and fixed all of the bugs that we will most likely have, then we will start trying to implement our design with the battery we choose, and see if we can generate a similar response. Once all of this is accomplished, all that will be left will be designing the housing for the whole project to fit into, and putting everything together in a way that will allow everything to operate at maximum efficiency.

# 14.0 Prototype Construction

# 14.1 Prototype Construction Beginning Notes

At the time of writing this document, we are still doing further research on parts, interfaces, and individual components to potentially use. As such, this caveat is included in all subsections as the parts mentioned in this document are subject to change due to manufacturing constraints, shipping delays, overall part availability, and final determination of usage based on the technical research done on these or other parts.

# 14.2 Prototyping Components

# 14.2.1 Processor/Controller

The processor/controller used for prototyping the Pick Pocket Tuner, at the time of writing this document is based around the ESP8266 microcontroller. The board used is the NodeMCU Amica-ESP8266 prototyping board which contains the ESP8266 microcontroller as well as soldered on-board pins for prototyping ease through a traditional breadboard or direct connection to the soldered-on pins, with a USB-micro

connection for ease of use when necessary to implement software to use for testing. This board was procured by the Team Member Luis Vargas, as he was previously familiar with the board and had spares to be able to provide for testing. This board is a simple open-source IoT platform, and is connected/interfaced with, through the Arduino IDE with the CP2102 Driver and the appropriate ESP8266 board manager library for the Arduino IDE platform. For readability this board will be referred to as ESP8266, the board, or simply MCU.

The set up for the testing environment for the Arduino IDE assumes that the Arduino IDE is already installed and is working correctly prior to proceeding further. The interfacing between the Arduino IDE and the MCU requires that the board manager for the ESP8266 family of boards be added, manually, to the Arduino IDE in order to then explicitly add the correct board to be able to upload the software appropriately. In doing so, this enables the Arduino IDE to communicate through a serial connection to the ESP8266 board allowing for the total use of the available pins and functionality of the board. Once this is accomplished, the Arduino IDE must be configured to recognize the board at the correct COM port to be able to gain full functionality at 9600 Baud, which is especially important when using the Serial Plotter or the Serial Monitor in the Arduino IDE. With the assumption that this works correctly, we are now ready to begin utilizing the ESP8266 for prototyping the project.

# 14.2.2 Sensor

The sensor utilized in the prototyping of the Pick Pocket Tuner still remains to be the Piezoelectric sensor defined under the previous Vibration Sensor section, where it is explained what function this sensor is to serve. This Piezoelectric sensor will be directly connected to the MCU so as to be able to utilize it as the main point of contact at which we will begin to test the capabilities of vibrational sensing and thus begin our signal processing. Given the importance of this piece to the Pick Pocket Tuner, there were two sensors initially purchased to be able to submit to testing from SparkFun Electronics, the first a circular ceramic disk Piezo sensor (part no. SEN-10293), and the second being a flexible PVDF polymer-film Piezo vibration sensor (part no. SEN-09196).

For both of these devices they are connected to the MCU through the analog input pin that the board has, as these are devices that generate an analog 'signal', vibration, to be processed into what we ultimately need to be able to accomplish what Pick Pocket Tuner set out to do.

# 14.2.3 Motor

The motor utilized in the prototyping of the Pick Pocket Tuner, at the time of writing this document, will start with a 5V DC Stepper Motor, model 2BYJ-48. This motor has a 4 coil unipolar arrangement with each coil rated for +5V, a torque of 0.03 Newton-Meters, and has 64 steps per revolution, thus making it a relatively simple motor to begin prototyping

with since it is not difficult to control with microcontrollers, like our ESP8266. This motor was procured through a kit that Team Member Jamie Henry already had in his possession. This motor is interfaced directly with the motor driver, which is identified in the Motor Driver section below. This motor/driver combination is then directly interfaced with the GPIO Pins on the MCU corresponding with the appropriate pins on the soldered-on board. Additionally, this motor requires an additional and/or externally supplied 5V DC power in order to operate appropriately.

After determining that the previously mentioned motor did not produce sufficient torque to appropriately turn the tuning pegs on a guitar, much less so for a bass guitar, and as a result of this we decided to move towards using the DFRobot FIT0441 Brushless DC Motor with an operating voltage of 12V that has a torque rating of 2.4 kg\*cm. This motor should be able to provide a sufficient amount of torque to turn the tuning pegs of just about any of the instruments we intend on testing our device with.

#### 14.2.4 Motor Driver

The motor driver used in the prototyping of the Pick Pocket Tuner, at the time of writing this document, will start with a Texas Instruments ULN2003AN Stepper Motor Driver, which is already connected to a pre-made PCB. This PCB is to be used as the primary interface/driver for the 2BYJ-48 motor mentioned previously. For the remainder of the Prototyping Components, the Prototype Testing, and Integration of Parts sections, when referencing 'the motor', the reader is to assume that the nomenclature is inclusive of the motor AND the driver simultaneously for simplification and ease-of-readability by the reader.

This 16-pin driver from Texas Instruments is chosen for initial prototyping since it came with the 2BYJ-48 motor in the parts kit that Team Member Jamie Henry already had procured previously. This ULN2003AN driver is made up of seven high-voltage, high-current, NPN Darlington transistor pairs that utilize suppression diodes for inductive loads with a base resistor to each Darlington pair. This combination of devices allows for the driver to maximize the effectiveness allowing operation directly with supply voltages of 5V, over a wide temperature range of 40°C to 105°C. This driver will be directly connected to the appropriate GPIO/Digital pins on the board so that we are able to control the stepper motor appropriately.

Similar to how the progress of the initial motor went, the ULN2003AN Stepper Motor Driver will be changed for the encoder that comes integrated with the DFRobot FIT0441 DC Brushless Motor described previously. This integrated controller comes with the leads necessary to be able to interface with it and is directly connected to the rear portion of the housing on the motor itself.

# 14.2.5 LCD Display

The LCD Display that will be used in the prototyping of the Pick Pocket Tuner, at the time of writing this document, is the Adafruit 1.69" Round Rectangle Color IPS TFT Display.

For simplicity, and ease-of-readability-and-reference, for the remainder of this document this aforementioned LCD Display will be referred to as simply as the 'display', 'LCD', or as the 'screen'. The display is an IPS-TFT, which means that this is an In-Plane Switching Thin-Film-Transistor display. This IPS-TFT model is an LED based LCD that due to the IPS allows for some of the best color reproduction and viewing angles among other types of common display panels, and the TFT allows for improvements in image contrast as well as addressability.

This device was procured by Team Member Paul Grayford from Adafruit (Model No. ST7789, Product ID: 5206). The full interfacing of this device is still under technical research status at the time of writing this document, however from preliminary findings it is determined that the display is able to be integrated using the SPI communication interface on the ESP8266 based on the datasheets of the display. The interface for the display through the MCU is through the SDMOSI, SDCK, SDMISO lines which the MCU is able to utilize to communicate the necessary data through.

# 14.2.6 USB-C Charging Circuit

The USB-C Charging circuit utilized in the prototyping of the Pick Pocket Tuner, at the time of writing this document, will start with the Adafruit Micro-Lipo Charger for LiPoly Batt with USB Type C Jack from Adafruit. This charging circuit was procured by team member Lucas Grayford. This charging circuit has breakout pads that allow for 5V, two data lines, D+ and D-, a GND, and VBAT. This charging circuit already has a USB-C jack soldered on, has a 100mA charging current with the capabilities of increasing that charging current to 500mA by shorting a jumper to facilitate fast charging in the device once integrated.

# 14.2.7 Battery

The battery utilized in the prototyping of the Pick Pocket Tuner, at the time of writing this document will start with the Lithium-Ion Polymer Battery -3.7V 1200mAh from Adafruit. This battery was procured by team member Lucas Grayford. This battery, as described above, is 3.7V output with a 1200mAh runtime. It is currently our choice for prototyping, and further integrating into our design choice.

# 14.3 Additional Components in Prototype Construction

# 14.3.1 Piezo Sensor Filter

The filter that will be used in the prototyping of the Pick Pocket Tuner, at the time of writing this document, is a Resistor-Capacitor based circuit. The purpose this filter serves is to take the input signal from the piezo sensor and then 'clean-up' the signal so that it is more easily read by the analog input pin on the MCU. The topology of this filter is simple, and still subject to further technical research and testing, however for the time being it is being used for initial prototyping. This filter takes two resistors at  $1M\Omega$ , R1 and R2, and two

capacitors. One capacitor, C1, is  $0.1\mu$ F and the other, C2, is  $0.01\mu$ F. They are all connected in parallel in the following order: In – R1 – C1 – R2 – C2 – Out. On the input side, we connect the Piezo electric sensor on the positive terminal and the negative to ground, on the output side we connect the positive terminal to the analog input pin and then the negative to ground. This is what we will initially use to clean-up the input analog signal from additional signal noise to the ESP8266 so that we may progress in our prototyping.

# 14.3.2 DC-IN Power for Breadboard

This piece, although seemingly inconsequential, is necessary since it will be used during prototyping to provide power to our devices when they require additional external power that the MCU cannot provide. This piece is unlabeled; however, it was procured by Team Member Jamie Henry in the same parts kit that was used to procure the initial motor used for prototyping. This DC-IN board takes power from a 9V/1000mA power supply and converts it to either 5V or 3V for use on breadboards. For initial prototyping purposes, it was primarily utilized as a 5V output to provide the necessary power for the motor to be used.

#### 14.3.3 3D Printed Guitar Peg-Winder

The peg-winder that will be used in the prototyping of the Pick Pocket Tuner, at the time of writing this document, is a 3D printed peg-winder procured by Team Member Lucas Grayford. This device is attached through friction onto the moving stem on the 2BYJ-48 motor so that we can affix the winder to the tuning peg on a guitar to test if the motor produces sufficient torque to be able to move the tuning peg during initial testing, and ultimately to be able to determine how much to turn the peg-winder to be able to tune the guitar.

# 14.4 Next Prototype Construction Steps and Ending Notes

At the time of writing this document Group 42, has only begun prototyping the currently acquired parts. The parts which we are in progress of researching, procuring, and testing include but are not limited to a ¼" input jack, other motors capable of delivering more torque and speed, and other piezo sensor filters to clean up the input signal. Additionally, the preliminary artist rendition of the mock-up of our system prototype is in Figure 20, below. Fig. 20 contains a breakdown of all the included parts in this initial prototyping phase with the wiring diagrams of the tested devices. Those devices which are part of the Prototyping Construction section but are still under technical research, i.e. the display, will be included in the mock-up, however specific wiring will not be included in this diagram.

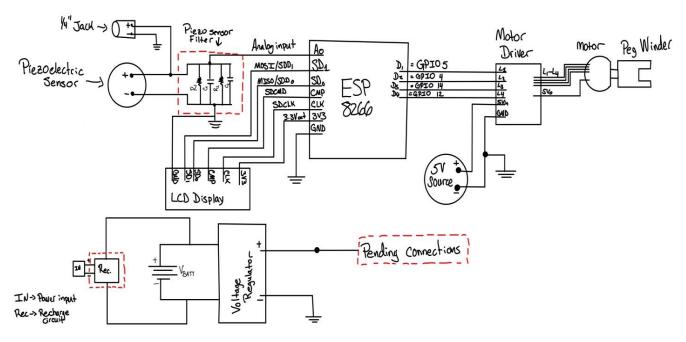


Figure 29, Artistic Rendition of the Initial Prototype Mock-Up

# 15.0 Inside of the Jowoom

We ended up finding a similar style of a tuning device as the Roadie but a bit more of a primitive type system that follow most of the same principles that we are going for but, we are going more for the interface style than how the Jowoom is. When taking apart the Jowoom it was held together by 5 screws mainly, three 20mm x 2mm screws and two 8mm x 2.5mm screws on the front face behind the peg head where there is also a screw holding the peg head in place too. After prying the case aside there were a quite a few things to learn how they went about making the Jowoom.

The first thing that was noticed was the brushless DC motor that they decided to use for their tuner which inspired us to make the change to a similar type motor for our design but the one we are using is a little slower in rpms but is still higher and faster than the Roadie 3 version. The motor they used is about a quarter longer than the motor that is being used in our design. The other thing that was noticed about their motor was it war a 6-pin motor than our 5-pin motor. We do not know what their extra pin line was for but maybe an extra control line.

There were a couple other things that we noticed that could help us improve upon our design, and one of the things was a extra vibration sensor that was tied in parallel to their system. One of the sensors was tied and mounted to the housing on the inside so it would be able to pick up the vibrations better when the housing is in contact with the instruments peg head, then the other sensor was tied to the board so it could transmit the vibration

signal to their embedded system. It seems like a smart decision to do that for our housing and properly mount the secondary vibration sensor on the inside of the housing like the Jowoom.

The reason stating that their system is a bit primitive is that they did not have a processor for determining most of their calculations and it was more of an embedded type system. Their system has three different select modes for the styles of tuning, which are a little hard to navigate though without the use of the user manual to get the exact setting type that the user is looking for. The first standard startup mode is the auto mode, which is the easiest mode to understand and works pretty well overall. Just put it on the tuning peg and pluck the corresponding string for that peg and it quickly reads the frequency range that the string is close to and make the adjustment to the peg and does a double beep and lights the green led to tell the user that the string is done and to go on to the next string.

The other two modes are custom and semi and the user can press the "s", button on the Jowoom to select the string type customization, which can be a little confusing for a novice to use its interface. The nice thing it has is a string number and the corresponding letter pitch for the string. It also allows the user to select through three different selections being guitar, "uke", and "chrom." Uke being short for ukulele setup and chrom for chromatic selection. However, the interface was being stubborn going to those selections after taking the device apart and putting it back together, even following the user manual to get to the settings.

The Jowoom has five buttons but really only two of those buttons are really used for the Jowoom, technically there are six buttons if including the reset button, but to access the reset button it requires a needle or pin to press it. The two main buttons used are the power and mode, simply to just turn on the device and mode button to change between the three selection modes when pressed and held. When just simply pressing the mode button it allows the user to manually select between the strings. Two of the other buttons are a up and down for manual winding mainly for quick manual restringing, buy our tuner will not have that and rather a restring option in the interface that will get the string to a close tune. Then the last button is the select button which allows the user to change the mode more for guitar, uke, or the chromatic settings.

There is only a plan to use three buttons in total for the Pick Pocket tuner. The buttons will be mainly as stated before in the buttons and switches section to have a left, right and select option, and hold select feature to go back or back to the main menu. Another feature the device has that was noticed later on after using it was that it has a auto shut off feature when the device is not used for around over a minute. For our device that won't be possible if we use a switch method, but there is a thought to add a chirp or beep to notify the user to turn off the tuner if it is no longer being used, so that the power can be saved in the system.



Figure 30, Jowoom internals

They had it set to be very simplified to where it had more of thresholds to adjust the tuning to match the frequency it needed. So, most of the outcomes are already hard set than calculated which can make the system quick and simple to use. For the system that is being designed on our end is going to be more of a mix of the Roadie and the Jowoom so there can be best of both worlds but will be more like the Roadie but a cheaper option and lighter than the Jowoom because their system is not heavy in the hand being 212 grams, but it still has a solid feel to it, where most of the weight is the motor and battery.

They designed their PCB board was a little odd besides it not actually using a processor. The board fills up most of the upper side of the of the board and there is a lot of empty space wasted in the design next to the battery that they used where their design could have been much slimer but there are 3 large components on the back that cause that space being a large inductor, capacitor, and the buzzer but then it is just empty room after that. They could have saved room on the battery that they used and used a LiPo battery like the Roadie but the guess was that they were going more for longevity and not needing to make as many recharges. The other thing that was the custom LCD display up by where the motor was housed and chip that they used to run through the LCD.



Figure 31, Jowoom internals front side

Overall, we are not going to reverse engineer and exact version of the Jowoom, but this gave us a lot of good insight on where to go and how to implement some small changes on our system that we may have missed in the first place. It allowed us to think over certain changes in the original design like the battery and motor change.

# 16.0 PCB Layout

Once all parts were finally picked and attained for the overall final design the PCB layout is able to commence and start a prototyped design for the main components of the tuner's design. First thing is determining what components are going to end up being on the PCB, most of the components are going to have lead wires running to the actual board. The components that are going to have pin headers and run lead wires to the board are going to be the battery, switch, motor and screen. The main components that are going to be on the actual PCB are the two main regulators being the 3.3V regulator and the 12V regulator, the last component attached to the board is going to be the ESP8266. The rest of the components will have varying pin headers placed on the board.

There are some problems with a good amount of the components, a lot of the components wire pin head types do not come with matching connector types. There is a problem trying to find the end connectors and making sure they match. The other problem is that the

libraries for most of the pin connectors are not available and either need to be downloaded from a potential unknown source or custom design. Instead of potentially wasting money on buying wrong connectors and trying to waste time troubleshooting, was the main reason for deciding to cut lead wires and run straight to pin headers. There is also a problem in supply chain issues with most of the components which goes back to the more of the moneysaving idea. A good amount of the connectors were only available in a large bulk buying amount, that's if they were even the right connectors, also most of the vendors had supply and demand issues and were about 30 weeks out on some of the lead times. The idea is more for ease of use than looking pretty, also the housing is going to be sealed away so the wires will be hidden out of view, there will be some cable management done when it is all put together in the housing so it will look more presentable if someone were to open the housing. This was the main idea for getting around some basic problems and still keeping the method to be practical.

### 16.1 Ultra Librarian

Ultra Librarian was what was mainly used to get most of the schematic and footprint designs for the PCB layout. There were problems with most of the products that were from the Adafruit library, where they would have lookup information for the components on file but not have any actual footprint and schematic files to go with them. It does not make much sense to have products on file then have zero things to provide under the file type for the product. Ultra Librarian gave footprints and schematics for regulators, ESP 8266 and the power MOSFETs for the regulators. For the regulators, even though we were limited to the regulator types that were available for use, since supply and demand issues were present for most of the more common and efficient type regulators, we had to use the largest regulators and not the most efficient ones because there is not much that could be done about the situation. The ESP8266 gave a nice schematic and the only changes that needed to be made to it was some channel labeling for the input and output pins for all of the possible lines that need to be run to interlink all of the proper components for the system. Even though Ultra librarian had its limited uses for what we were able to find and use it was still a helpful tool with key parts that were needed in the overall PCB layout and design.

### 16.2 PCB Parts Placement

The first component on the far left of the schematic is going to be the USB-C type charger for the battery, which will connect to the power line of the battery to allow for recharging. The battery and the switch are going to be tied to a 4-pin header. The idea is to cut the lead wires for both the battery and the and the switch and attach female end adaptors so that they can plug into the male pin headers. Ground will run to pin 1 and power from the battery will run to pin 2. Pin 2 and 3 will be wired together on the PCB board design and the power switch lines will be connected to 3 and 4, where 4 will be the main line that runs off to the two regulators that will run in parallel to the rest of the system. The 3.3V regulator will then run into the ESP 8266 input pin. From there are mostly interconnections with all of the GPIO pins and other data lines running to each set components. There are a total of eight main components that are going to be interconnected with the ESP 8266, which

are the four different pin header runoffs, two 1x2, one 1x5, and 1x8 pin headers. The other 4 components are going to be the three buttons that will be connected to three different GPIO lines and having a data line voltage sent through them to know which buttons are going to be pushed. Each button requires a  $1k\Omega$  resistor runoff to ground. The last component tied to the ESP 8266 is the buzzer that is going to be used for indicating when the tuning is complete for the peg being tuned and to go to the next peg or when fully done tuning.


Most of the components are going to be laid out surrounding the ESP8266 to make routing lines as short as possible and keep it as efficient in layout planning as we can. Since most of the components plugging in are going to be done through pin headers it allows us to line up most of the lines to the right places without tangling lines up too much. The two largest pieces that are going to be in the way on the PCB are the two rather large inductors which will take up most of the room on the PCB layout design. The target design is to have the board be nice and compact but not too compact where the inductors might give off some interference to the other electrical components. The layout is going to roughly follow a similar layout to how it is setup in the schematic and for how it is arranged too. The battery and switch will be far off to the left-hand side of the setup where the charging section will be too. Next the regulators will follow and will be formed rather close together and will sit parallel to each other, but inductors will be slightly off stacked diagonally from each other so there will be some room for them. Next to follow is the ESP8266, pin headers, buttons, and buzzer which will off to the right-hand side of the regulators.

The locations for most of the components are going to lead to a more elongated type of breadboard design which is okay for what we want since the housing and PCB are going to be going hand and hand with each other. There are other options for changing the variation on the PCB since there may be problem that could happen to the first board whether it will work correctly or not, which would take a little more time since corrections would need to be made and any adjustments in the layout placement for the board. The board is going to have a flush fit to sit at the base of the housing or to the top of the housing. The main cause for it being on the top side is because of the buttons need to be able to get pressed or else it makes the useless if they are not accessible for the user. The layout could have a change to make them run lead wires too if they are not able to extrude from the housing to be pressed by the user. The goal is to have the board mounted with 4 through holes on the edge of the board with backside surface mounts on the housing that will line up with the holes to hold it in place securely. The through hole size will for 2.5 mm screws length may vary with housing.
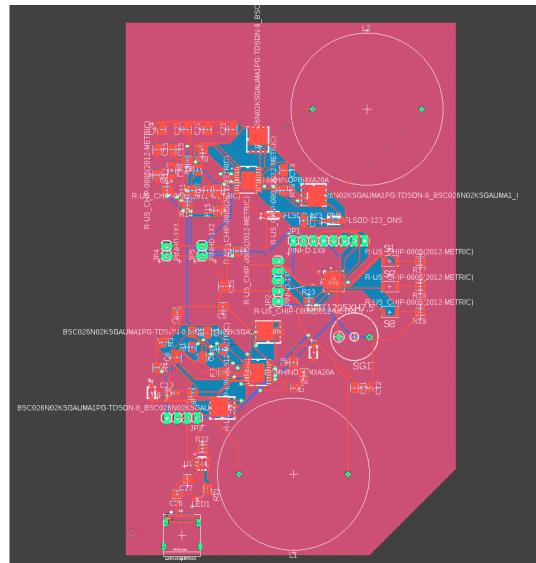
#### 16.3 PCB Lead Wired Part Placements

There are some other components that need to be considered for how they are going to be placed around the PCB even though they are not going to be attached to the PCB directly. This applies to battery, motor, display, audio jack and the power switch. The battery will be tucked on the lid of the housing with a plastic bracket holding it in place with a small dab of glue to make sure it stays in place better in case the device gets dropped or knocked around. The motor was already described for how it is going to be

mounted in the housing, and it will sit just above the ESP 8266 and out of the way of the lead wire. It may protrude out slightly depending how much room is going to be given. The display screen is going to be as close to the buttons as it can possibly be so it is more user friendly because it will not make sense to have the buttons on the opposite side of the screen, original idea for the screen was to put it on the butt-end of the device opposite of the motor head, if that were to be the case then the buttons would need lead wires run to them. The audio jack and switch are the two most flexible pieces for the design because they can be mounted to the housing wherever there is room left over for them to sit, both also are having lead wires run to the board, the only thing to focus on is not tangling up all the lead wires that are running inside of the housing. This is all possible to change in the final design.



#### 16.4 PCB Prototype

Figure 32, PCB prototype

There are some finishing touches that still need to be made to it mainly being the through holes for the drilled location, and routing the vias in. There is a difference in the version being used which does not have a rats nest option to put everything together. There is also a issue where converting the whole piece to the 3D design would not work and put the layers in and it would just put the component pieces in only.

### 16.5 PCB Wiring

To aid the group from confusion of which lines go where the ESP 8266 routing pins table to lead wire components will be used. This will help keep track and save time from second guessing for what wire went where and can also help for later changes in the design if there was a wire that was previously sent to the wrong spot and can easily be fixed with a simple rerouting. This will also be used to help keep lead lines under better control that will be wired to the components before soldering the lines wrong. It is not mentioned in any of the tables but the input line for the ESP 8266 for voltage in coming from the regulator is pin 7- CHIP\_EN, which enables the chip high for on and low for off and small current consumption.

ESP 8266 Pin # / Type / Other	Motor pin # / Type
10 – MTDI, GPIO12	1 – PWM
33 – GND	2 – Power (GND)
13 – MTDO, GPIO15	3 – Direction
9 – MTMS, GPIO14	4 – FG signal (requires 5kΩ resistor)
12V Regulator	5 – Power (12V+)

Table 7, Motor Pin Connections

Most of the pin connections of the motor were a little more complicated that what they should be. For the first part the motor lines come with a nice ribbon with partial incorrect labeling which is bad and already lead off a couple things to be more confusing. The ribbon does not mention that is goes with any proper method for the final joint end connector. Some of the lines trade places so it made it harder to determine what each line was and what each line's function was on top of that.

The motor said it could be used to plug straight into an Arduino board which was a lie, because even in the diagram that they show they do not us the straight plug-in connector and rather send out lead wires to the corresponding pin ports that are also poorly shown. For the plugin side that is supposed to go straight to Arduino, we snipped that end off completely, so there is no hassle needed to go around and find the proper end connection that will work and trying to configure the lines that were mixed up on the wire ribbon.

On top of everything to make matters worse the lead wires do not match the diagrams color coding sequence. The only lines that do match the two power lines for line two being the black power line for negative/ground and line five being red for positive power. The

wire coloring coming out from the motor from line one to five was: blue, black, yellow, green, and red. In the diagram provided on the pdf for the layout of the wires from one to five was labeled: grey, black, blue, yellow, and red. This already leads to basic confusion if the lines are even the same, but its not all bad in the end because the three wires that are the main confusion are all going to different GPIO pins. The actual truth will come from the GPIO pins when testing the software through each pin. The lines may take more time with having to reconfigure the motor commands in the code.

ESP 8266 Pin # / Type	Display pin # / Type
33 – GND	1 – GND
3 – VDD3P3 3V	2 – 3v3
21 – SDIO_CLK, GPIO6	3 – CLK
20 – SDIO_CMD, GPIO11	4 – CMD
23 – SDIO_DATA_1, GPIO8	5 – SD1
24 – GPIO5	6 – D1
25 – GPIO3	7 – D2

Table 8, Display Pin Connection

The display connection pins are more straight forward when connecting the lines to the ESP 8266. Most of the lines corresponded between the datasheets, but the displays data sheet was not every clear with some of the pin run offs. The first five lines are using the main descriptions and not the GPIO pins, but they were added for labeling just in case, however, the last 2 pin line for D1 and D2 are going to be using GPIO pins for the digital display. There was a debate to whether the display should have been directly mounted to the PCB using a 1x11 pin header so all the pin slots would be filled on the display but not all of them would be used. Instead, it was a better idea to use only the pins that are going to be used on the display and run the necessary lines only. It allows room to be saved on the actual PCB for the final run.

Since the regulators are taking up the most room on the actual board there needs to be anyways that can be used to save room in the end. If the screen were to be placed on the actual PCB too it would also take up unnecessary room where other components could be instead. Running lead lines for the display fixes this main issue, the only other issue is making sure a pin line is not missed for the display to work properly.

ESP 8266 Pin # / Type	Button #	
16 – GPIO4	1	
18 – GPIO9	2	
19 – GPIO10	3	
17 – VDDPST, Digital Power Supply 1.8-3.6V	All buttons	
Table 9, Push Button Pin Connections		

All the buttons will be tied to the set GPIO pin numbers. When a button is pressed it will draw a voltage from the ESP 8266 pin 17 and take the voltage in tied through the connected GPIO line which will allow the system to read the set input given to interact with the interface for the tuner. The buttons will mainly be used for the user to do directional interactions with the interface in this method. Each button will also have a  $1k\Omega$  resistor tied to them.

ESP 8266 Pin # / Type	Frequency in Pin #
6 – TOUT, ADC	1
33 – GND	2
14 – GPIO2	Buzzer
Table 10 Frequency Device Pin Connecte	

Table 10, Frequency Device Pin Connects

The last pin headers are the 2 pins that are going to connect the Piezo vibration sensor and the audio jack. Even thought they are two different 1x2 pin headers both pin lines number one are going to run into the ESP 8266 pin 6 which is used for all frequency measurements that will be read from the instrument when the tuner is pressed up against the tuning knobs picking up the string's vibration. The audio jack acts as a more precise way for measuring the vibrations. It has the same approach where the tuner will be pressed up against the tuning peg but will take the readings through the  $\frac{1}{4}$ " jack to tell the tuner how much it needs to tune.

# 17.0 Project Summary – Hardware

A large amount of the time for the hardware side was researching proper parts and part acquisition for the project. It came down to what was mainly needed to achieve the end objective goals and determining what was going to be the best approach. There were a few ways to going about right component choice and it was more of a group effort to figure out what should be used and what worked well for other members in the group. Most of the tasks were divided off into split group objectives. The hardware side was in charge of most of the physical components that were going to be used in the system and integrating them together to have a finished form. Only a few parts were managed by the software side which was mainly the ESP 8266.

There was a fair amount of second guessing ourselves and where somethings needed further research before moving on to the next step. If both the software side and hardware side were out of sync with each other certain processes started to slow down and would take more unnecessary time to resolve when there could be an easier solution to the answer than what was already being thought of.

Its not to say that the software side did not need the hardware components because they needed a good amount of the components to do the actual software testing on them to make sure they would work properly for them. Some of the main parts were mainly the screen and motor for the system testing. There were other side components tested too

like the vibration sensor to see if it would pick up the necessary frequencies for instrument testing. After most part acquisition was completed and out of the way it came down to tying everything together in a schematic and forming a PCB layout.

There were definitely issues with supply chain and ordering certain parts for testing purposes, it also limited what was either originally going to be used for some things, some examples were the regulators and the motor choices being constantly changed. Towards the end most of the things that needed to be accomplished or what was at least wanted. The plan was to end with a prototype PCB by the end of the semester so there would be less time lost when it comes to finishing the final design in the last semester. The only thing that we fell behind on was having a pre running prototype or the more makeshift version to see all the parts working together, but that will be starting first thing for the next semester. We know that our components work but have not been fully integrated with all the pieces together to have a partial working system. That was one of the big goals that we wanted to end this semester with, but we were at least able to get relatively close to that end goal and have a PCB design to start with.

# 18.0 Prototype Testing

## 18.1 Prototype Testing Beginning Notes

At the time of writing this document, we are still doing further research on parts, interfaces, and individual components to potentially use. As such, this caveat is included in all subsections as the parts mentioned in this document are subject to change due to manufacturing constraints, shipping delays, overall part availability, and final determination of usage based on the technical research done on these or other parts.

The testing procedures were not specifically written beforehand, and as such, are based on a trial-and-error methodology that is primarily used to determine compatibility and proof-of-concept prototyping. For the sections beyond the ESP8266 section below, it is assumed that the device has been properly set up with use on the Arduino IDE platform and can successfully communicate via the USB connection to be able to upload the testing software onto the board for use, therefore no additional setup beyond testing will be explained.

### 18.2 Prototype Component Testing

### 18.2.1 ESP8266 Testing

The MCU that was chosen has been researched and tested by all team members, across various meetings in order to determine whether or not this MCU would be the choice for our project. At the time of writing this document, it was determined and agreed upon by all of the members in Group 42 that the ESP8266 would be utilized as the center of

operations for our Pick Pocket Tuner. The testing methods employed for this device, due to parts constraints, availability, and time, were simple.

We determined that the core components of our project (i.e. motor, LCD, and piezo sensor) were able to be interfaced through the available number of pins, and communication methods (SPI, UART, etc) available on the MCU. Through further technical research we additionally determined that an external Analog to Digital Converter is likely to not be necessary and will be further tested with the piezo sensor. This device, since it was already connected to a prototyping board, all we did was connect the pins used as needed, and/or connected the board/pins to a breadboard to then use Dupont jumper cables as needed for the necessary wiring.

Additionally, we tested the ESP8266 with both a Windows based machine and Mac-OS based machine and determined that due to the Arduino IDE framework/platform, this resulted in the MCU being platform independent and able to be programmed by either operating system, as long as the correct drivers and libraries were installed correctly as it was discussed in the Prototype Construction ESP8266 section.

### 18.2.2 Piezo Sensor and Filter Testing

The Piezo sensors that were chosen were tested primarily by Team Members Paul Grayford, and Luis Vargas. Since it wasn't immediately clear which piezo sensors would be needed, the team procured a Snark ST-8 Super Tight Clip On Tuner to disassemble, in an attempt to reverse engineer the method in which this device operates. This Snark ST-8 operates using a silicone-like covered clip that would be placed on the headstock of a stringed instrument, like a guitar, and then would pick up on the vibration waves carried from the instrument to then display whether the string strummed is in correctly in tune or not. The waves would travel from the headstock to the silicone clip, then through a ball-and-socket joint made of similar silicone/plastic material, and then through the ST-8 housing where it would be picked up by the sensor that would transmit the information on to determine the tuning. Knowing this, we disassembled the ST-8, and determined that the sensor used by the ST-8 is a ceramic disc piezo sensor. We utilized this information as encouragement that the disc sensor that we already had would likely be the correct choice but kept the option for utilizing the polymer film sensor as well just in case.

In both the piezo disc and the film sensor, we had to solder on some longer wires to be able to use as leads so that they may not only fit the breadboard, but also reach it to begin with as the leads that were soldered on during manufacturing were insufficient in length and thickness to be able to be used appropriately during testing. The testing of each sensor was initially carried out in a manner to determine if they were operational, then to determine how the analog input of the ESP8266 would read the information generated by the sensor, then how the sensitive the sensor itself would be based on testing methods.

The operational tests of the sensors were simple, we used a circuit with a resistor of  $1M\Omega$  between the positive lead of the sensor and ground to attenuate the generated signal, and then connected this into the analog input pin, A0, of the MCU board, with the negative

terminal of the sensor into ground with a ground pin from the MCU board into the breadboard to complete the circuit. Once this was done, we initialized the Arduino IDE, and utilized the sketch example "Knock", which is included with the Arduino IDE, but also describes how to set up the analog sensor so that the program is able to recognize the input from it. Following this, the Knock program was compiled and uploaded onto the MCU so that we could begin testing of the sensors.

Once the IDE informed us that the upload completed successfully, we opened up the Serial Plotter that is a part of the Arduino IDE, and we noticed a single line in a graph that would greet us whenever we ran this program. In doing so, we then began to test the sensor by ensuring that it was laying flat upon a wooden desk/table and we would knock on the table at varying forces, and repeated this process for both the Piezo disc and film sensors. From this we determined that the disc sensor would be optimal in detecting the vibrations from the stringed instrument, since the film piezo requires that the film itself vibrate/resonate for it to detect the necessary information, so it would not be used.

For the next test of the piezo sensor chosen, we separated the main housing of the ST-8 from the clip and utilized the ball-and-socket joint with the clip to simulate a string vibration to see if the sensor/MCU combo would be able to pick up on the signal at all. To do this, we took the clip and covered an iPhone XS earpiece speaker and used the YouTube app to play a series of tones at different frequencies, 440Hz, 1000Hz, and 323Hz. Once those frequencies were playing, the ball end of the stem attached to the clip that is then attached to the iPhone XS speaker, is placed on top of the sensor as the Knock program is still running to see if we would be able to detect the tone from the frequency as it travels through a different medium.

This test proved to be successful, and we were able to see in the Serial Plotter that the different frequencies on the tones generated different analog inputs on through the sensor, which meant we were in the right direction. However, it was at this point that we also noticed that the sensor was always introducing some sort of noise into the signal, and we devised a simple filter to try and attenuate that noise from the sensor into the Analog input of the MCU.

Using the filter mentioned in the previous section and repeating these two tests, we determined that the noise introduced was reduced, and the analog signal read by the analog pin was not adversely affected. To solidify our initial findings, we utilized an oscilloscope to determine whether the piezo sensor was transmitting the correct frequency into the analog input, and we found that immediately after the sensor we were matching the frequency from the tone. This same test, we repeated using two channels to test both the signal coming off of the piezo sensor directly and then after the filter, as a comparison, and the resulting frequency reading at both ends was matching to the tone being generated. Figure 21, Figure 22, and Figure 23 below, serve to demonstrate the prototyping breadboard set up, before including the motor for movement, and the oscilloscope response when reading from the piezo lead wires, and then after the filter is added.

This testing done on the piezo sensor the base point for the testing for the rest of the devices used. Since we are able to accurately read a vibration at a specified frequency, and correctly transmit that information to the MCU via the analog pin, we decided to move on to not only testing the other devices, but further refining this basic operation of the piezo sensor in our prototype.

While completing further technical research, the general consensus was determined to be that we should add a second piezo sensor to our prototype/device. Initially, while using one sensor we determined that the sensitivity while knocking on a wooden table, and through the iPhone XS 'test' employed previously yielded satisfactory results. However, once we procured the Jowoom Guitar tuner, and subsequently disassembled the product, one of the immediate things that stood out to us is that the Jowoom employs the use of two piezoelectric disc sensors simultaneously, however they are connected in parallel as seen in Figure 20 below.



Figure 33, Jowoom Automatic Tuner (deconstructed) showing two piezoelectric sensors in parallel

Without being able to compare it to other in-market competitors, like the Roadie3 Tuner, to see if these other competitors employed this parallel-piezo design the team decided to

implement this piezo sensor set up to see how the sensitivity and accuracy would be affected by connecting the two in parallel.

Through further technical research, our group determined that the implementation of the piezo sensors in parallel, without being able to 100% confirm with the manufacturer of the Jowoom tuner, was a design decision to produce more consistent results. As can be seen in Figure 20 above, there is one piezo sensor directly attached to the housing of the Jowoom device, and another to the PCB, when noticing this specifically it led us to look into "seeing" the piezo sensor as a device akin to an electric guitar's pickups, where wiring pickups in parallel is a fairly standard procedure since you can modulate the incoming signal from the strings using a switch and the pickups on the guitar to obtain a different sound. The concept of adding a secondary piezo sensor is similar to this, when considering the piezo sensors as pickups rather than the individual electric sensors that they are. So, this reasoning leads us to believe that the integration of a secondary piezo sensor would assist in further isolating the incoming analog signal while also boosting the necessary sensitivity so that we are able to take the analog input from the piezo sensors and obtain a more accurate representation of the incoming frequency when repeating the iPhone XS "test" that previously yielded satisfactory results.

As of November 15, 2021 we are waiting for additional Piezo sensors so that we could test additional configurations of wiring more sensors in parallel, or with other components (i.e. capacitors, and/or resistors) in between to further examine the effects that these configurations would have on the analog signal incoming into our analog input for the MCU and the limitations of the MCU when dealing with the changing signal generated.

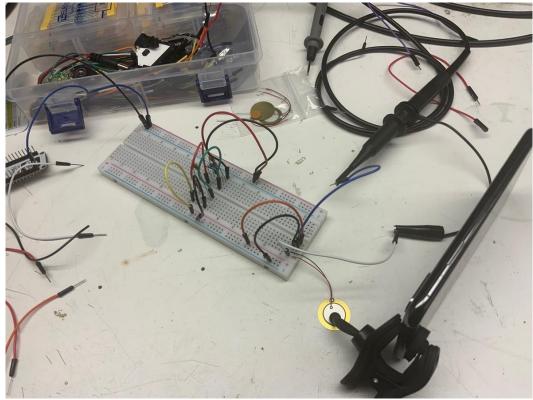


Figure 34, Breadboard Prototype Demonstrating iPhone Speaker Vibration/Tone Test

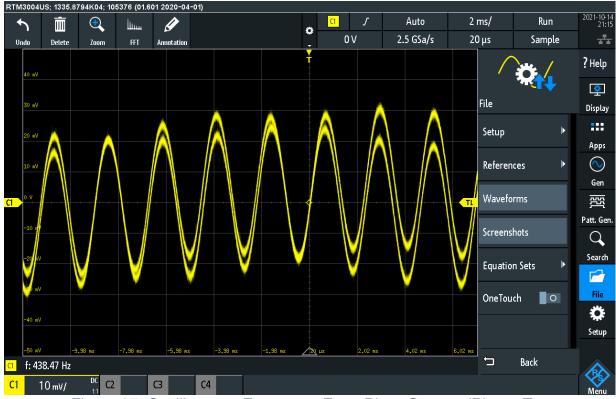


Figure 35, Oscilloscope Frequency From Piezo Sensor, iPhone Test

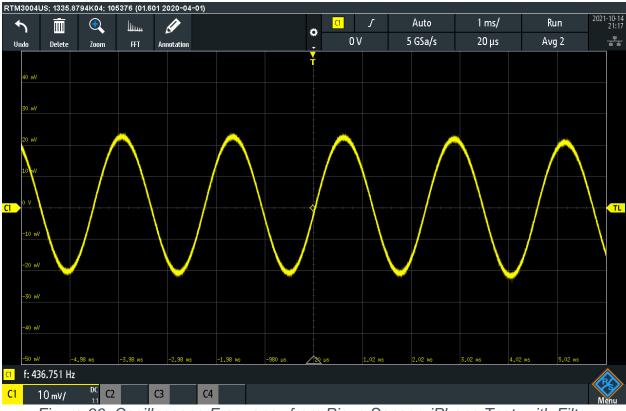


Figure 36, Oscilloscope Frequency from Piezo Sensor, iPhone Test, with Filter

### 18.2.3 Motor Testing

The testing of the motor, at the time of writing this document, is very similar to that of the Piezo Sensor. It follows a step-by-step sequencing of attempting to determine the operational capacity, then introduction of variability to determine if the device is adequate for our final operational purposes. To test the motor/driver, aka motor, similarly to the piezo, we utilized the Arduino IDE provided example of "stepper\_oneRevolution" program, and modified it slightly to match the operational capacity of the motor so that the steps for one revolution and speed in the program matched the specifications of our motor, and we also changed the pins used in the program to those we would use on the MCU.

After doing so, we wired up the motor driver board to the appropriate pins so that in the driver PCB pins IN1, IN2, IN3, IN4 correspond with physical pins D1, D2, D5, D6 on the MCU prototyping board. Once done, we added the necessary power using the DC-IN board mentioned earlier and attempted to compile the program so that we could get the motor turning. After some debugging of the program, due to non-matching GPIO pins in the code, we were able to get it turning. The testing of the operational capacity of the motor was a success.

It was at this point that we would attempt to run the device again, however we would attach the 3D Printed Peg-Winder onto the stem to see if we could turn a tuning peg on a guitar. After completing this test, we determined that this specific motor, the 2BYJ-48, does not produce enough torque to turn the tuning peg thus we would have to do more technical research in order to choose a motor that would work. However, with these findings, we decided that it would be beneficial to test the integration of the motor into the prototype so that we can test to see if the ESP8266 can transmit the information so that we can turn the motor based on whether the sensor detects a knock, or a tone.

So, we first set up the testing environment first so that the filtered sensor inputs into the analog input of the MCU, and with the sensor lying flat on the table to sense a knock on the wooden table. In doing so, we also wired up the motor so that it could also be used when the analog input is recognized by the MCU the motor would rotate. We modified the existing code and integrated the working parts of the "Knock" Arduino example so that we could turn our motor head whenever there was a knock sensed. After compiling and uploading the code, we opened the Serial Plotter and began knocking the table to find if the integration of the two devices worked, and it did. The motor moved whenever a knock was sensed from the table.

Building upon this success, we took the sensor set-up and modified it so that it would now resemble the testing setup for the detecting the tone generated from the iPhone speaker. Using this set-up, we began playing a 440Hz tone and placed the ball-and-socket ball end on the sensor and saw that the sensor was picking up the tone successfully, and the motor was moving consistently since the vibration was non-stop. This successful test demonstrated to us that the integration of the three devices, so far, was successful. From here, however, since this motor was not adequate to turn the device, it was determined that further testing on the motor would be suspended since we would need to replace it with a different one.

As of November 18, 2021 we have received the new motor, the DRobot FIT0441, that we intend to utilize for the next step in our prototyping and testing. Once we are able to determine the necessary code to be able to interface with the motor through the ESP 8266 MCU, we will attempt to some testing with the 3D Printed Guitar Peg Winder attached to see how fast we are able to get the motor to turn a guitar tuning peg, and with how much accuracy we can adjust the motor so that we can get fine-tuner control of the tuning peg on the guitar.

### 18.2.4 LCD Display Testing

The testing of our LCD Display, at the time of writing this document, is very similar to that of the Piezo sensor. We essentially attempted to follow a step-by-step sequencing to determine the operational capacity of the procured piece. This was done in order to ensure that the LCD that we received was not a dead-on-arrival piece. To test the device, successfully, we had to solder on the header pins onto the device in order for us to be able to interface with it through the ESP8266 and the Arduino software. Once the header pins were soldered on successfully, it was noticed that the LCD Display was able to

accept a voltage input of 3V to 5V DC and was capable of outputting a regulated voltage of 3.3V, thus reducing the need for an added voltage regulator in the overall project by one.

To really begin testing the LCD, we used the guide that Adafruit has for wiring it to an Arduino development board and made the necessary pin adjustments in order for our ESP8266 development board to connect and interface with the display via SPI. Initially, the wiring diagrams were seemingly correct and were properly implemented when conducting the previously mentioned adjustments, however there was no backlight after connecting the correct DC voltage to the appropriate pins. Thinking that this may be due to the controller for the LCD not being directed to utilize the supplied voltages to turn on, we proceeded to attempt the connection of the two devices through the Arduino software using the libraries for this LCD display supplied by Adafruit for use with the Arduino IDE. These libraries, "Adafruit\_GFX", "Adafruite BusIO", "Adafruit Zero DMA", "Adafruit ST7735 and ST7789", "Adafruit SPIFlash", and "SdFat – Adafruit Fork", are the ones that would initially be used to try to interface the ESP8266 MCU with the LCD display through the ST7789 TFT driver that this LCD display uses.

Further following the supplied Adafruit guide for testing this LCD, we attempted to utilize an Arduino IDE example provided by the "Adafruit ST7735 and ST7789" library called "graphicstest". This example driver code needed to be updated/modified according to the specific display and display driver that was being used, since this is a general-use code provided by the manufacturer. Once this code was updated, we ran into significant issues trying where the compiling of the program would fail, and we were unable to determine the operational capacity of the LCD display. In order to determine the source of the issue so that we could come to a solution, we began testing each and every one of the libraries being used in the "graphicstest" example code and determined that the very library that provided the example, was causing compilation errors on a MacBook Air.

Further testing was done on the Arduino environment on another computer, but the same errors were run into when trying to flash the example code to the processor. These issues led to the switching of testing the LCD screen on the uPyCraft environment with a self-created test code in MicroPython. The SPI connection was researched and implemented based off similar displays and processors. However, further issues were run into when testing the display on the new environment.

The SPI connection was successfully created, but unfortunately the test code was not drawing onto the display correctly. Further research is being conducted at the moment to iron out all the issues as the tuner is heavily reliant on visual feedback to the users. Research will include wiring diagrams of the similar ESP32 processor along with comparing the python code with the example C++ code from Arduino. Code comparison will help iron out any display issues explicitly as the flow of code will be the same despite the difference in languages used to create the code.

## 18.2.5 FFT Input Testing

Alongside testing the input piezo sensor, we will also test the implementation of the fast Fourier transform on the input data sent from the sensor. We will then display the computed frequency onto the display once they are all connected. The procedure would be the same as the testing of the piezo sensor. However, we will have a program sampling the analog voltage input and performing the transform to test the accuracy of the sensor and the accuracy of the written code. This would also be a challenge as we are creating this code in Python as opposed to Arduino, which was what we were originally testing the senor with prior.

## 18.2.6 USB-C Charging Circuit and Battery Testing

The testing of our USB-C Charging Circuit and battery, at the time of writing this document, was more for a verification of operational capacity to determine if either of the two devices were dead-on-arrival. Further integration into the system will determine the runtime on a single charge, the time needed to charge the battery with both a 100mA charging current as well as with a 500mA charging current from 0% to 100%, amongst other tests. Currently, we have determined that the battery and charging circuit both work since we are able to connect the battery and charge it and determine that it has been charged with an external voltmeter used.

Additionally, since the charging circuit we are prototyping with has two data line pads, D+ and D-, it is our group's intent to utilize these pads during testing to try and determine the current status of the battery, i.e. whether it is charged or not and the percentage of battery remaining on the device. The reason for testing on both the charging circuit and the battery not having begun is that there was insufficient amount of time between the time between choosing, ordering, and receiving the parts and performing adequate testing. However, the inclusion of this section is determined to be necessary due to the importance of demonstrating that progress in prototyping the final project is being made and that considerations for testing/implementation is being conducted in an efficient and timely manner.

### 18.3 Next Prototype Testing Steps and Ending Notes

At the time of writing this document, the next testing and integration to be done for the prototyping is determining how to analyze the analog signal being output from the piezo, through the filter, and into the analog input pin and converting it into a frequency signal that we can then use to be able build the rest of the software component of the Pick Pocket Tuner. With some preliminary technical research done, we have determined that we would need to use the Fast-Fourier Transform to be able to convert the signal to the frequency to then be able to use it accordingly. From there, the next testing would be to determine if the updated motor can turn the tuning pegs as needed, and with sufficient force and speed, so that we can begin integrating software functions to accomplish the activation of the motor based on the frequency that is being 'read' at the sensor.

Once these basics are completed, the more rigorous and detailed testing of the overall prototype begins since at that point the members of Group 42 will be able to begin writing the software needed to meet the requirement specifications for all our defined, and yet-to-be defined features/functions of the Pick Pocket Tuner.

# 19.0 Software Block Diagram

The main purpose of the software component for the project is to take in inputs from both the user and the sensor. This will provide a created algorithm with the desired string tuning frequency and what frequency the string is currently tuned to. This will allow the algorithm to detect the difference between the two frequencies and then turn the motor accordingly to wind the tuning peg to the user desired frequency. The software will also allow the user to save and reuse frequency values. The software will also communicate with the display to show any measured inputs and an interface for easier access to options for the user to select their input.

Our software will have preset frequency values for the user to choose from when tuning strings along with past used frequencies. The program will display to the user the frequencies in order of most used for convenience. This will also save some time since our users will most likely be re tuning instruments to their previous frequency with our project. After the frequency is selected, the software will prompt the user to pluck the string that they are tuning, and our sensor will pick up its frequency with a fast Fourier transform to save computation time.

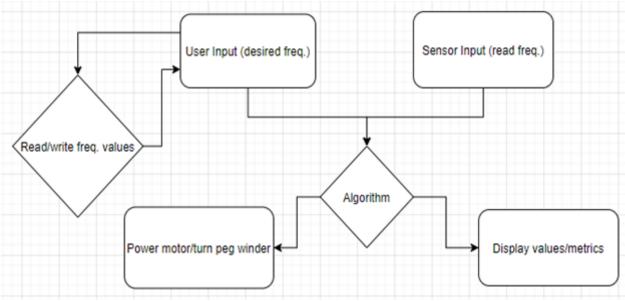


Figure 37, Software Block Diagram

# 20.0 Algorithm

Using data science, we will find a correlation between a string's gauge and the torque needed to tune that string,  $C_{guage}$ . This correlation will then be translated to voltage supplied to the motor to turn the string to the correct frequency dependent of the gauge. We will also use this data and test our motor to find the relationship between voltage supplied to the motor and the change in frequency of the string that was winded,  $C_{factor}$ . This will allow our algorithm to scale with many string gauges.

The process for acquiring the constant,  $C_{guage}$ , is to study the relationship between torque needed to turn the string based on the certain string's gauge. With this torque relationship between gauges, we can then translate that into a factor of voltage needed to send to the stepper motor for the certain gauge. Further researching and testing will have to be done on the stepper motor to find out the steps needed for a certain amount of torque applied to the string peg. (Table of data points/plot of data points to be inserted)

The process for acquiring the constant,  $C_{factor}$ , will be plotting steps sent to the stepper motor against the change in frequency on the string being winded. Using this data and plotting the results will help find a correlation between the two values and that correlation will present a constant that is present within the points and will allow more accurate calculations in the algorithm. **(Table of data points/plot of data points to be inserted)** 

The algorithm will have two inputs,  $f_{sensor}$ ,  $f_{user_input}$ , and use them alongside the defined constants/correlations,  $C_{guage}$ ,  $C_{factor}$ , to output the correct voltage to the motor to turn the peg winder so the string reads the desired frequency,  $V_{motor_output}$ . The function created is the difference between the desired frequency and the frequency of the string that was read by the sensor. This difference is the main factor of how far we will have to turn our peg winder to match the desired frequency. This difference is then multiplied by the constant and correlation defined to create the correct voltage to send to the motor/motor driver based on the string's gauge and how much torque is needed to correct the string's frequency.

 $V_{motor\_output} = (f_{user\_input} - f_{sensor}) \times C_{guage} \times C_{factor}$ Equation 1. Algorithm for Stepper Motor Output

# 21.0 Software Features/Functions

### 21.1 Fast Fourier Transform

When reading the filtered analog voltage from our vibrational sensor, we will have to convert it to the frequency domain to send to the algorithm for accurate tuning. The input from the vibrational sensor is in the time domain and a Fourier transform would convert that reading from the time domain to the frequency domain. However, the discrete Fourier transform has a time complexity of  $O(n^2)$  where *n* is the size of the input data being read. The fast Fourier transform will be used in our project as it has a time complexity of

O(nlogn) which is significantly faster and will save computation time when tuning each string. This transform will help satisfy our multiple time-restraint technical requirements with fast computation at each string. During the tuning process, the sensor will sample the readings from the plucked string over a certain amount of time. After the reading is complete, we will perform the fast Fourier transform on the wave and obtain the frequency to send over to the main algorithm to finish tuning the string.

## 21.2 Tuning a New String

The Pick Pocket Tuner will have an option for tuning a brand-new string. This means that when a string is being replaced, the user will select an option for tuning a new string. When the user selects this option, it will prompt the guitar player to select the string they are replacing on the interface, and then select a "go" option for when the string is ready to be wound. The motor will automatically start to turn, bringing the string up to tension. The device will then ask the user to start plucking the string of the guitar. As the string gets tighter, the device will be able to read the frequency with the sensor or the output jack and tune the string in one easy step. The goal is to be able to complete this process in under a minute. The challenge will come with the quality of the electrical components, as well as with the quality of the software behind this option. The way that this code is written is a crucial part in how fast and accurately the tuner can tine the string. This feature will be required, because the competition does not have a setting like this, thus causing our product to have a competitive edge.

When this option is selected, the software will turn the peg winder a certain amount without prompting to get close to the lowest frequency among the six strings. This amount will be calculated with further testing and researching. We will have to find the average frequency of a newly installed string from a sample of users, and we will use that average frequency to calculate the difference between this and the resulting low frequency. After the string is brought to the low frequency, the software will work as normal and prompt the user for the desired frequency of the string and tune it. **(Table of sample data, finding the average to be inserted)** 

Making this process as automatic as possible is key when trying to stay under roughly the same time frame when tuning a guitar with six new strings as opposed to a guitar with six strings that are only slightly loosened over time. This will provide ease-of-use for all occasions and reasons to tune multiple strings on a guitar and make our product more valuable.

### 21.3 Display Interface

The interface for the device is where some artistic liberty can be taken. The interface will be constructed in the later part of the project. The group wants to make sure that user input with the interface works before the display is modern looking and streamlined. However, this will be a fun part of the project, as it allows the device to have a personality, and has the potential to be an effective selling point to a customer. Most interfaces today follow a simplistic approach, using neutral colors, and following a color scheme. Even

though this does not seem to have too much of an importance on the project, it can really elevate the user's experience and make it more enjoyable to use. Our style will be determined later into the project, and inspiration will be gathered from devices such as the Roadie3, smartphones, and other small handheld appliances with screens on them.

Creating this seamless and modern looking display will be challenging as we plan to have five buttons for the user to interact with our device. These buttons will be four directional buttons with a selection button as the fifth. The interface will play to these directional buttons to create simplistic menu changes and user selections for choosing modes of string tuning and frequency selection. Knowing the button layout before creating the menu hierarchy will play a big role in creating the esthetic ease-of-use display for our users and clients.

Creating a simple interface will also help us achieve our technical requirement of easeof-use display and our timing requirement for tuning all the strings on a guitar. If the user can access the desired frequencies and menus to tune the strings to those frequencies, the faster our device will tune the user's guitar. Our device will also allow the user to save past used frequencies for easier access to later. This will provide even faster access to string tuning as our device will be used mostly for retuning guitars back to the past frequency they were set at as the peg will naturally loosen over time. If we allow for more saved frequencies, then the user will have an easier time with tuning their guitar to multiple sets that they enjoy playing.

The Adafruit graphics library is created for Arduino but can also be used in Python for easy graphics creation. This is essential to our project as the display driver library is well programmed and our group will have access to many high-level graphic drawing functions to create our simple and ease-of-use interface. Further testing with the library will be conducted to help create a seamless interface and to find the limitations of the library itself with what graphics can be created on the display.

### 21.4 Tuning Libraries (Stretch Goal)

One of the stretch goals that was implemented into our project is to create different tuning libraries, to be able to accommodate a wide range of guitar players of varying skill levels. The purpose of this is to be able to store a preferred tuning of an electric guitar on the Pick Pocket Tuner's internal memory so that the user will to be able to change from standard tuning (EADGBe) to an alternate tuning, for example DADGAD, with ease. Additionally, this feature would allow the user to store a preferred tuning for use with different guitars, or even different use cases like performances, recording, or just practicing.

## 21.5 Tuning Other Instruments (Stretch Goal)

An additional stretch goal that we would like to be implemented, is to have the capability to tune different stringed instruments, including but not limited to banjos, Ukuleles, Cello,

Violin, etc.. The software needed for these other instruments would change slightly since different frequencies would be necessary to be read due to the pitch changes based on the size/length of the instrument, and the torque output to the tuning pegs would also need to change based on the type of strings used. What this means, for example, is that tuning a string to a G note on a guitar requires "x" ft. Lbs. of torque, meanwhile tuning a ukulele to that same G would require "y" ft. Lbs. of torque.

## 21.6 Programming Language(s)

The programming language(s) to be used and implemented are still in a research/to-bedetermined stage due to still picking out the necessary parts, and testing for the parts as they are acquired. As it currently stands, the Piezoelectric Sensor (a.k.a. PES) and most other parts would be able to be utilized and interfaced via the Arduino environment using the Arduino IDE, however our group is not sure, and undecided on how the final software design will look like so the process will likely change through further technical investigation and parts acquisitions.

However, as further development and investigations occur, the members of Group 42 are able to make informed decisions on the software development process as needed. These decisions, impacting what languages or methods to use for software implementation, are sometimes simple determinations made for the group by the algorithm that we wish to employ itself, as is the case with the fast Fourier transform. That algorithm itself is able to be implemented with different languages, however one of the most efficient and 'easiest' to implement with is in Python.

Additionally, since we know we are utilizing the Arduino IDE for prototyping, we know that both the Arduino-based framework language will be used, as well as C/C++, especially since the Arduino-based framework language is directly based off of C/C++. As stated previously, we are not limiting ourselves to any one set of languages, at the writing of this document, since we are still in the early stages of development primarily since during the integration of all the different components with the ESP8266 and other functions may lead to changes in our choices.

### 21.7 Programming/Software Libraries

The utilization of any specific library or software is still undecided at this moment. During the prototyping stages of our project design is where we're likely to decide on what to specifically use, however it is known that there are various libraries in existence already that would not only aid in facilitating the mathematical processes for analyzing the frequencies but would aid in the integration and interfacing of the hardware that we are to use.

At this time, we are employing the use of Python's SciKit and Numpy libraries, in order to complete the Fast Fourier Transform. Additionally, we are utilizing some Arduino libraries

in conjunction with the listed C/C++ libraries to accomplish some of the fine control that is necessary for the motor, and in order to interface with the display correctly.

These libraries in the Arduino/C/C++ suite are Stepper.h, math.h, Adafruit\_GFX.h, Adafruit\_ST7789.h, Adafruit\_ST7736.h, and SPI.h. The one other library/software package that might end up being used is MicroPython or CPython, where these two libraries are optimized for operating on a microcontroller as they are lightweight and quick in program execution. Beyond what has already been said, through further integration tests, and frankly, trial-and-error, we will determine what other software libraries are to be used.

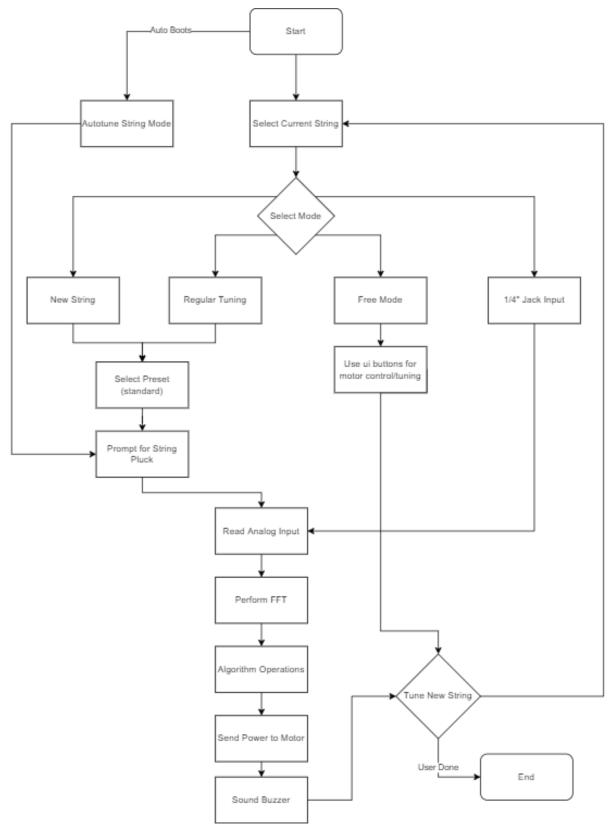


Figure 38, UI/UX Software Hierarchy/Design

# 22.0 UI/UX Software Hierarchy and Design

#### 22.1 Software Hierarchy Description

In Error! Reference source not found. above, we have decided to visually mark how t he overall UI/UX Software Hierarchy is loosely intended to work. The intended method of interfacing between the Pick Pocket Tuner and the end-user is dependent on the utilization of buttons that are on the device itself and the software necessary to receive the inputs from said buttons. Through all this, the device displays all the information back through a GUI that is designed by the members of Group 42 in an attempt to relay the most information in an accessible and readable manner. The LCD display software hierarchy/design will be discussed in a different section; however it is relevant to mention at this juncture since almost all of the feedback of the tuner and interfacing will depend on the performance and implementation of the LCD display. Additionally, it is worth mentioning that the assumption for user inputs to the device are performed strictly through the buttons on the device as there is no other input required of the user. At the moment, this implementation allows for further refining and addition of other elements to facilitate in providing a positive, intuitive user interface. With this statement, however, since this is a work in progress, all of the elements described and defined here are subject to change pending testing and integration.

In discussing the specific flow this diagram, we have determined this pathing as it is relatively self-explanatory. Once the device boots up, at the Start block, the software package will automatically load the method that would enable the automatic tuning to occur in order to tune the guitar to E Standard. Then, the UI will prompt the user for input to tune the correct string and thus proceed through the tuning process. Next, if the device gets a to-be-determined button combination input, this would allow the user to change the mode of operation to either Direct Input using the ¼" input jack, Free Mode, New String, or Regular (a.k.a. Automatic) tuning. Once the mode of operation is chosen, the display will proceed through the necessary software steps to accomplish the tuning process, and loop back to select the string, in other words move the Pick Pocket Tuner, to the next string to tune, or if the user is done with all the strings, to the end of the process.

#### 22.2 Software Tuning

The process of tuning a string on the software side requires communication between the piezo sensor, the display, and the ESP8266. When the user is prompted to pluck the string, the software will read in the input analog voltage from the piezo sensor over a determined duration. The duration of the analog reading is currently in the process of being tested for maximum accuracy. This duration must be accurate, but it also must be fast to meet both of our technical requirements of accuracy within 5 cents and a short time duration to tune all strings on the guitar in 3 minutes.

For electric guitars, the ¼" input jack will be used to bypass the piezo sensor due to the guitar's internal circuit. Reading the string frequency from the guitar's circuit will result in a more accurate reading than if the string pluck was read by the piezo sensor. However, the ¼" input jack will send its analog voltage into the same ESP8266 pin resulting in the same steps with tuning an electric guitar. This allows our product to have multiple ways of tuning and allow multiple instruments to be tuned without multiple steps of code for the differing steps.

To test the frequency and accuracy of the fast Fourier transform, we will hook up the piezo sensor to the NodeMCU and create a python program to read in the input. The python program will be run in the uPyCraft environment. The testing of the read frequency will be the same testing when we were testing the sensor itself. However, this time we will perform the transform onto the input sensor values and graph the resulting frequency value for accuracy. The numpy and scipy python libraries will be used to perform the array operations and Fourier transform of the data.

Duration	<b>Test Frequency</b>	<b>Read Frequency</b>	<b>Computation Time</b>
3 s	400 Hz	To be determined	To be determined
5 s	400 Hz	To be determined	To be determined
10 s	400 Hz	To be determined	To be determined
15 s	400 Hz	To be determined	To be determined
20 s	400 Hz	To be determined	To be determined
Table 11 FET Computation Time Based on Duration of Test Fragmann			

Table 11, FFT Computation Time Based on Duration of Test Frequency

The numpy python library is used mostly for their numpy array data structure. This data structure is useful for mathematical operations across whole data arrays. This allows for a faster Fourier transform since the operations are fine tuned to operate over whole arrays. Numpy also provides other mathematical operations which allows for less libraries needed for the mathematical operations that are used in the algorithm.

For the scipy python library, research was conducted to find the library that would perform the transform in the fastest computation time. This is to ensure that our project will spend the least amount of time tuning the guitar. To test these libraries, we created a sine wave with a constant frequency and timed the transform of it across the libraries. The computation time is an average of multiple runs of the same transform onto the same sine wave and is compared in the table below. Ultimately, scipy was chosen as the library moving forward to perform the transform for the input data.

FFT Library	<b>Computation Time</b>	Units
scipy	71	ms
numpy	88	ms
•		

Table 12, Average Computation Time for the FFT Using scipy and numpy

During the specified and researched duration, the input analog voltage values will be stored into a numpy data structure array for faster computation. This array will then be transformed from the time domain with the fast Fourier Transform to convert it into the frequency domain.

To find the right frequency that is being read in, the data array of converted frequencies is combed through to find the value that is greater than 1. Since the frequency should not be changing in the string, if it is greater than 1, then the power of the frequency is highest in this data array and that can be concluded as the resulting frequency of the string.

This input frequency value is then compared to the frequency chosen by the user, which is the desired string frequency. This comparison will result in a difference of frequency values that will be used to calculate the amount of voltage needed to send to the motor which will then turn the peg winder. If the voltage sent to the motor was correct to tune the string to the desired frequency, the buzzer will have voltage sent to it to provide the user feedback. The amount of voltage needed to send to the motor will be tested as it is related to the torque of the winded peg and to the change in frequency onto the tensioned string.

#### 22.3 Software Display

During the tuning process, the display will show the menu options for the user to traverse through with directional buttons. The menu options will be displayed in a hierarchy that can be selected with the selection button. Backwards menu traversing will be made possible with the user holding down the selection button.

Reusing buttons for other actions while traversing through the menu will allow our product to have a simpler design that is not too complicated for the user to understand and use. These will both help result in a faster tuning time and an easier product for all users to use.

After the user has selected their string and desired frequency, the display will then prompt the user to pluck the string. Further iterations of this prompt are desired to be more aesthetically pleasing, such as an image or an animated image. However, after the string is plucked, the display will then show the read frequency, the string being tuned, and the desired frequency. This text will be shown alongside a graphic that shows the range of the tuned string within its sharp/flat frequency.

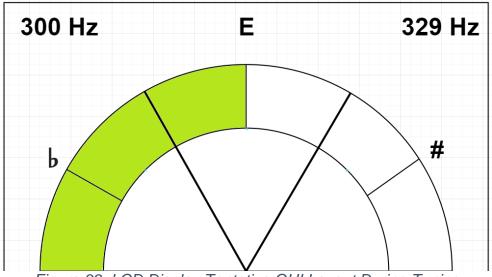


Figure 39, LCD Display Tentative GUI Layout During Tuning

Having the diagram display this graphic shows the user the whole tuning process with a simplistic display with the green bar being the tuned frequency. With the middle peg being the correct and in-pitch frequency. The diagram also displays the flat and sharp frequency placements for comparison. These being on the display also allows for users to have more knowledge in their string frequencies if they are tuning to certain flat and sharp notes compared to the natural frequency.

Using this diagram as opposed to simply displaying the frequency values in text form will result in a more aesthetically pleasing display to the user. This diagram will also work as more interactive feedback, as frequency values are not as well-known while flats and sharps are more relatable information when tuning certain instruments.

This will also show the accuracy of our product's tuning more graphically with the midpoint lines shown within the arc of the flat, natural, and sharp frequencies. Since a big technical and customer requirement is accuracy, this diagram hits all the points of a simplistic, yet effective, design.

For more aesthetic appeal and to have more unique designs, a stretch goal for the display would have graphics during user downtime. This would include the device powering on/off and during the string frequency reading processes. Having these graphics would help bring more appeal to our product as opposed to our competitors and would allow for graphical uniqueness on the market for users to pick from.

Throughout the process of tuning strings and navigating the menu, another stretch goal is for the display will be displaying battery indications. This would preferably be in the top right corner as users are more familiar with that location for any battery indications for handheld devices. This indication will also be useful for users to know if they will need to charge the device before planning any events that our product will be needed for.

This can be implemented with our current recharging circuit as it has two data pads (D+ and D-). We intend to use these pins to communicate the battery percentage/status to the display and further provide the user with knowledge of the device and how much longer it is needing charging.

## 22.4 Handling Flat and Sharp Notes

The purpose of this section is to define and identify a potential issue with how different notes are interpreted by the system in order to display the correct feedback to the user based on the specific pitch of the string that is actively being tuned and the desired pitch that the user wishes. For simplicity, Figure 27 below is what will be used to reference the information to be described here. The content of this section will be explained as if it were a keyboard, however, since this information is based on music theory the same information applies universally across instruments.

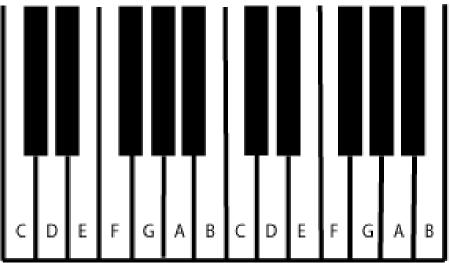


Figure 40, Natural Notes Written on the Keys of a Keyboard

As can be seen above in Figure 27, we can see that the white keys all repeat periodically, from the letters A through G. These seven letters name all the natural notes in music. The black keys in this instance are the remaining 5 notes that are in an octave, these black keys are referred to as sharp or flat corresponding to either the preceding or following letter. When describing a sharp note, like A#, it means that the note A# is one half step higher than the natural note A, and when the note is flat, like Ab, it means that the note Ab is one half step lower than the natural note A. One distinction to be made, which can be seen in the figure above, is that not all natural notes have intermediate steps to go through, like between natural notes E and F, and between B and C, so in this instance when referring to E sharp, E#, it would mean the same as if one were referring to the natural note F since there is only one-half step between the notes E and F, likewise with notes B and C.

Flat Note - Frequency	Natural Note - Frequency	Sharp Note - Frequency
Cb – 246.94 Hz	C – 261.63 Hz	C# - 277.18 Hz
Db – 277.18 Hz	D – 293.66 Hz	D# - 311.13 Hz
Eb – 311.13 Hz	E – 329.63 Hz	E# - 349.23 Hz
Fb – 329.63 Hz	F – 349.23 Hz	F# - 369.99 Hz
Gb – 369.99 Hz	G – 392.00 Hz	G# - 415.30 Hz
Ab – 415.30 Hz	A – 440.00 Hz	A# - 466.16 Hz
Bb – 466.16 Hz	B – 493.88 Hz	B# - 523.25 Hz

Table 13, Flat/Natural/Sharp Frequency Example starting at Middle C

With that brief music theory out of the way, the idea behind how this is intended to be utilized is when specifically determining what tuning a string is in, it is necessary to be able to distinguish whether the tuning is natural, sharp, or flat, and thus be able to relay that information to the user so that it can be used. Since each note has a specific frequency, we can determine an offset for the device to display back to the user whether the note will be flat, natural, or sharp. Typically, a difference in 10-15Hz, either higher or lower, would cause the note to become flat or sharp, as shown in found. Above, when considering starting at what is referred to as 'Middle C'.

From this table it is clearly shown that the range for where a note is determined to be flat or sharp varies. So, between each half step, it would be necessary to find a range so that when it crosses that 10-15 Hz threshold the information relayed to the user would display the note as being sharp, natural, or flat. Similarly, to what was previously stated, this threshold would need to be adjusted and tested in order to fully determine what would be the most appropriate 'stepping' for the frequencies to go through to determine the pitch accurately.

### 22.5 Math for Voltage Sent to Motor

Our currently picked motor has 270 pulses per revolution. This results in 1.33 degrees per turn. Using these measurements, we can relate the torque from the resulting turn. This torque can be then further related to the tension brought onto the string if it was being winded by the peg winder driven by the motor turning it. Further testing on a guitar string with this motor is needed to find an ideal variable between the voltage sent to the motor and the amount of frequency gained/lost.

This is needed as communicating with the motor for winding the peg will be the number of steps, having the right relation between frequency and steps will result in the utmost accuracy. Having this relation can then be built on with further stretch goals of scaling that mathematical factor with string thickness, guitar length, and coating of the string. However, having average values for these mathematical relationships is ideal as to not overload the user with inputting needless measurements such as string composition, string thickness, etc.

We will continue to further research the center point of averaging out values to have our algorithm provide the right number of steps to be within our 5 cents accuracy technical requirement when tuning. Multiple tests on multiple different types of strings and instruments are needed to gain this accuracy.

Below is the relation between degrees per step and pulses per revolution. This is needed as the more pulses the motor can achieve per revolution, the more precise of a degree each step is. With our motor being precise and having 1.33 degrees per step, it is the ideal choice for our technical requirement and accuracy of fine tuning any string or most instruments.

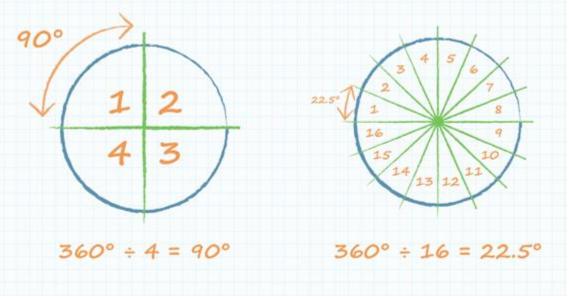


Figure 41, Relation Between Degrees Per Step and Pulses Per Revolution

### 22.6 New String Mode

This mode of operation, at first, would be limited to just guitar and bass, however could be expanded to include additional stringed instruments determined by testing and further refining of the software. Since we have identified the rudimentary frequency threshold to determine whether the string is flat, sharp, or natural one of the first methods for utilization and improving the UI/UX with the Pick Pocket Tuner is our implementation of a New String mode.

The intended method of accomplishing this would give us the capabilities of stringing a guitar faster than a human, and faster than the competitors already in the market. The manner in which the software method would accomplish this would take into account octaves on a guitar/bass, and music theory.

As seen in Figure 27, each note repeats, which means that when the note interval repeats are that it's changing octave. This means that each frequency also repeats by a specific factor, the distinguishing feature between a higher/lower pitch is whether or not the frequency of that same note is doubled or halved.

For example, if a C note at 65.4Hz, one octave higher means the frequency doubles to 130.8Hz, and one octave lower means that the frequency halves to 32.7Hz. Table X below shows this for other notes to further exemplify this. When each octave moves from one to the next, the pitch is what changes, and since the pitch determines the sound we hear as either being high or low, it corresponds to the frequency.

Octave Lower - Frequency	Note - Frequency	Octave Higher - Frequency
A – 220.00 Hz	A – 440.00 Hz	A – 880.00 Hz
B – 246.94 Hz	B – 493.88 Hz	B – 987.77 Hz
C – 261.63 Hz	C – 523.25 Hz	C – 1046.50 Hz
D – 293.66 Hz	D – 587.33 Hz	D – 1174.66 Hz
E – 329.63 Hz	E – 659.25 Hz	E – 1318.51 Hz
F – 349.23 Hz	F – 698.46 Hz	F – 1396.91 Hz
G – 392.00 Hz	G – 783.99 Hz	G – 1567.98 Hz

Table 14, Frequency Examples of One Higher and Lower Octave For Each Frequency

We can use this information to set an arbitrary 'new string mode' note to achieve with the correct octave, to not over tighten the string causing the string to snap, and conversely to not leave the string so loose so that the vibrations won't be picked up by the tuner due to low frequencies.

A good middle ground that has been discussed, proposed, and is subject to testing, which is when in the "new string mode" we are to guide the tuner to wind a string to one or two steps below the E standard tuning, during the initial winding. What this would look like would be that if the string is meant to be tuned to G, this mode of operation would wind the string to E and then ask the user to move to the next string, the octave and thus frequency which is tuned to would be determined by which string is being tuned.

When doing this, it would allow the guitar body and other strings to ease into the tension that is required to tune it to E Standard and help in mitigating damage. While undergoing this process, the UI/UX would prompt the user to either change strings or to continue plucking the current string until the preset tuning is achieved. The following table visually demonstrates the tunings which would be produced given the one or two steps below E Standard.

E Standard Tuning	1 Step Lower ( D Standard)	2 Steps Lower ( C Standard )
Low E	Low D	Low C
А	G	F
D	С	A#
G	F	D#
В	A	G
High E	High D	С

Table 15, Demonstrating One and Two Step Offset Tuning from E Standard Tuning

All of this winding would be as a response to the strumming that generates the soundwaves that are then read and analyzed by the rest of the system and the motor responds in a way to turn the tuning peg. All of this, would be used to facilitate the tuning mode the relayed information to the user would be displayed through the LCD screen so that the user will be able to know when to strum or switch to the next string. Additional feedback could be implemented by adding a buzzer and/or an LED that could also be used to alert the user that the tuning of that particular string is complete.

## 22.7 Autotune Mode

The purpose of this section is to demonstrate the manner in which we intend to implement the autotune mode for a positive, intuitive UI/UX experience. At the time of writing this document, we intend to make the Autotune mode the initial mode of operation that the Pick Pocket Tuner would load into after booting up. The idea behind this mode is that the user is able to just turn on the device and tune to whatever the closest string is at, be able to use the on-device buttons to tune to a preset tuning chosen from the library of tunings available, or to choose from a user-defined preset tuning that is recalled from the device memory.

When using the autotune mode without the presets, the idea is that the user would utilize the tuner, assuming that the string isn't too far from whatever the intended string is supposed to be tuned to, by just placing the tuning peg in the peg winder of the Pick Pocket Tuner, and be prompted by the LCD screen to strum so that the device can begin tuning the guitar, as is shown when following the flow chart in Figure X above. Once complete, as with all other modes, the user can either move on to the next string needing to be tuned, or end the tuning process altogether.

The second sub-mode of operation, would entail having accomplished our stretch goal of including/implementing a tuning library that could store both preset tunings, and/or the storage of user-defined tunings for their guitar, or other stringed instruments. What this sub-mode of operation would entail is adding an additional step. This step would be where the user, through interacting with the buttons on the housing of our Pick Pocket Tuner, would lead them to select a tuning to tune to or create a new preset that would be stored based on the tuning that they tell the device what tuning they want as they move through all of the strings.

If choosing from the preset tunings, all the device would do is load the tuning and prompt the user to start from the lowest string, and pluck the string to begin reading/analyzing the frequency, inform the user through the LCD screen and/or a buzzer/LED that the tuning of that string is complete, and then prompt to move to the next string. If there is no next string then the user can simply be done with tuning.

If the user would like to create a new tuning preset for them to use, they would instead select the necessary prompt so that they can begin setting the string as necessary. They can then start to proceed through selecting the note they want the guitar tuned to, tune the guitar, then once tuned save that string in that preset, and move on to the next, repeating the process until all strings are saved/completely tuned.

To recall this user-defined tuning, all it would be is choosing it from the library of tunings as if it were a preset tuning from the library of available tunings. As with the other tuning methods, the feedback for creating a new user-defined tuning would be through the LCD display where the necessary prompts would display to the user instructing them what to do, but it would also give the user the feedback from a buzzer and/or an LED relaying that the step they are currently on is complete, until no other strings remain, or the user is done.

## 22.8 Free Move Mode

If the user selects the free move mode, the directional UI buttons are used to turn the peg winder both clockwise and counterclockwise. For example, the "up" directional button would turn the peg counterclockwise, tightening the string, and the opposite for the "down" directional button, by loosening the string.

The user is still prompted to pluck the string in this mode to learn what the string's frequency value is. This frequency value is then used to provide the display for the closest standard string value it corresponds to. This will be displayed along with the starting frequency and the target frequency will be replaced with the current calculated frequency based on the revolutions from the user's button input.

Using this mode will allow the user to have more freedom with tuning their string if they like to have their frequencies more towards flat or sharp frequencies. Users might also find it more helpful to know which frequency they are tuning for and using this mode to fine tune the peg to that desired frequency.

Using a brushless dc motor will also allow for a smoother transition from rotating the peg clockwise and counterclockwise in succession. As opposed to a stepper motor that was researched before choosing the brushless motor. Having the ability of rotating the peg both clockwise and counterclockwise gives the user more accuracy based on the visual from the display.

This would require the visual to be heavily accurate in real time calculation from the algorithm based off the starting frequency and the number of steps/revolutions in both the

clockwise (positive) and counterclockwise (negative) direction. Requiring the math to be accurate still, but not as accurate as relying purely on the math/algorithm like the other modes.

This mode is opposed to all the other modes as they are heavily based on the mathematical equations and algorithms derived from our research into the number of steps needed to tune to the correct frequency desired. This allows for the user to also see more of the process of personally tuning the string to the correct frequency and being in control of the entire process.

# 23.0 Software Summary

Software was implemented to our project with the ESP8266 microprocessor and with Python as our programming language. Using the uPyCraft programming environment, MicroPython was utilized to easily write the software onto the processor. This software setup was chosen as opposed to Arduino's environment and their programming language C++. Arduino's environment was ultimately not used because of the difficulty to implement the Fast Fourier Transform. Since this transform was an important aspect of the project, MicroPython was implemented and tested on.

The software for the Pick Pocket tuner consists of hierarchal menus to guide the user to tuning the correct string at their desired frequency. This menu is displayed to a TFT LCD screen via a SPI connection. The input vibrational sensor sends its frequency reading to the processor via an analog voltage. The software will read this value for a specified polling time and the resulting voltage wave will be transformed into the frequency domain. After the algorithm decides the amount of voltage to be sent to the motor/peg winder, the software will update the user onto the LCD screen visually and audibly with a voltage sent to a buzzer located on the housing. The software will then repeat with tuning the remaining strings until the user is done.

# 24.0 Project Budget Estimates

For the project budget estimations, we researched most of the components we intend to use for this project. The final table lists roughly how much each component will cost, and how many we will need for the final product. We expect to keep the budget of our final prototype below \$100, but the overall budget of the project will be greater because of early prototypes and testing materials. The table below shows the optimistic cost for the final prototype. This budget will likely be subject to change, especially since we do not have the full design down yet, however we are hopeful about keeping the cost to a minimum.

# 24.1 Final Prototype Cost (Estimated Range)

Components	Quantity	Costs
Battery	1	\$12
Motor	1	\$20
Display screen	1	\$20
DC-DC converter	2	\$13 (total)
Vibration sensor	2	\$13 (total)
On/off switch	1	\$1
buttons/inputs	3	\$0.50 (each)
Peg winder head	1	\$1
Housing	1	\$5
Micro controller	1	\$2
Potential microphone (not factored in costs and	1	\$7
quantity)		
PCB	1	TBD
Total	15	\$88.50 +TBD

Table 16, Estimated Final Cost for Device

Some of the budget estimations may vary due to some supply chain issues that have arisen. Most parts just not being in supply or have too long of expected restock dates that are too far out where some range over a year and other alternative methods for items are required. For one instance is the regulators for the most part are out of stock on most supplier and even third party suppliers and the back order are multiple weeks out if not even more than a year out of stock. Most of the other parts are attained from Amazon as the main supplier for most parts except specific ones such as the motor.

## 24.2 Project Development Costs

Along with other project requirements there are the development costs that will come in and be larger in costs than the actual prototype. These costs will mostly come from buying testing equipment to make sure the specific components work properly to fit the design specifications. These costs will vary largely as the project proceeds in the right direction. The standard development estimate range is around \$500 and could even range up to \$1000. Another part of the development costs is time to learn how the parts work and the time it takes to research the right parts that are need for the job.

## 24.3 Development Cost (Estimated Range)

Components	Quantity	Costs
Snark ST 8 Clip-on Super-Tight Chromatic Tuner	1	\$14
ADXL345 Digital Accelerometer	1	\$17.50
Nema 16 Stepper Motor	1	\$12
Nema 17 Stepper Motor	1	\$15
3D print material 1kg	1	\$20
Node MCU ESP8266	1 (3 pack)	\$15
SN754410NE	5	\$3
L298N Motor Driver	1 (4 pack)	\$10
Piezo Vibration Sensor	1	\$4.95
Piezo Element	4	\$1.50
28byj 5V DC Stepper Motor with Dirvers	1 (5 pack	\$12
12V DC Brushless Stepper Motor	1	\$20
Stepper Driver	1	\$35
Jowoom	1	\$34
Guitar Strings	1 (3 pack)	\$17
Electric Guitar Strings	1 (3 pack)	\$15
Lithium-ion Polymer battery	1	\$12
Boost up Converter 2V-24V	1 (10 pack)	\$11
Adafruit 4410 Micro Lipo charger usb type C	1	\$9
Rocker on /off switch	1 (8pack)	\$9
Tactile Momentary Push Buttons	1 (25 pack)	\$8
1/4 Inch Output Jack	1	\$5
Total Estimated Development Cost Range:	29	\$316.45

Table 17, Estimated Cost for Development of Project

Most of the research costs are going to go towards the vibration sensor which is a key component that is needed for the device to work the best. There are multiple vibration sensors that need to be tested and only on will be chosen which meets the best requirements for the overall system. Another big research cost is going to be getting ahold of the parts themselves due to production delays or costs from manufacturers themselves. Another development cost will be finding the torque needed to turn the pegs of multiple string instruments.

Some instruments mostly being the orchestra styled instruments being the violin or cello, the tuning pegs work slightly different where the pegs must be pushed inwards and turned at the same time to properly be adjusted and tuned. Whereas most of the basic stringed instruments can simply be turned at the peg heads. Now not all the stringed instruments will be tested or can even be tested for since some will not be compliant, for example the harp is a stringed instrument and is somewhat well known, but it does not have peg heads to tune them, and it would take a long time to tune all the strings so it's not a logical

choice. Other instruments that will not be tested are instrument that are more oriental or have oblong peg heads that are meant to be tuned by hand or with a very special tool. As many things that have a basic or friendly peg head design and is a well-known instrument will be trialed and tested. The music department at UCF has agreed to lend us any aid in testing stringed instruments through UCF's music program's students and supply any" Subjects," we may need, which will save costs of having to go out and rent instruments.

There have also been a few issues with the development costs that are big things that should try to be avoided but arise in any case. Most of the issues are buying things then realizing they are wrong or not going to end up actually working for the project. Most of these issues came from trying to pick already end version types of products than testing purpose types of products. Most of them came down to the motor and battery type for what was going to be used. We were already pretty certain on the software side for what software was going to be used and the processor that was going to be up for the job. The next part was finding the components that were mostly going to be compatible to work along-side with the software. There were some issues at first when deciding on the motor which was planned for testing a stepper motor that would meet the torque requirement at first. The first motor that we ended up getting was a Nema 17 stepper motor that did over the amount of torque that was needed to potentially help reach the stretched goals right away. There was one main issue with it being a little too big for the design and heavy also. Then there was the decision to step down from the Nema 17 to a Nema 16 which was about half the size and half the torque but still had enough torque for what was desired.

There was one good thing that came out next and that was buying a Jowoom and seeing the internals of what they used and how they implemented everything together. Getting the Jowoom also saved a substantial amount of spending on the development costs from saving the group of buying a Roadie 3 which would have costed \$129 plus shipping off of Roadies website, but instead we were able to find a Jowoom on eBay for only \$32. That alone saved the spending costs of \$97 for the development costs section. Buying and taking apart the Jowoom gave a lot of insight to finalize the decision of the motor for the final design. Besides accidentally buying a few extraneous parts the budget has mainly been on a good track of getting most of the other proper parts.

# 25.0 Project Milestones

For the project budget estimations, we researched most of the components we intend to use for this project. The final table lists roughly how much each component will cost, and how many we will need for the final product. We expect to keep the budget of our final prototype below \$100, but the overall budget of the project will be greater because of early prototypes and testing materials. The table below shows the optimistic cost for the final prototype. This budget will likely be subject to change, especially since we do not have the full design down yet, however we are hopeful about keeping the cost to a minimum.

Project Task	Assignee	Date	Date Due	Status
		Started		
Decide project idea	All	08/27/2021	09/17/2021	Completed
Identify Parts	All	08/27/2021	10/01/2021	In Progress
Final Report Subtask	S			
D&C v1.0	All	09/07/2021	09/17/2021	Completed
D&C v2.0	All	09/17/2021	10/01/2017	Completed
60-page Draft	All	10/01/2021	11/05/2021	Completed
100-page Draft	All	11/05/2021	11/19/2021	Completed
Final Document	All	11/19/2021	12/07/2021	TBA
Final Design Parts	·	·		
Motor/Motor Driver	Lucas	09/10/2021	10/01/2021	In Progress
Vibration Sensor	Luis	09/10/2021	10/01/2021	Completed
Display	Jamie	09/10/2021	10/01/2021	Completed
System Controller	Luis	09/10/2021	10/01/2021	Completed
Voltage Regulator	Paul	09/10/2021	10/01/2021	Completed
Input Buttons	Jamie	09/10/2021	10/01/2021	Completed
Switch	Lucas	09/10/2021	10/01/2021	Completed
Battery	Paul	09/10/2021	10/01/2021	Completed
Housing	Lucas	09/10/2021	10/01/2021	Completed
PCB	Paul	09/10/2021	10/01/2021	Completed
End of Semester Design Goals				
Acquisition of Parts				In Progress
Final PCB Design				In Progress
Working Prototype				In Progress

Table 18, Project Milestones Chart

# 26.0 Hardware & Software Requirement Specifications Tables

This section is to be utilized as a simple-to-navigate portion of the present documentation, in conjunction with the following section, which relates to the final testing plan that will determine a successful and/or failed implementation of the corresponding Requirement Specifications.

### 26.1 Hardware Requirement Specifications

#### No: 26.1.1

Statement: The Pick Pocket Tuner shall tune the entire guitar within a maximum amount of time.

Source: Team Member Discussions, In-Market Competitors, Technical Research

Dependency: 26.1.3

Conflicts: None

Supporting Materials: In-Market Competition

Evaluation Method: The User will be able to tune a guitar in 5 minutes, ±1 minute

Revision History: Luis Vargas, 11/29/2021, Created Table

### No: 26.1.2

Statement: The Pick Pocket Tuner shall tune a new, individual, string within a maximum amount of time.

Source: Team Member Discussions, In-Market Competitors, Technical Research

Dependency: 26.1.3

Conflicts: None

Supporting Materials: In-Market Competition

Evaluation Method: The User will be able to restring a string and tune it in 3 minutes,  $\pm 1$  minute.

Revision History: Luis Vargas, 11/29/2021, Created Table

### No: 26.1.3

Statement: The Pick Pocket Tuner shall tune the strings to the correct frequency for that string.

Source: Team Member Discussions, In-Market Competitors, Technical Research

Dependency: None

Conflicts: None

Supporting Materials: In-Market Competition

Evaluation Method: The User will be able to tune the string of the instrument (guitar) accurately, within ±5 cents of accuracy

Revision History: Luis Vargas, 11/29/2021, Created Table

#### No: 26.1.4

Statement: The Pick Pocket Tuner shall be able to tune more than 100 strings.

Source: Team Member Discussions, In-Market Competitors, Technical Research

Dependency: 26.1.3

Conflicts: None

Supporting Materials: In-Market Competition

Evaluation Method: The User will be able to tune more than 100 strings before needing to recharge the device

Revision History: Luis Vargas, 11/29/2021, Created Table

#### No: 26.1.5

Statement: The Pick Pocket Tuner shall weigh less than 3 pounds.

Source: Team Member Discussions, In-Market Competitors, Technical Research

Dependency: None

Conflicts: None

Supporting Materials: In-Market Competition

Evaluation Method: The user will not need much strength to use the device.

Revision History: Luis Vargas, 11/29/2021, Created Table

#### No: 26.1.6

Statement: The Pick Pocket Tuner shall have the ability to tune to alternative tunings.

Source: Team Member Discussions, In-Market Competitors, Technical Research

Dependency: 26.1.3

Conflicts: None

Supporting Materials: In-Market Competition

Evaluation Method: The User will be able to tune to tunings such as Drop-D, Drop-C, etc.

Revision History: Luis Vargas, 11/29/2021, Created Table

#### No: 26.1.7

Statement: The Pick Pocket Tuner shall have an easy-to-use physical User Interface.

Source: Team Member Discussions, In-Market Competitors, Technical Research

Dependency: None

Conflicts: None

Supporting Materials: In-Market Competition

Evaluation Method: The User will be able to easily reach and use all the physical components of the device

Revision History: Luis Vargas, 11/29/2021, Created Table

#### No: 26.1.8

Statement: The Pick Pocket Tuner shall be ergonomic, and small enough to fit in one hand.

Source: Team Member Discussions, In-Market Competitors, Technical Research

Dependency: 26.1.7., 26.1.5

Conflicts: None

Supporting Materials: In-Market Competition

Evaluation Method: The User will be able to hold and use the device comfortably with one hand

Revision History: Luis Vargas, 11/29/2021, Created Table

No: 26.1.9

Statement: The Pick Pocket Tuner shall have an easy-to-read display.

Source: Team Member Discussions, In-Market Competitors, Technical Research

Dependency: None

Conflicts: None

Supporting Materials: In-Market Competition

Evaluation Method: The User will be able to read the screen in the majority of light conditions

Revision History: Luis Vargas, 11/29/2021, Created Table

### No: 26.1.10

Statement: The Pick Pocket Tuner shall be able to use a  $\frac{1}{4}$  -inch input jack with a  $\frac{1}{4}$  - inch instrument cable.

Source: Team Member Discussions

Dependency: 26.1.3

Conflicts: None

Supporting Materials: In-Market Competition

Evaluation Method: The User will be able to use the jack/cable combo to tune the guitar as a back-up method of tuning.

Revision History: Luis Vargas, 11/29/2021, Created Table

# 26.2 Software Requirement Specifications

No: 26.2.1

Statement: The Pick Pocket Tuner shall have an easy-to-understand software menu structure

Source: Team Member Discussions, In-Market Competitors, Technical Research

Dependency: 26.1.3

Conflicts: None

Supporting Materials: In-Market Competition

Evaluation Method: The User will be able to easily choose the desired mode of operation

Revision History: Luis Vargas, 11/29/2021, Created Table

### No: 26.2.2

Statement: The Pick Pocket Tuner shall be able to choose between four available modes of operation.

Source: Team Member Discussions, In-Market Competitors, Technical Research

Dependency: 26.2.1

Conflicts: None

Supporting Materials: In-Market Competition

Evaluation Method: The User will be able to choose how they want to utilize the device to tune.

Revision History: Luis Vargas, 11/29/2021, Created Table

#### No: 26.2.3

Statement: The Pick Pocket Tuner shall display the current tuning to the display.

Source: Team Member Discussions, In-Market Competitors, Technical Research

Dependency: 26.1.3

Conflicts: None

Supporting Materials: In-Market Competition

Evaluation Method: The LCD Display will read the current tuning and the user will be able to determine if the tuning is correct or not

Revision History: Luis Vargas, 11/29/2021, Created Table

No: 26.2.4

Statement: The Pick Pocket Tuner shall be able to distinguish between flat and sharp notes

Source: Team Member Discussions, In-Market Competitors, Technical Research

Dependency: 26.1.3

Conflicts: None

Supporting Materials: In-Market Competition

Evaluation Method: The device will be able to display sharp and flat notes to the display for the user to see

Revision History: Luis Vargas, 11/29/2021, Created Table

### No: 26.2.5

Statement: The Pick Pocket Tuner shall be able to differentiate between octaves of the same note.

Source: Team Member Discussions, In-Market Competitors, Technical Research

Dependency: 26.1.3

Conflicts: None

Supporting Materials: In-Market Competition

Evaluation Method: The device will be able to tune a string at an octave-lengthdifference based on frequency

Revision History: Luis Vargas, 11/29/2021, Created Table

#### No: 26.2.6

Statement: The Pick Pocket Tuner shall report accurate notes and frequency values.

Source: Team Member Discussions, In-Market Competitors, Technical Research

Dependency: 26.1.3, 26.2.3, 26.2.4, 26.2.5

Conflicts: None

Supporting Materials: In-Market Competition

Evaluation Method: The device will move the motor according to the guitar's tuning frequency read

Revision History: Luis Vargas, 11/29/2021, Created Table

# 27.0 Final Testing Plan

## 27.1 Objective for Final Testing

The Objective for the hardware and software testing is a simple, and straightforward one, which is to ensure that the final device outlined in this documentation meets the requirements, specifications, and successfully executes/implements the necessary combinations of hardware and software to accomplish the outlined goal: tune a guitar/bass automatically. The assumption for this Test Plan, for all intents and purposes, is that in the final version, the device will accomplish the goal within a reasonable "error-free" experience.

## 27.2 Description of Final Testing Environment

For the Pick Pocket Tuner, the test environment will realistically be physically anywhere that the group will be able to use a guitar/bass. Ideally, since the device is meant to be hand-held and portable, we can implement our testing procedures in various spaces, and settings, including but not limited to a garage, a recording studio, an auditorium, to an empty lecture hall on the UCF campus. The benefit of this is that the testing parameters aren't all necessarily limited by environmental factors, unless specifically and discretely noted. On both the hardware and software sides, the testing parameters outlined throughout this documentation details how the intended use of each component is, and in this section specifically we will assume the previously mentioned parameters will be included in further testing.

For Hardware the Testing Environment is more closely related to the physical environment, in which case, for optimal results, the group will be testing the device in the same location, however using varying guitars with different tuning pegs. Ideally, we will be reaching out to the UCF College of Music to inquire about potentially using one of their practice rooms for testing since they are built for the separation of sound between those being emitted from the inside of the practice room versus those originating from the surrounding hallways. The guitars that are to be initially used for testing will be provided by Lucas Grayford, Paul Grayford, and Luis Vargas.

Lucas' guitar was manufactured by Behringer, model METALIEN. The METALIEN is an electric guitar with an unknown manufacturer of tuners, and as an electric guitar it has a 1⁄4 inch jack for a 1⁄4 inch instrument cable to be used with it. Additionally, this guitar also has a floating bridge, which is also non-branded. Since the bridge is floating, we are going to be "blocking" the floating bridge essentially turning it into a standardized "traditional"

static bridge. Paul's guitar was manufactured by the Indiana Guitar Company, model Scout Black Acoustic. The Scout is an entirely acoustic guitar, which means that there are no electronic components with which to interact with, and has also non-branded tuners. The bridge on this guitar, since it is acoustic, is a standardized "traditional" non-floating bridge and as such, there are no necessary alterations needed to be made. Luis' guitar was manufactured by the ESP guitar company, model is the LTD-DJ600 and for tuners it uses Sperzel Locking Tuners. The DJ600 is an electric guitar, which means it has a ¼ inch jack for a ¼ inch instrument cable, and it also has a Floyd Rose Tremolo Floating Bridge, this typically indicates that the tuning process is significantly more complex as a traditional tuner, however, for Luis' guitar in particular, this Bridge has been blocked off, and it does not "float" but instead operates in the same manner as a traditional standardized guitar bridge.

The brand and specific model of guitar strings to be used for testing is at this time still to be identified, investigated, and reviewed by the group members, due to availability, cost, and/or delivery constraints. For final verification of tuning accuracy, the tuning of the strings individually will be checked against the AXE I/O guitar interface. The AXE I/O interface houses a chromatic tuner, which through the electric guitar's ¼ inch output and an instrument ¼ inch cable, will let us confirm if the pitch that our final device adjusts the string to is correct or not. Additional tools for confirming hardware testing successes and/or failures include but are not limited to items such as oscilloscopes, voltmeters, stopwatch timers, and/or a power supply to be used, as needed for different testing steps. These devices will be implemented in an as-needed basis, and shall be used as a 'safety net' for additional confirmation beyond that of what the Pick Pocket Tuner and the AXE I/O reports as the tuning of the guitar string.

For the software aspect of our Testing Environment, our intended testing environment is a straightforward one. The devices used to interface directly with the ESP8266 will be the extent with which the device will need to be 'ran' on. The compilation of the final software to be tested will be done on these machines, which will then upload onto the ESP8266 for the device to run on-device directly, with the available on-device memory. Information regarding the hardware of the ESP8266 can be referenced above in the section detailing the specifications of the ESP8266. The machines who will be used with interfacing with the ESP8266, shall use an operating system agnostic environment for compiling and uploading the code. This environment, which will also be used for testing is the most recent, up-to-date version of the Arduino IDE software. For both Windows (7 and newer), as well as for MacOS (10.10 or newer) it is Arduino IDE v1.8.16. Beyond these mentioned devices/interfaces, the software testing will be more-or-less done simultaneously with the hardware testing so initially the physical environment, as well as guitars, and hardware used will be the same as the hardware testing environment.

While the testing environments isn't meant to be a 'catch-all' for any and all situations, the reason for detailing this information is to layout a baseline from which to begin the determinations for the device to be marked as a successful product. Additionally, detailing these tools and environments will aid in reducing the number of extraneous variables that could introduce unneeded errors that can affect the results of our testing. As previously

stated, at the time of writing this document, this is what we have currently deemed necessary to complete the final testing for the Pick Pocket Tuner. However, it is entirely within a sizeable possibility that between now and final delivery of the product, the information in this document could be outdated or have been altered to suit the needs of the Senior Design team.

## 27.3 Stopping Criteria

The stopping criteria for each test case will be dependent on a Pass/Fail system. This system will be used for test cases throughout the entire project, to determine how well the individual components will be integrated into the overall system, however they will be incredibly important when the final testing development phase has been reached. If the test case at hand results in a "Pass" rating, we will then move on to the next test case, until a test case "Fail" rating is reached. If a "Fail" rating is reached, the failing test case will be documented, and the hardware/software feature and/or module dependency for that test case is determined. From there, the dependency is then analyzed as part of the system and independently to determine the cause of failure. Once said cause of failure is determined through said analysis, we will attempt to address it immediately. If it can be addressed immediately, we will return the affected to the developer/integrator to determine a solution. If it is determined that the fix cannot be done at the moment, whether due to missing/yet-to-be-implemented features/modules, or as an example due to waiting for hardware to be acquired, the reasoning for this is also documented so that the team can continue with other hardware/software feature/module implementations.

In addition to this, if no errors are found, and integration/development is still underway, the team will re-assess the system and any currently unlisted/undetermined test cases will be constructed to attempt to filter out any false positive "error free" test runs. If all features/module implementations have been completed and the test case run returns with all test cases receiving a "Pass" rating, additional test cases will be constructed at that time to determine the reliability and robustness of the system. Once this is secondary, more extensive testing is completed, if the reports return that all test cases, this includes the original set and the new set, receive a "Pass" rating we will then assess and determine if the product is ready to be considered as a deliverable item. However, if there is a "Fail" rating in these test cases, depending on the test case and cause for failure, we will either work to find a fix or find a work-around as a resolution for the issue, if it is an issue that is determined to be a necessary issue to be fixed. Once no known errors are found after fixing all the "Fail" ratings, the device will be submitted for approval for consideration as a deliverable item.

## 27.4 Description of Individual Test Cases

As it was previously mentioned, this list is neither exhaustive, nor is it a comprehensive list of test cases. At the time of writing this document, we are still determining additional Test Cases to satisfy the Specification Requirements of the Pick Pocket Tuner, so for the time being, the test cases we are initially considering are listed in the tables below.

Test Case Number	1
Test Case Objective	Battery & System Test
Test Case Description	The user will flip the switch on the device providing power to the entire device and it will boot to our "beginning" screen
Test Case Conditions	See Testing Environment.
Expected Results	The device turns on successfully.

Test Case Number	2
Test Case Objective	User Interface Test
Test Case Description	The user will use the display and
	interface elements to navigate through
	the menus.
Test Case Conditions	See Test Environment.
Expected Results	The user will be able to move in and out of all the menu hierarchies.

Test Case Number	3
Test Case Objective	User Interface Test
Test Case Description	Using the UX/UI and display the user will
	be able to change the tuning method to
	utilize.
Test Case Conditions	See Test Environment.
Even a start Discutto	The mean will be able to able meads
Expected Results	The user will be able to change the mode
	of operation from one of those available
	to be selected.

Test Case Number	4
Test Case Objective	Tuning Test
Test Case Description	The user will be able to use the device and tune a string as the string is being plucked.
Test Case Conditions	See Test Environment.
Expected Results	The guitar will be in tune when the strings are strummed at once, or individually.

Test Case Number	5
Test Case Objective	Motor/Tuning Test

Test Case Description	The user will use the device to signal the device that there is a new string added.
Test Case Conditions	See Test Environment.
Expected Results	The new string will be re-strung to a yet- to-be-decided frequency. Left to be ready for "final tuning"

Test Case Number	6
Test Case Objective	Tuning Test
Test Case Description	The device will assist the user in tuning the guitar faster than the human would be able to do so manually.
Test Case Conditions	See Test Environment.
Expected Results	The time it takes to tune a single string will be under 30 seconds.

Test Case Number	7
Test Case Objective	Restring/Tuning Test
Test Case Description	While in the appropriate tuning mode, the
	user will be able to restring and tune a
	new string on the guitar faster than a
	human would be able to do so manually.
Test Case Conditions	See Test Environment.
Expected Results	The time for this process will be under 3
	minutes.

Test Case Number	8
Test Case Objective	Motor/User Interface Test
Test Case Description	The user will be able to use the user interface to manually drive the motor
Test Case Conditions	See Test Environment.
Expected Results	The motor turns in one of two directions for as long as the corresponding button is held down.

Test Case Number	9
Test Case Objective	Tuning Test
Test Case Description	The device's components correctly
	transfer the vibrational frequencies

	through the housing/components to the piezoelectric disc for analysis.
Test Case Conditions	See Test Environment.
Expected Results	The device is able to interpret a string vibrating at a given frequency, after the string is plucked.

Test Case Number	10
Test Case Objective	Tuning Test
Test Case Description	The user is able to use the interface to tune strings to different, i.e. alternate, tunings
Test Case Conditions	See Test Environment.
Expected Results	The tunings of the strings reflect the desired tuning from the user.

Test Case Number	11
Test Case Objective	Battery Test
Test Case Description	The battery life will be tested to determine how long the operational capacity will be.
Test Case Conditions	See Test Environment.
Expected Results	The device will be able to run all of the components simultaneously and tune strings on a guitar.

Test Case Number	12
Test Case Objective	Weight Test
Test Case Description	The device will be weighed once all
	components are acquired.
Test Case Conditions	See Test Environment.
Expected Results	The device will be weighed with the housing to determine the overall weight of the device.

Test Case Number	13
Test Case Objective	User Interface Test
Test Case Description	The UI of the device will be determined
-	how user-friendly and intuitive the
	controls are based on how long it takes to

	change the mode of operation until the device is ready to tune a string.
Test Case Conditions	See Test Environment.
Expected Results	The user will be able to change between menus/modes of operation and select the desired information in a easy-to-use manner.

Test Case Number	14
Test Case Objective	Tuning Test
Test Case Description	The device will be able to analyze the lower frequency from a bass guitar string and tune it.
Test Case Conditions	See Test Environment.
Expected Results	The bass guitar string will be in tune

Test Case Number	15
Test Case Objective	Ergonomics Test
Test Case Description	The device will take shape based on designs described as ergonomic and comfortable.
Test Case Conditions	See Test Environment.
Expected Results	Comfortable to hold and use

Test Case Number	16
Test Case Objective	User Interface Test
Test Case Description	The buttons on the device will be able to
	navigate in the desired direction and
	select the desired item.
Test Case Conditions	See Test Environment.
Expected Results	The user will be able to use buttons and the display to navigate and use the device

Test Case Number	17
Test Case Objective	User Interface Test
Test Case Description	The necessary, relevant, information will be displayed on the device's display.
Test Case Conditions	See Test Environment.

Expected Results	The user will be able to use visual feedback to make a decision if the string
	is in the tuning they want yet or not.

Test Case Number	18
Test Case Objective	Tuning Test
Test Case Description	The tuning process of the string doesn't take a long time for each string. The device is able to handle the calculations needed, and provide the necessary signals to turn the motor appropriately
Test Case Conditions	See Test Environment.
Expected Results	The tuning is a lag free experience, and the tuning isn't plagued with processing lag.

Test Case Number	19	
Test Case Objective	Tuning/ESP8266 Test	
Test Case Description	The device is able to store a	
	predetermined tuning for ease-of-use	
Test Case Conditions	See Test Environment.	
Expected Results	The default tuning to tune to when the device boots up is E-Standard Tuning.	

Test Case Number	20	
Test Case Objective	Display/Tuning Test	
Test Case Description	The device will display the correct tuning,	
	and frequency, when note is flat.	
Test Case Conditions	See Test Environment.	
Expected Results	The display will inform the user that the	
	string being plucked is X note but flat	

21	
Display/Tuning Test	
The device will display the correct tuning,	
and frequency, when the note is sharp.	
See Test Environment.	

Expected	Results

## 27.5 Trace of Individual Test Cases to Requirements

The purpose of this table below, is to begin mapping the previously outlined test cases to the requirement specifications. This will serve as a starting point to be able to determine if the Pick Pocket Tuner is ready to receive the mark of "Complete". However, as previously stated, the test cases and the results are still evolving based on a multitude of factors, so the information in this, and other tables, is subject to change.

Req. ID	Req. Description	Test Case Reference	Status
26.1.1	The Pick Pocket Tuner shall tune an entire guitar within a maximum amount of time.	1, 3, 4, 6, 7, 9, 10, 11, 14, 18, 19, 20	In Progress
26.1.2	The Pick Pocket Tuner shall tune a new, individual string, within a maximum amount of time.	1, 3, 4, 5, 6, 7, 9, 10, 11, 14, 18, 19, 20	In Progress
26.1.3	The Pick Pocket Tuner shall tune the strings to the correct frequency for that string.	1, 3, 4, 5, 6, 7, 9, 10, 11, 14, 17, 18, 19, 20	In Progress
26.1.4	The Pick Pocket Tuner shall be able to tune more than 100 strings.	1, 3, 4, 5, 6, 7, 9, 10, 11, 14, 18, 19, 20	In Progress
26.1.5	The Pick Pocket Tuner shall weigh less than 3 pounds.	1, 3, 4, 11, 13, 14, 15, 16, 17,	In Progress
26.1.6	The Pick Pocket Tuner shall have the ability to tune to alternate tunings.	1, 2, 3, 4, 6, 7, 9, 10, 11, 14, 17, 18, 19, 20	In Progress
26.1.7	The Pick Pocket Tuner shall have an easy-to-use Physical User Interface.	1, 2, 3, 4, 6, 7, 8, 9, 10, 13, 15, 16, 17,	In Progress
26.1.8	The Pick Pocket Tuner shall be ergonomic, and small enough to fit in one hand.	1, 2, 3, 4, 8, 9, 11, 13, 14, 15, 16, 17,	In Progress

26.1.9	The Pick Pocket Tuner shall have an easy-to-read display.	1, 2, 3, 4, 5, 6, 7, 9, 10, 14, 17, 19, 20	In Progress
26.1.10	The Pick Pocket Tuner shall be able to use a ¼ inch input jack with a ¼ inch instrument cable.	1, 4, 6, 7, 10, 11, 18,	In Progress
26.2.1	The Pick Pocket Tuner shall have an easy-to-understand software menu structure.	1, 2, 3, 5, 6, 7, 8, 10, 14, 16, 17,	In Progress
26.2.2	The Pick Pocket Tuner shall be able to choose between four available modes of operation.	1, 2, 3, 5, 6, 7, 8, 10, 16, 17,	In Progress
26.2.3	The Pick Pocket Tuner shall display the current tuning to the display.	1, 3, 4, 5, 6, 7, 9, 10, 11, 14, 17, 19, 20	In Progress
26.2.4	The Pick Pocket Tuner shall be able to distinguish between flat and sharp notes.	1, 3, 4, 5, 6, 7, 9, 10, 14, 17, 18, 19, 20	In Progress
26.2.5	The Pick Pocket Tuner shall be able to differentiate between octaves of the same note.	1, 3, 4, 5, 6, 7, 9, 10, 14, 17, 18, 19, 20	In Progress
26.2.6	The Pick Pocket Tuner shall report accurate notes and frequency values.	1, 3, 4, 5, 6, 7, 9, 10, 14, 17, 18, 19, 20	In Progress

# 28.0 Conclusion

The experience of designing this project has been very educational and encouraging. It allowed our team the opportunity to learn much more than we did before, not only in the designing aspect, but also in the day-to-day real world challenges engineers face on a regular basis. Whether that be solving a design flaw, supply chain issues, team meeting efficiency, collaboration with teammates and many other aspects we do not learn about from a textbook, this experience provided us with valuable knowledge on how to tackle common issues in the engineering realm. While our academic curriculum has given us the necessary tools to successfully complete this project, the reality is that this project has exposed each-and-everyone of us in the group to the different steps necessary in the product development process, from inception to final product delivery. We are excited and optimistic about the outcome of our project, even with the challenges we will face while assembling our device.

# Bibliography

- Ada, Lady. "Li-Ion & LiPoly Batteries." *Adafruit Learning System*, 6 Dec. 2021, <u>https://learn.adafruit.com/li-ion-and-lipoly-batteries/proper-charging</u>.
- "A440 (Pitch Standard)." *Wikipedia*, Wikimedia Foundation, 27 Nov. 2021, <u>https://en.wikipedia.org/wiki/A440\_(pitch\_standard)</u>.
- "Brushless DC Motor vs. AC Motor vs. Brushed Motor." Oriental Motor U.S.A. Corp., <u>https://www.orientalmotor.com/brushless-dc-motors-gear-</u> <u>motors/technology/AC-brushless-brushed-</u> <u>motors.html?gclid=CjwKCAiAhreNBhAYEiwAFGGKPDWLT4VICIx25Se5uYD</u> <u>dfa0hdppbdn4xKDQiR9ayByDR-rdY74ZJbBoCpK4QAvD\_BwE</u>.
- "Designing an Electric Guitar with Shapes." *TeachRock*, 22 Feb. 2021, <u>https://teachrock.org/lesson/designing-an-electric-guitar-with-shapes/</u>.
- "ESP LTD DJ-600 Dan Jacobs | ZZounds." *Www.zzounds.com*, <u>https://www.zzounds.com/item--ESPDJ600</u>.
- "FIT0441\_BRUSHLESS\_DC\_MOTOR\_WITH\_ENCODER\_12V\_159RPM." *DFRobot*, <u>https://wiki.dfrobot.com/FIT0441\_Brushless\_DC\_Motor\_with\_Encoder\_12V\_1</u> <u>59RPM</u>.
- "Fourier Transform in Python Vibration Analysis." *AlphaBold*, 2 Mar. 2021, <u>http://www.alphabold.com/fourier-transform-in-python-vibration-analysis/</u>. "Guitar Tuning Machines from Sperzel." *Www.sperzel.com*, www.sperzel.com/guitar-
- "Guitar Tuning Machines from Sperzel." Www.sperzel.com, <u>www.sperzel.com/guitar-</u> tuners.php.
- "How to Properly Connect Lithium Batteries in Series and in Parallel." *Wsd*, 1 Mar. 2019, <u>https://www.lithium-battery-factory.com/ithium-batteries-parallel/</u>.
- "How to Tune the Guitar to Standard Tuning." *Www.guitar-Chord.org*, <u>www.guitar-chord.org</u>, <u>www.guit</u>
- "How to Use the Stratocaster Pickup Selector Switch." *Www.fender.com*, <u>www.fender.com/articles/tech-talk/sounds-aplenty-the-stratocaster-pickup-selector-switch</u>.
- "Inductor Placement: Basic Knowledge." *ROHM TECH WEB: Technical Information Site of Power Supply Design*, <u>https://techweb.rohm.com/knowledge/dcdc/dcdc\_pwm/dcdc\_pwm04/9321</u>.
- "JOWOOM T2 Smart Automatic Guitar Tuner Peg String Winder for Guitar Chromatic Us." *EBay*, <u>https://www.ebay.com/itm/133889033602?chn=ps&\_trkparms=ispr%3D1&am</u>

data=enc%3A15-

djjHG3TxCbDkMqqaaAAw95&norover=1&mkevt=1&mkrid=711-117182-37290-

<u>0&mkcid=2&itemid=133889033602&targetid=1262906534602&device=c&mkt</u> ype=&googleloc=9012409&poi=&campaignid=15275224983&mkgroupid=131 097072938&rlsatarget=pla-

1262906534602&abcld=9300697&merchantid=101492064&gclid=CjwKCAiAh reNBhAYEiwAFGGKPFQFowQx8HS73pbnVZhCFv1ftcTEQuzyFqCv9ZSv4oi V203XVDM\_iRoCwjsQAvD\_BwE

"Measuring Vibration: The Complete Guide | Brüel & Kjær." *Www.bksv.com*, www.bksv.com/en/knowledge/blog/vibration/measuring-vibration.

"Piezo Vibration Sensor Hookup Guide - Learn.sparkfun.com." *Learn.sparkfun.com*, <u>https://learn.sparkfun.com/tutorials/piezo-vibration-sensor-hookup-guide/all</u>.

"Piezoelectric Pressure Sensors." *Avnet*, <u>https://www.avnet.com/wps/portal/abacus/solutions/technologies/sensors/pressure-sensors/core-technologies/piezoelectric/</u>.

- "Piezoelectric Sensors How Do Piezoelectric Sensors Work." *Sensor Works*, 3 Dec. 2019, <u>www.sensor-works.com/how-do-piezoelectric-sensors-work/</u>.
- "Placement of Inductors: Basic Knowledge." *ROHM TECH WEB: Technical Information Site of Power Supply Design*, Tech Web, 7 Dec. 2017, <u>https://techweb.rohm.com/knowledge/dcdc/dcdc\_pwm/dcdc\_pwm03/3254</u>.
- "Pure Tone Mono Multi-Contact 1/4" Output Jack." *Pure Tone Technologies*, <u>https://puretonetechnologies.com/products/pure-tone-multi-contact-1-4-output-jack</u>.
- "Scout BK." Indiana Guitar Company, <u>www.indianaguitarcompany.com/scout-black.html</u>.

"Software." Www.arduino.cc, www.arduino.cc/en/software.

- "Stepper vs Servo." *Tutorial: Stepper vs Servo*, <u>https://www.amci.com/industrial-</u> <u>automation-resources/plc-automation-tutorials/stepper-vs-servo/</u>.
- "The String Family: Instruments, History & Facts Video & Lesson Transcript | Study.com." *Study.com*, 2019, <u>https://study.com/academy/lesson/the-string-family-instruments-history-facts.html</u>.

"What Is a Piezoelectric Sensor? - Utmel." *Www.utmel.com*, <u>www.utmel.com/blog/categories/sensors/what-is-a-piezoelectric-sensor</u>. *AXE I/O*, http://www.ikmultimedia.com/products/axeio/index.php?p=specs.

Belokobylskiy, Ivan. "St7789py\_mpy." *GitHub*, https://github.com/devbis/st7789py\_mpy/blob/master/st7789py.py. Frequencies of Musical Notes, <u>https://pages.mtu.edu/~suits/notefreqs</u>.

Industries, Adafruit. "Buzzer 5V - Breadboard Friendly." *Adafruit Industries Blog RSS*,

https://www.adafruit.com/product/1536?gclid=CjwKCAiAhreNBhAYEiwAFGG KPMRSK4GWxT5ykCDRAdUEalYp7kv5BtQm\_5SA5EDeYfPiEk45zi7BoCQkAQAvD\_BwE.

- Industries, Band. "Roadie Automatic Guitar Tuner." *Roadie Music's Automatic Tuners*, <u>https://www.roadiemusic.com/roadie3?gclid=CjwKCAiAhreNBhAYEiwAFGGK PMOMM9OG3GPRvfUm8dTntVZuZueJNEqLsKVcnPJUSMaBilh0qSjVTRoC X-YQAvD\_BwE</u>.
- Kuklovskaia Elizaveta. "DP." *Amazon*, "Books by Mail" Pub. Co., <u>https://www.amazon.com/dp/B00J2QET64?psc=1&ref=ppx\_yo2\_dt\_b\_produc</u> <u>t\_details</u>.
- Kuklovskaia Elizaveta. "DP." *Amazon*, "Books by Mail" Pub. Co., <u>https://www.amazon.com/dp/B015RQ97W8?psc=1&ref=ppx\_yo2\_dt\_b\_produ</u> <u>ct\_details</u>.
- Kuklovskaia Elizaveta. "DP." *Amazon*, "Books by Mail" Pub. Co., <u>https://www.amazon.com/dp/B01E38OS7K?psc=1&ref=ppx\_yo2\_dt\_b\_produ</u> <u>ct\_details</u>.
- Kuklovskaia Elizaveta. "DP." *Amazon*, "Books by Mail" Pub. Co., <u>https://www.amazon.com/dp/B07BK1QL5T?psc=1&ref=ppx\_yo2\_dt\_b\_produ</u> <u>ct\_details</u>.
- Kuklovskaia Elizaveta. "DP." *Amazon*, "Books by Mail" Pub. Co., <u>https://www.amazon.com/dp/B07RNBJK5F?psc=1&ref=ppx\_yo2\_dt\_b\_produ</u> <u>ct\_details</u>.
- Kuklovskaia Elizaveta. "DP." *Amazon*, "Books by Mail" Pub. Co., <u>https://www.amazon.com/dp/B07XC5KB8D?ref=ppx\_yo2\_dt\_b\_product\_detai</u> <u>ls&th=1</u>
- Kuklovskaia Elizaveta. "DP." *Amazon*, "Books by Mail" Pub. Co., <u>https://www.amazon.com/dp/B08168GWVJ?psc=1&ref=ppx\_yo2\_dt\_b\_produ</u> <u>ct\_details</u>.

LeVan, John, et al. "The ABCs of Output Jacks." Premier Guitar, 9 Sept. 2021, <u>https://www.premierguitar.com/diy/guitar-shop-101/guitar-jack-wiring</u>.

- Libretexts. "Pitch- Sharp, Flat, and Natural Notes." *Humanities LibreTexts*, Libretexts, 11 Apr. 2021, <u>https://human.libretexts.org/Bookshelves/Music/Book:\_Understanding\_Basic\_Music\_Theory\_(Schmidt-Jones)/01:\_Notation\_-\_Pitch/1.03:\_Pitch-\_\_\_Sharp\_Flat\_and\_Natural\_Notes.</u>
- Ltd, Magnolia International. "Behringer | Product | GPK836BK." *Www.behringer.com*, <u>www.behringer.com/product.html?modelCode=P0836</u>.
- Maklin, Cory. "Fast Fourier Transform." *Medium*, Towards Data Science, 29 Dec. 2019, https://towardsdatascience.com/fast-fourier-transform-937926e591cb.
- Rembor, Kattni. "Adafruit 1.3' and 1.54' 240x240 Wide Angle TFT LCD Displays." *Adafruit Learning System*, <u>https://learn.adafruit.com/adafruit-1-3-and-1-54-</u> 240-x-240-wide-angle-tft-lcd-displays?view=all.
- Rowley, Jared. "What Is the Difference Between a Mono And Stereo Jack?" *Guitarandampparts.com*, Sheehan Enterprizes, 24 June 2019, <u>https://guitarandampparts.com/2019/06/24/what-is-the-difference-between-a-mono-and-stereo-jack/.</u>
- Simple Projects, et al. "Interfacing Arduino with ST7789 TFT Display Graphics Test Example." *Simple Projects*, 3 Sept. 2019, <u>https://simple-circuit.com/arduino-st7789-ips-tft-display-example/</u>.

Study.com, 2021, <u>https://study.com/cimages/multimages/16/violinconstruction.jpg</u>. Success, Dan-Fret. "What Are the Guitar String Frequencies?" *Fret Success - Guitar Tuition*, 26 Mar. 2019, <u>http://fretsuccess.com/what-are-the-guitar-string-frequencies/</u>.

- Swagatam. "Designing a Customized Battery Charger Circuit." *Homemade Circuit Projects*, 31 Oct. 2020, <u>https://www.homemade-circuits.com/designing-</u> <u>customized-battery-charger/</u>.
- Taifur, and Instructables. "Seven pro Tips for ESP8266." *Instructables*, Instructables, 24 Apr. 2018, <u>https://www.instructables.com/ESP8266-Pro-Tips/</u>.
- Team, The Arduino. "Stepper Speed Control." *Arduino*, <u>https://www.arduino.cc/en/Tutorial/LibraryExamples/StepperSpeedControl</u>.
- Thingiverse.com. "Superior Universal Guitar String Winder Quick Tuner by Mordraden." *Thingiverse*, <u>https://www.thingiverse.com/thing:46231</u>.